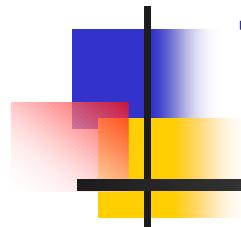


Dynamics of Parallel-Type and Serial-Type Charge Pump Circuits for High Voltage Generation




K. Kashiwase, H. Kobayashi, N. Kuroiwa,
N. Hayasaka, S. Inaba

EE Dept. Gunma University, Japan


M. Takao, T. Suzuki, T. Iijima, S. Kawai

Sanyo Electric Co. Ltd., Japan

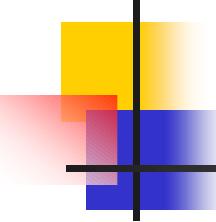

Contents

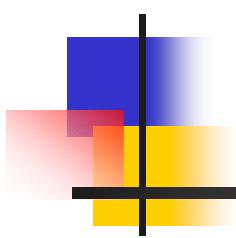
1. Research Background & Goal
2. Parallel-Type Charge Pump
 - Transient Analysis
 - Steady State Analysis
3. Serial-Type Charge Pump
 - Steady State Analysis
 - Comparison of Parallel- and Serial-types
4. Summary



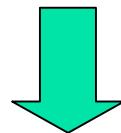
1. Research Background & Goal


Research Background

- Mobile equipment prevails everywhere.
- Mobile phone, Digital still camera, PDA



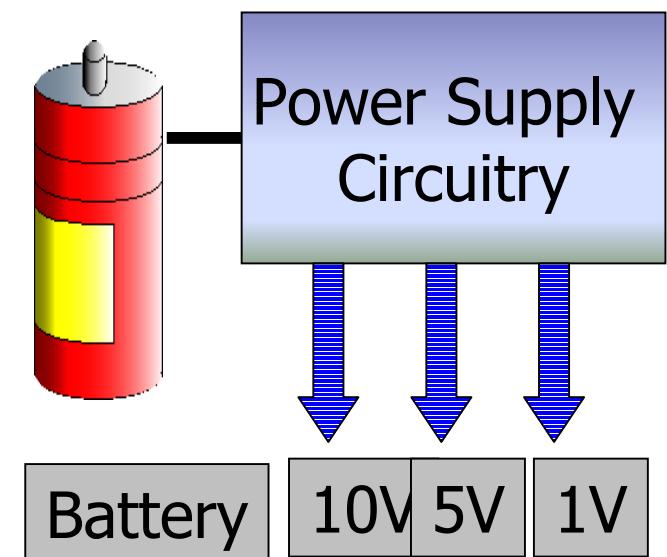- Small size, High efficiency
- High- and low-voltage multiple supplies




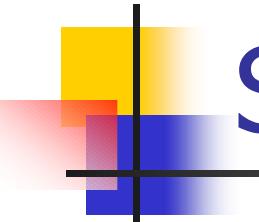

Switching Regulator

- Merit
 - High efficiency
 - Continuously varying output voltage
 - Large output current

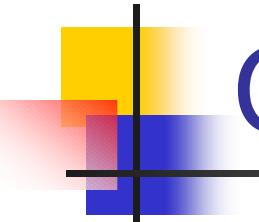- Demerit
 - Coils are required. ➔ bulky and costly
 - Switching noise




Charge Pump Circuit


- Merit
 - No coils
 - Less noise
- Demerit
 - Low efficiency
 - Small output current
 - Output voltage = $2V_{dd}$, $3V_{dd}$, $4V_{dd}$, ...

Our Charge Pump Circuit Implementation

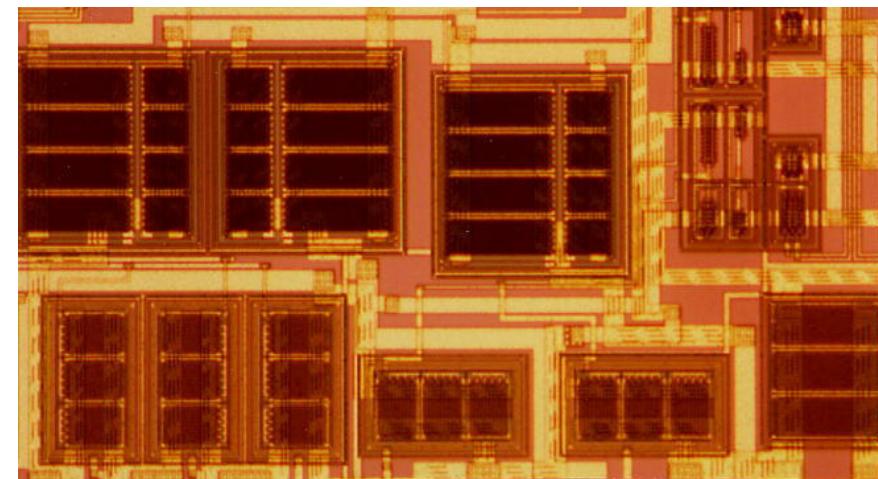- Fabricated in Sanyo Process.
- Commercialization has started.
- Applications:
 - PDA (Personal Digital Assistance)
 - DSC (Digital Still Camera)
 - Mobile Phone




Chip photo: 3.99mm × 4.35mm

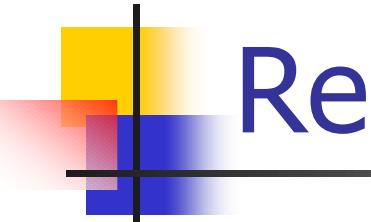

Research Goal

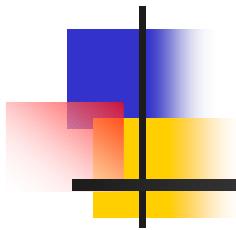- To establish the design methodology of charge pump circuits
- To compare two types of charge pump circuits:
 - Parallel-type (Dickson-type)
 - Serial-type (Switched-capacitor type)




2. Parallel-type Charge Pump Circuit

2.1 Transient Analysis

- Node Voltage
- Energy Flow

2.2 Steady State Analysis

- Output Voltage
- Efficiency

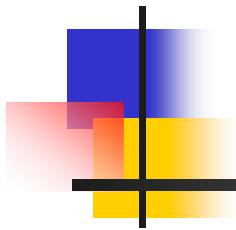

2. Parallel-type Charge Pump Circuit

2.1 Transient Analysis



- Node Voltage
- Energy Flow

2.2 Steady State Analysis


- Output Voltage
- Efficiency

Parallel-type (Dickson-type) Charge Pump Circuit

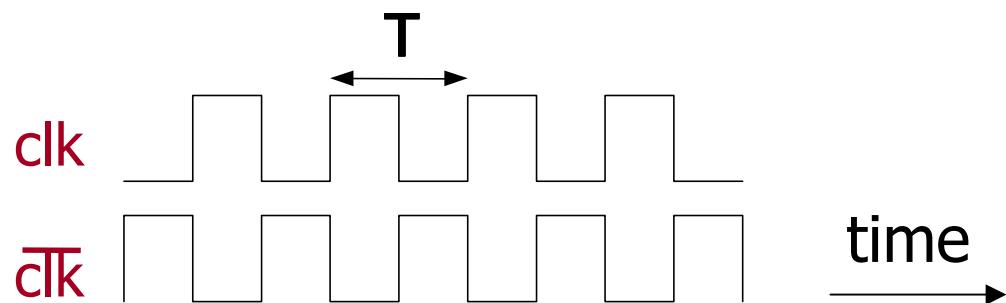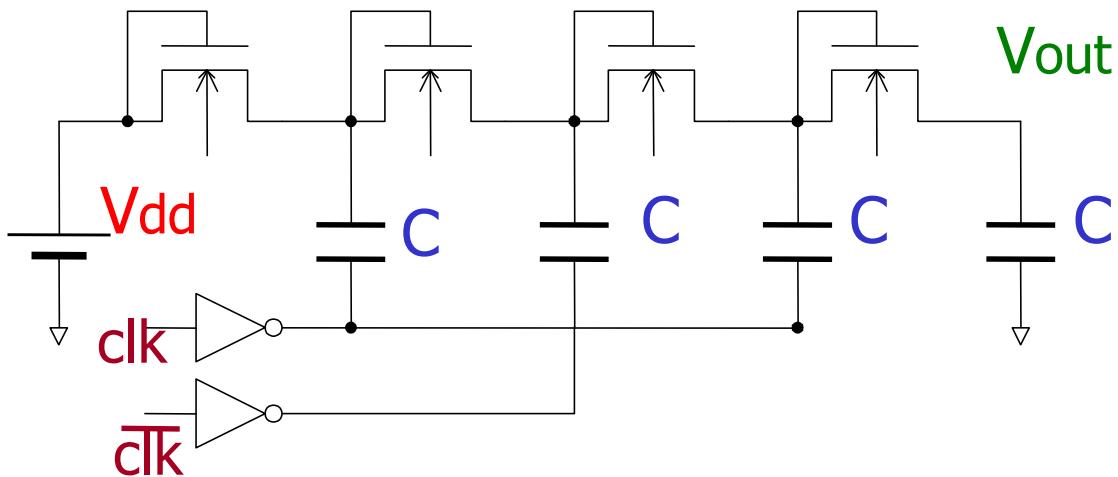- Input V_{dd}
- Output V_{out}
- Diode-connected MOSFETs
- Capacitors C
- Clock clk , \bar{clk}




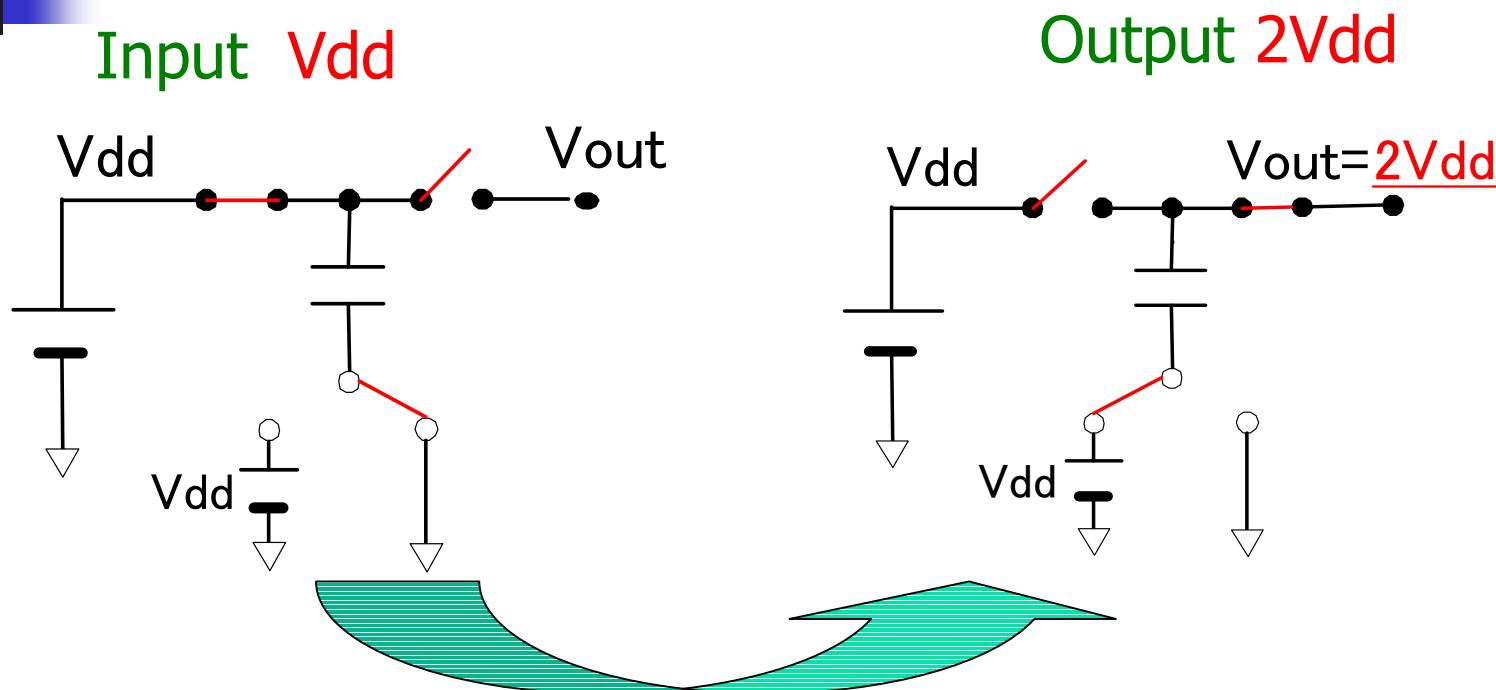Principle of Parallel-type Charge Pump Circuit



- A parallel-type charge pump circuit is cascade of the above circuit.

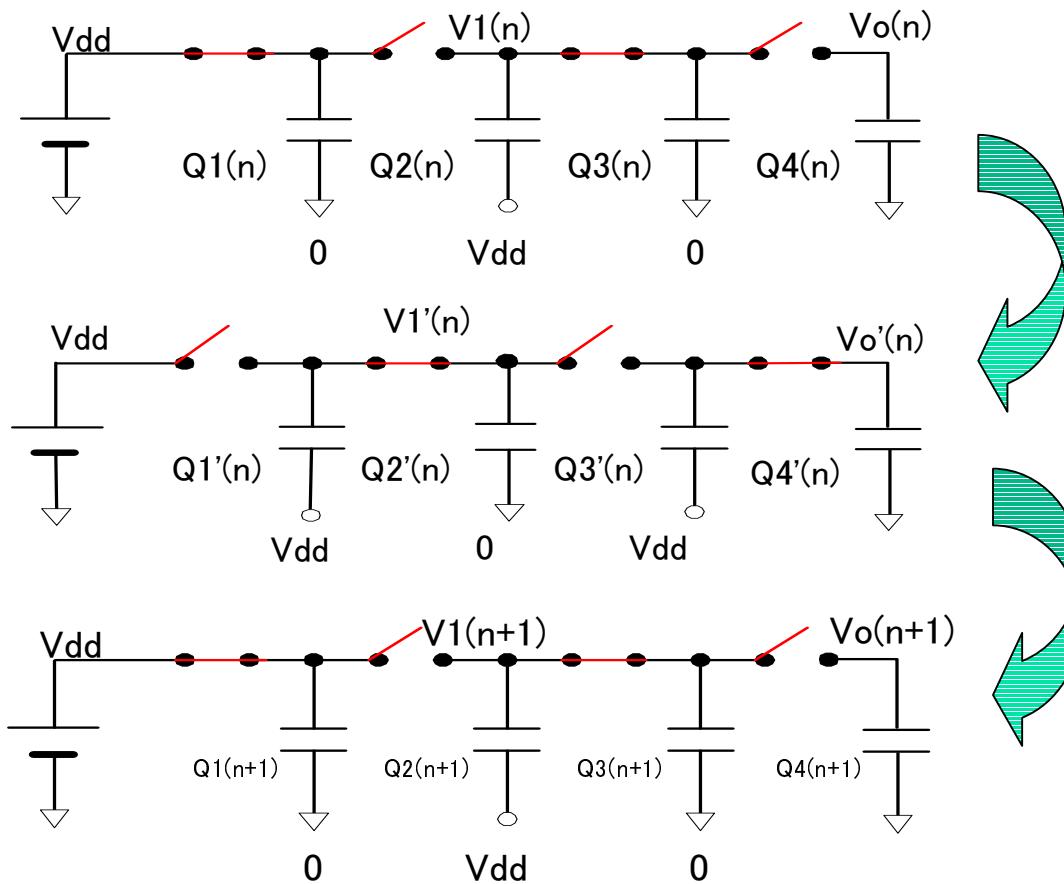State Transition of 3-stage Charge Pump Circuit




at time n

at time n'

at time $n+1$

Time n vs. Time n'

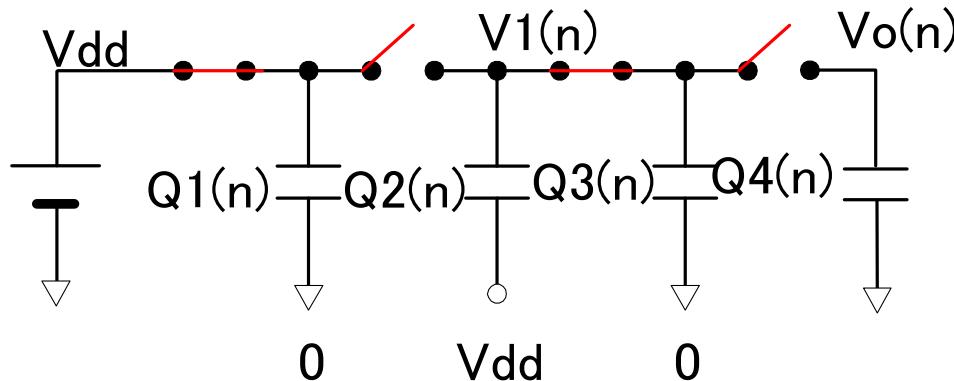


At time n

$$Q1(n) = CV_{dd}$$

$$Q2(n) = C[V1(n) - V_{dd}]$$

$$Q3(n) = CV1(n)$$

$$Q4(n) = CVo(n)$$

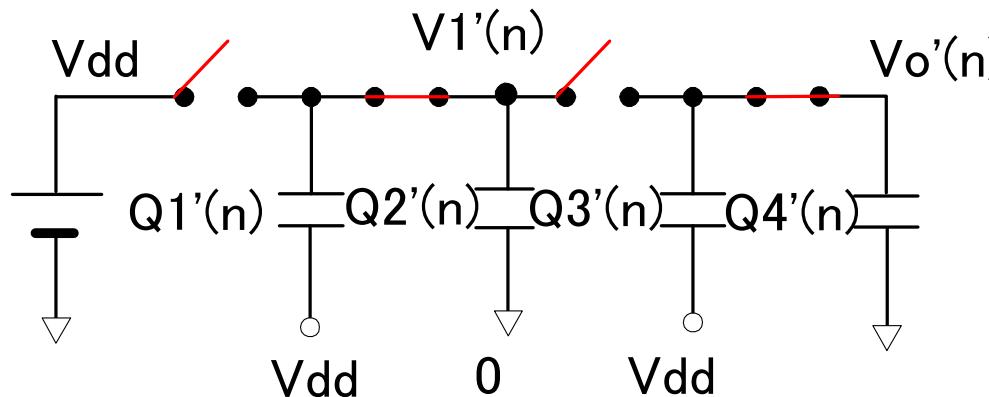

At time n'


$$Q1'(n) = C[V1'(n) - V_{dd}]$$

$$Q2'(n) = CV1'(n)$$

$$Q3'(n) = C[Vo'(n) - V_{dd}]$$

$$Q4'(n) = CVo'(n)$$

Time n vs. Time n'

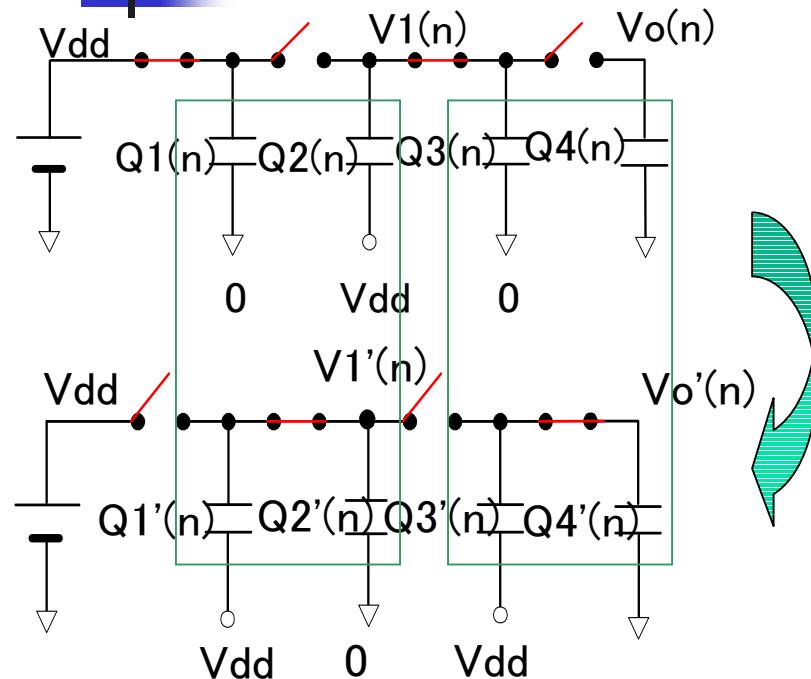

From charge conservation law

$$Q1(n) + Q2(n) = Q1'(n) + Q2'(n)$$

$$Q3(n) + Q4(n) = Q3'(n) + Q4'(n)$$

$$\therefore CV_{dd} + C[V1(n) - V_{dd}] =$$

$$C[V1'(n)V_{dd}] + CV1'(n)$$


$$CV1(n) + Cvo(n) =$$

$$C[vo'(n) - V_{dd}] + Cvo'(n)$$

$$V1'(n) = [V1(n) + V_{dd}] / 2$$

$$vo'(n) = [V1(n) + vo(n) + V_{dd}] / 2$$

Time n vs. Time n+1

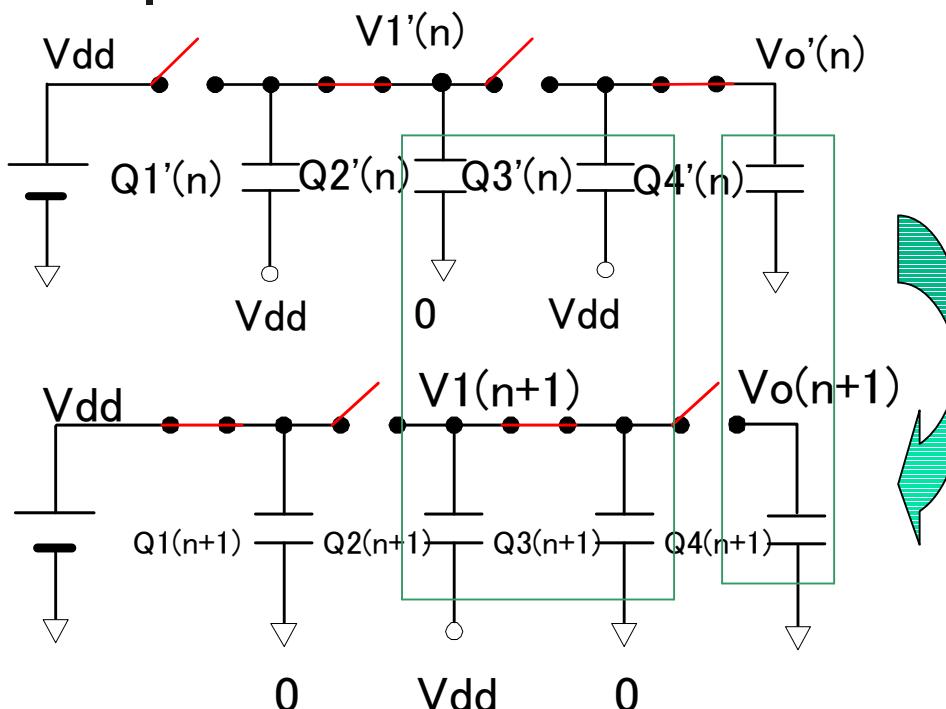

From charge conservation law

$$Q2(n+1) + Q3(n+1) =$$


$$Q2'(n) + Q3'(n)$$

$$\therefore C[V1(n+1) - Vdd] + CV1(n+1) =$$

$$CV1'(n) + C[Vo'(n) - Vdd]$$

$$Vo(n+1) = [V1(n) + Vo(n) + Vdd] / 2$$
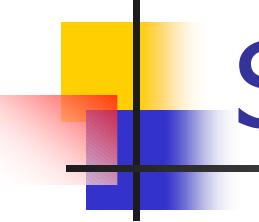
$$V1(n+1) = [2V1(n) + Vo(n) + 2Vdd] / 2$$




State-Space Approach

- State equation

$$\begin{bmatrix} Vo(n+1) \\ V1(n+1) \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & \frac{1}{2} \\ \frac{1}{4} & \frac{1}{2} \end{bmatrix} \begin{bmatrix} Vo(n) \\ V1(n) \end{bmatrix} + \begin{bmatrix} \frac{1}{2}Vdd \\ \frac{1}{2}Vdd \end{bmatrix}$$

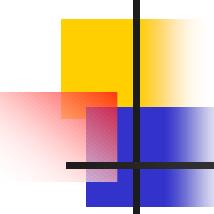- This **state-space approach** can be used for a general **N-stage** charge pump circuit.



Node Voltage Formula

$$V_{O(n)} = \frac{1}{2}(\lambda_1^n + \lambda_2^n)V_{O(0)} + \frac{1}{\sqrt{2}}(\lambda_1^n - \lambda_2^n)V_1(0) \\ + \left(\frac{-2\sqrt{2}-3}{\sqrt{2}}\lambda_1^n - \frac{2\sqrt{2}-3}{\sqrt{2}}\lambda_2^n + 4 \right)Vdd \quad \dots \quad \textcircled{7}$$


$$V_1(n) = \frac{1}{\sqrt{2}}(\lambda_1^n - \lambda_2^n)V_{O(0)} + \frac{1}{2}(\lambda_1^n + \lambda_2^n)V_1(0) \\ + \left(\frac{-3-2\sqrt{2}}{2}\lambda_1^n + \frac{2\sqrt{2}-3}{2}\lambda_2^n + 3 \right)Vdd \quad \dots \quad \textcircled{8}$$

Where $\lambda_1 = (2+\sqrt{2})/4 < 1$, $\lambda_2 = (2-\sqrt{2})/4 < 1$.


\therefore as $n \rightarrow \infty$, $\lambda_1^n \rightarrow 0$, $\lambda_2^n \rightarrow 0$,

$V_{O(\infty)} = 4Vdd$, $V_1(\infty) = 3Vdd$.

Energy Flow When Charging Capacitor

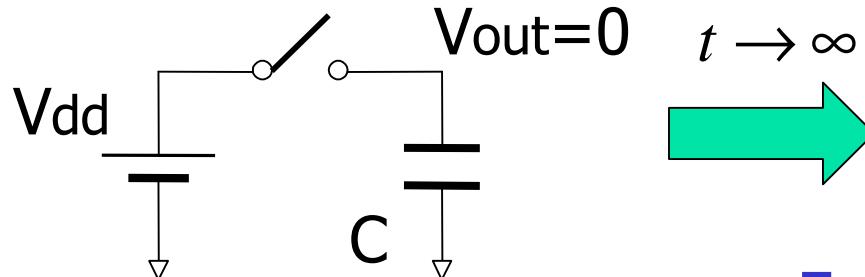

$$E_{sup} = CV_{dd}^2$$

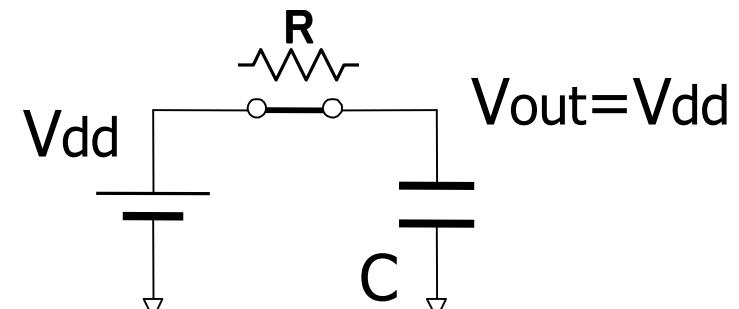

$$E_{cap} = \frac{1}{2}CV_{dd}^2$$


E_{sup}: Total supplied energy from V_{dd}

E_{loss}: Total dissipated energy through R

E_{cap}: Stored energy in C

$$E_{sup} = E_{loss} + E_{cap}, \quad E_{loss} = E_{cap}$$

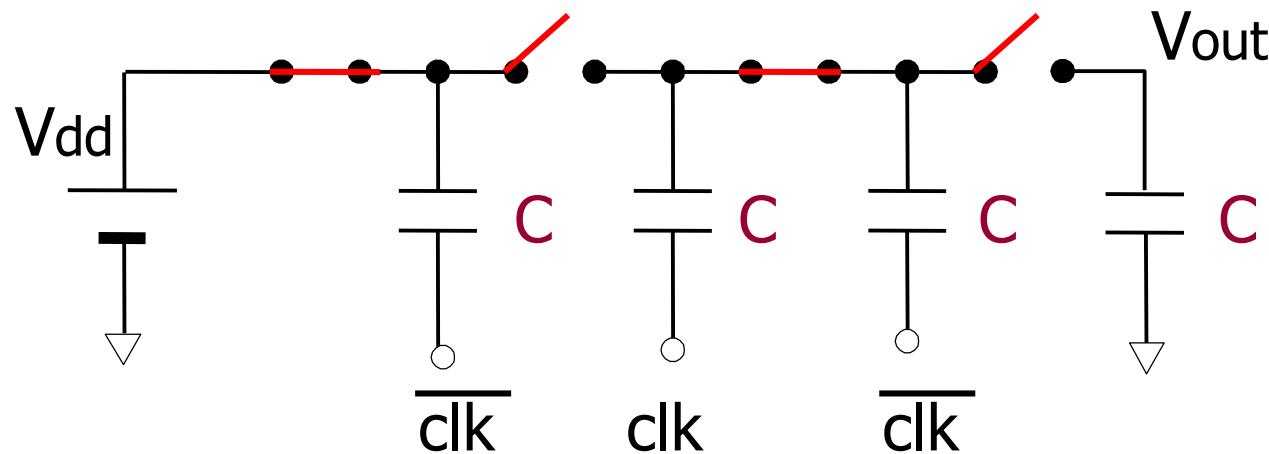Ideal Parallel-type Charge Pump in Transient State




At $t=0$, charges in all capacitors are zero.

E_{sup} : Total supplied energy from V_{dd} , clock drivers

$t \rightarrow \infty$ E_{loss} : Total dissipated energy through switches

E_{cap} : Stored energy in capacitors
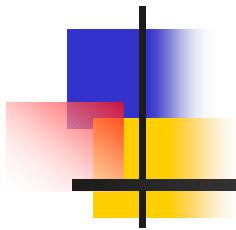
$$E_{sup} = E_{loss} + E_{cap}, \quad E_{loss} = E_{cap} (= 15CV_{dd}^2)$$



2. Parallel-type Charge Pump Circuit


2.1 Transient Analysis

- Node Voltage
- Energy Flow

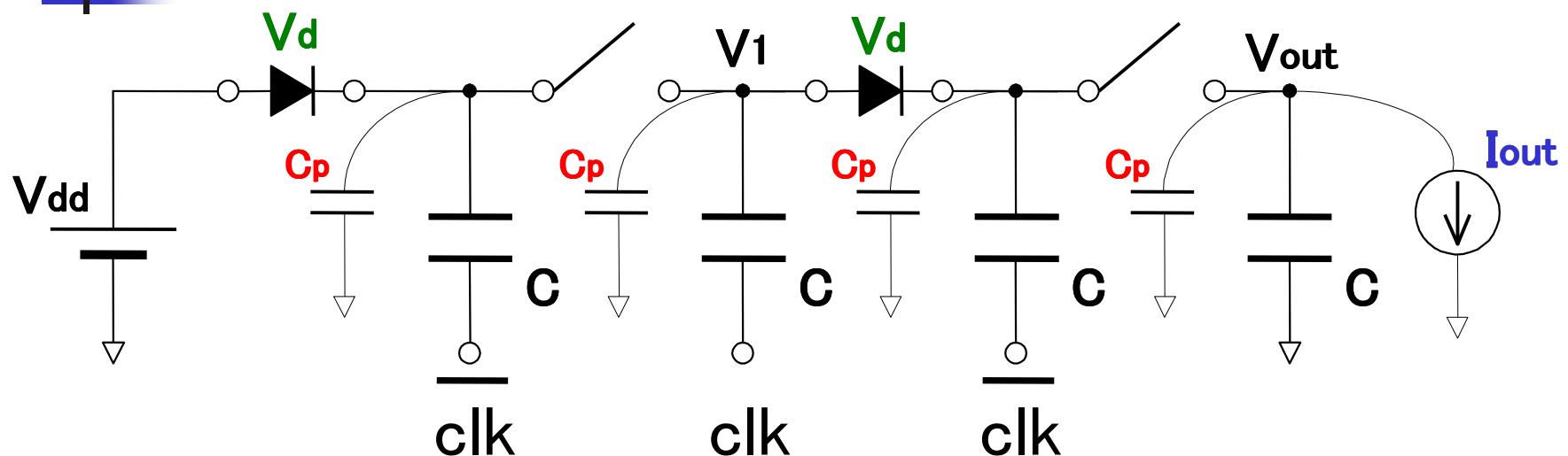2.2 Steady State Analysis

- Output Voltage
- Efficiency


Parallel-type Charge Pump Circuit with Non-idealities



V_d : Voltage drop across switch

C_p : Parasitic capacitance to ground

I_{out} : Output load current

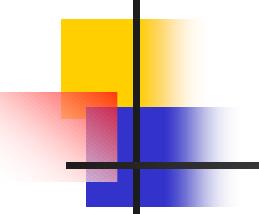

Parallel-type Charge Pump Node Voltage in Steady State

As $n \rightarrow \infty$


- Output voltage

$$V_{out}(n) \rightarrow \left[4 - \frac{3 C_p}{C + C_p} \right] V_{dd} - 4V_d - \frac{7 T I_{out}}{C + C_p}$$

- Internal node voltage


$$V_1(n) \rightarrow \left[2 - \frac{3 C_p}{2(C + C_p)} \right] V_{dd} - 2V_d - \frac{7 T I_{out}}{2(C + C_p)}$$

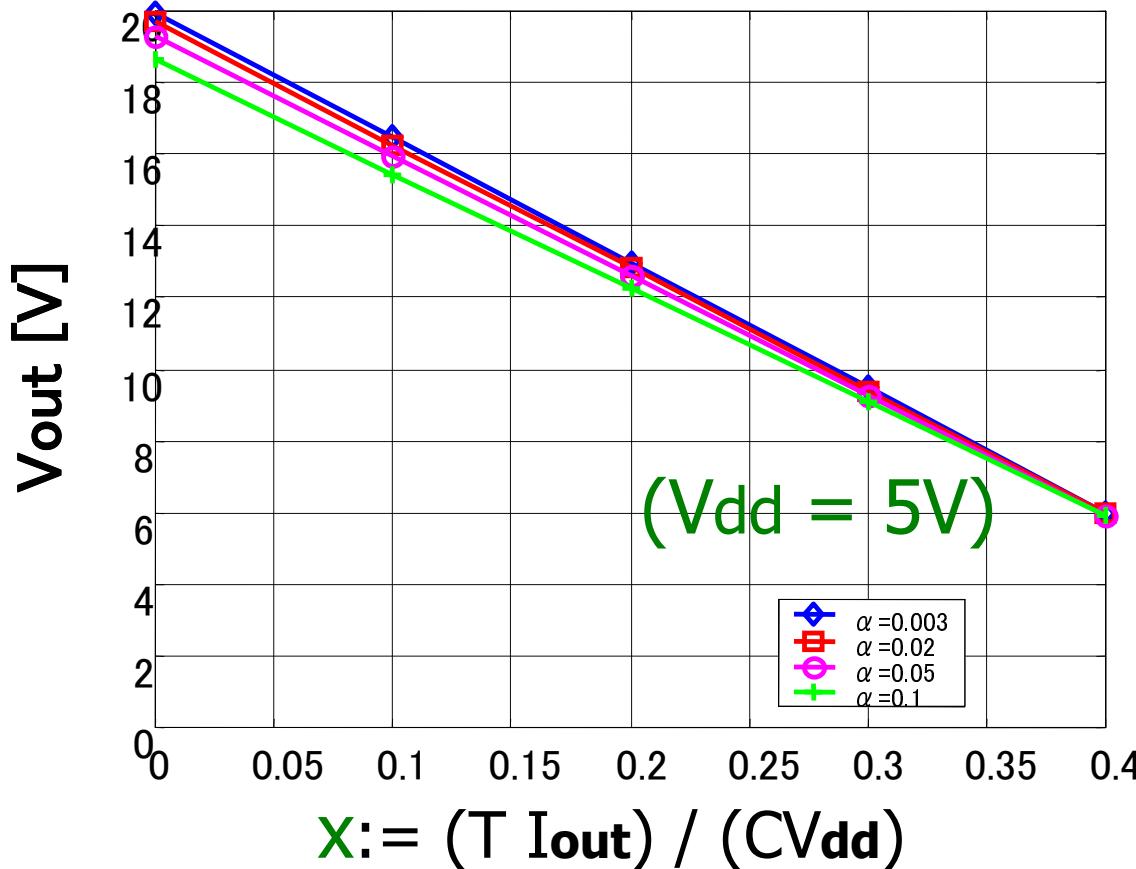Parallel-type Charge Pump Output Voltage from Formula



3-stage charge pump ($N=3$), $\beta := V_d/V_{dd} = 0.0$

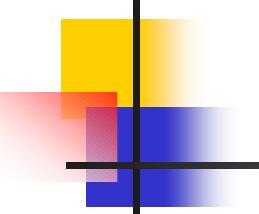$\alpha := C_p/C = 0.003, 0.02, 0.05, 0.1$



Parallel-type Charge Pump Efficiency η in Steady State

$$\eta := \frac{\text{Output power from } V_{\text{out}}}{\text{Supplied power from } V_{\text{dd}} \text{ and clock drivers}}$$

$$= 1 - \frac{N\alpha + 2(N+1)(1+\alpha)\beta x + 4Nx}{N\alpha + 2(N+1+\alpha)x}$$


Where

N : number of stages

$x := (T I_{\text{out}}) / (C V_{\text{dd}})$,

$\alpha := C_p/C$, $\beta := V_d/V_{\text{dd}}$.


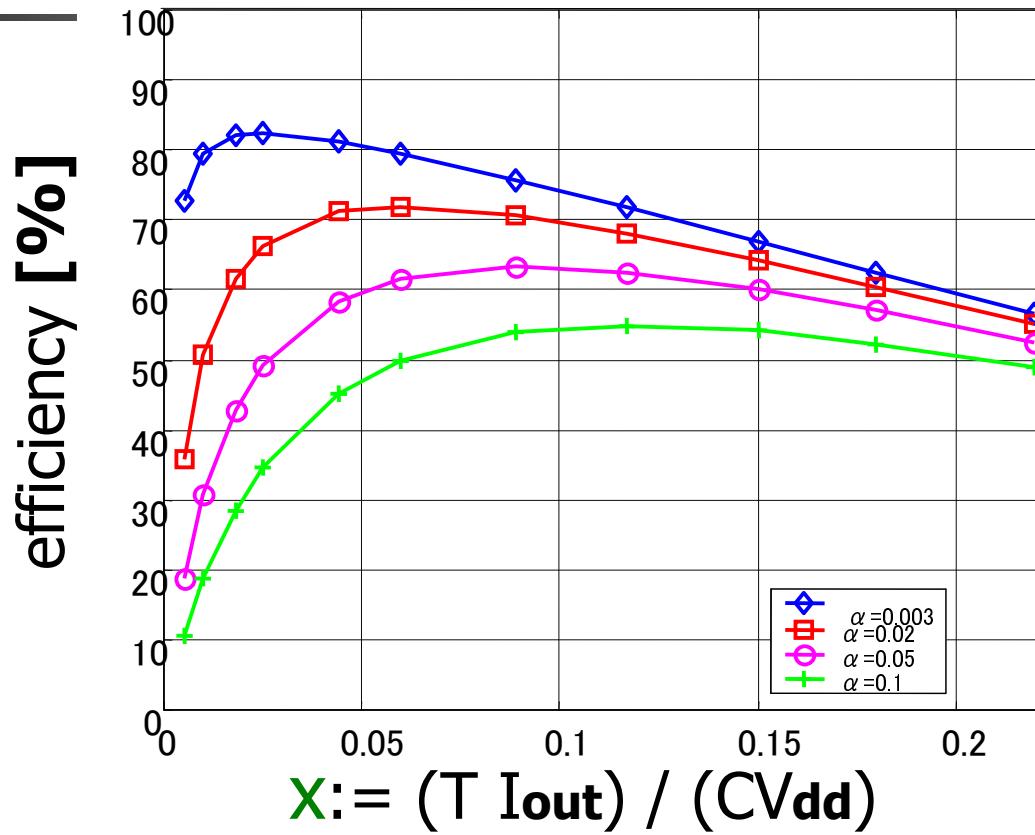
Parallel-type Charge Pump Efficiency from Formula




3-stage charge pump ($N=3$), $\beta := V_d/V_{dd} = 0.1$

$\alpha := C_p/C = 0.003, 0.02, 0.05, 0.1$

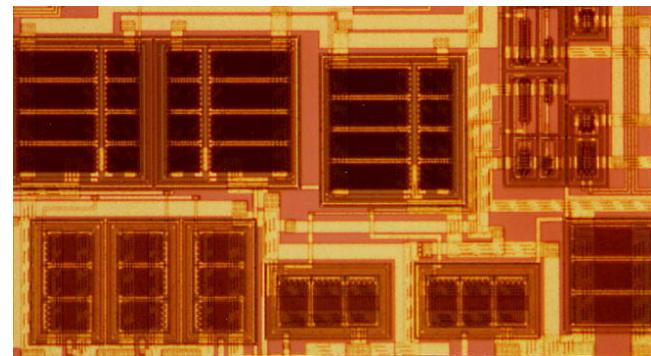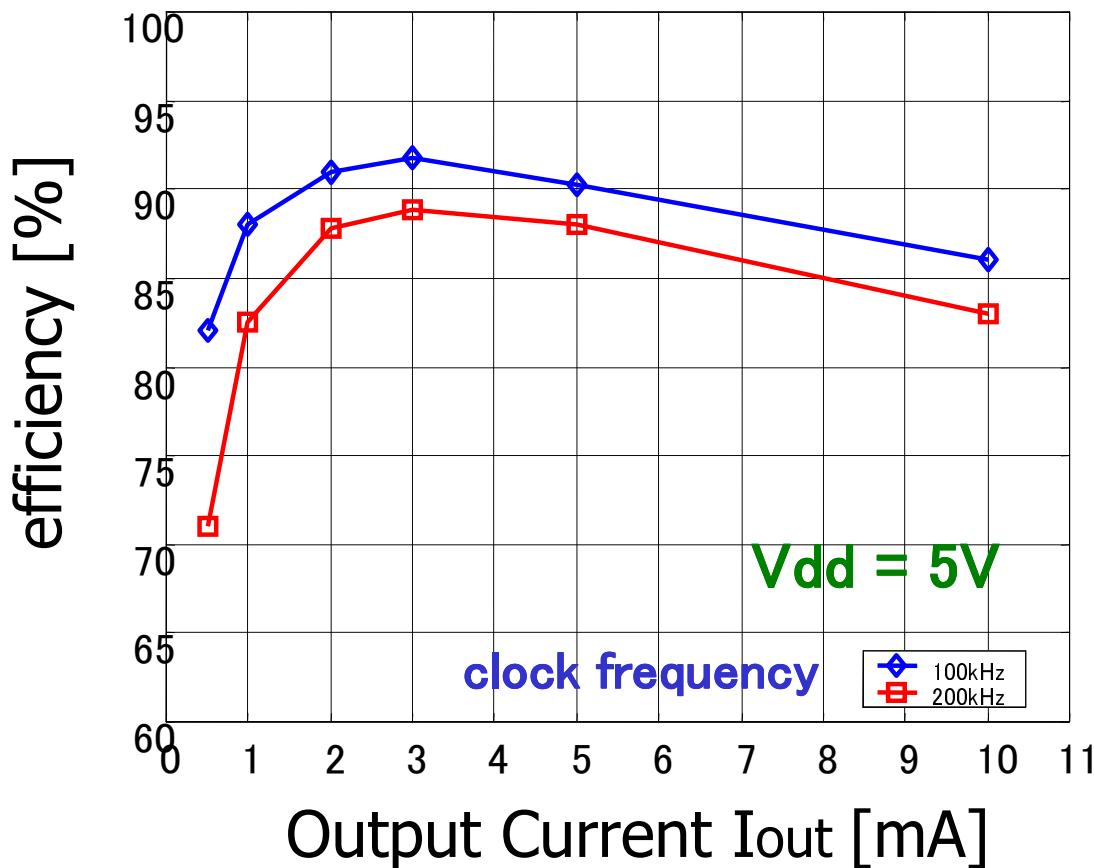Measured Parallel-type Charge Pump Efficiency



3-stage charge pump
TEG chip photo

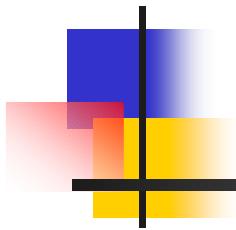


3. Serial-type Charge Pump Circuit

3.1 Steady State Analysis

- Output Voltage
- Efficiency

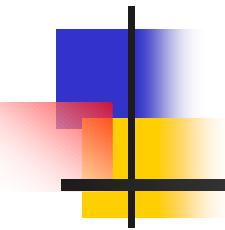3.2 Comparison of Parallel and Serial-type Charge Pump Circuits




3. Serial-type Charge Pump Circuit

3.1 Steady State Analysis

- Output Voltage
- Efficiency


3.2 Comparison of Parallel and Serial-type Charge Pump Circuits

Principle of Serial-type Charge Pump

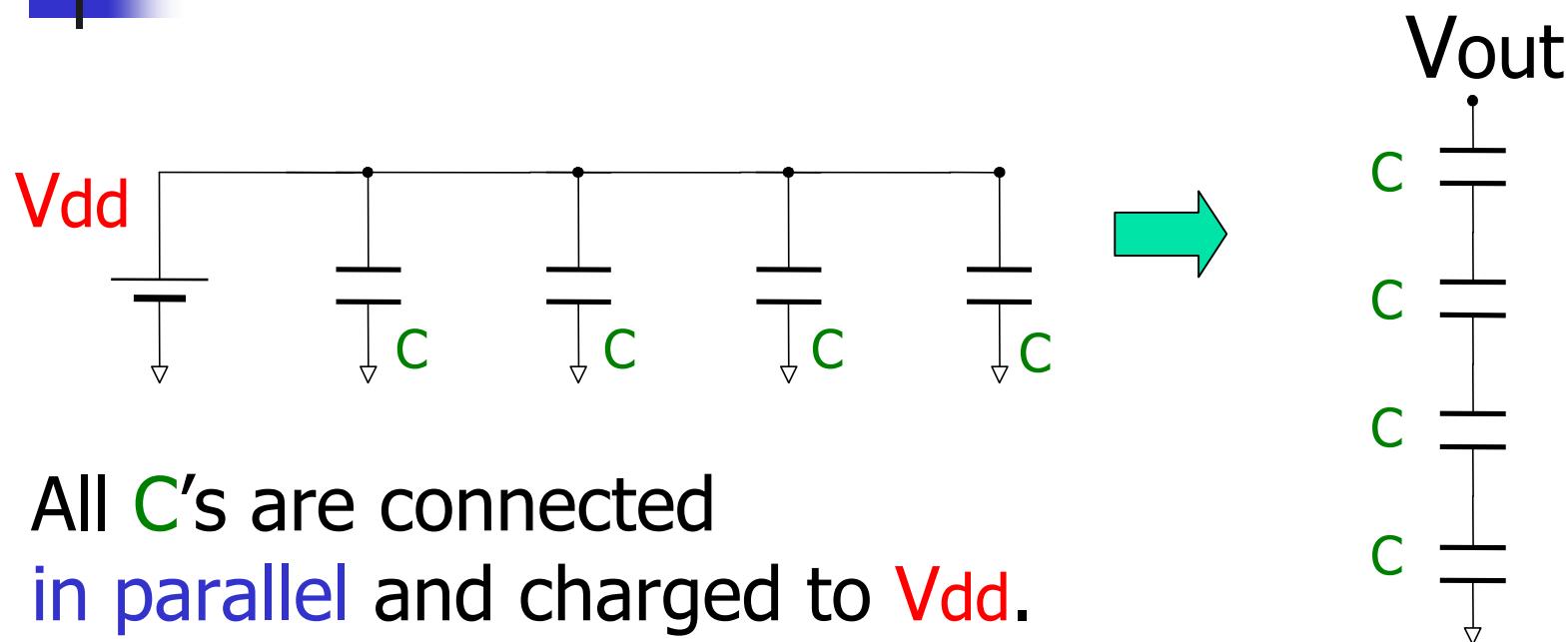


All C 's are connected in series to produce high output voltage.

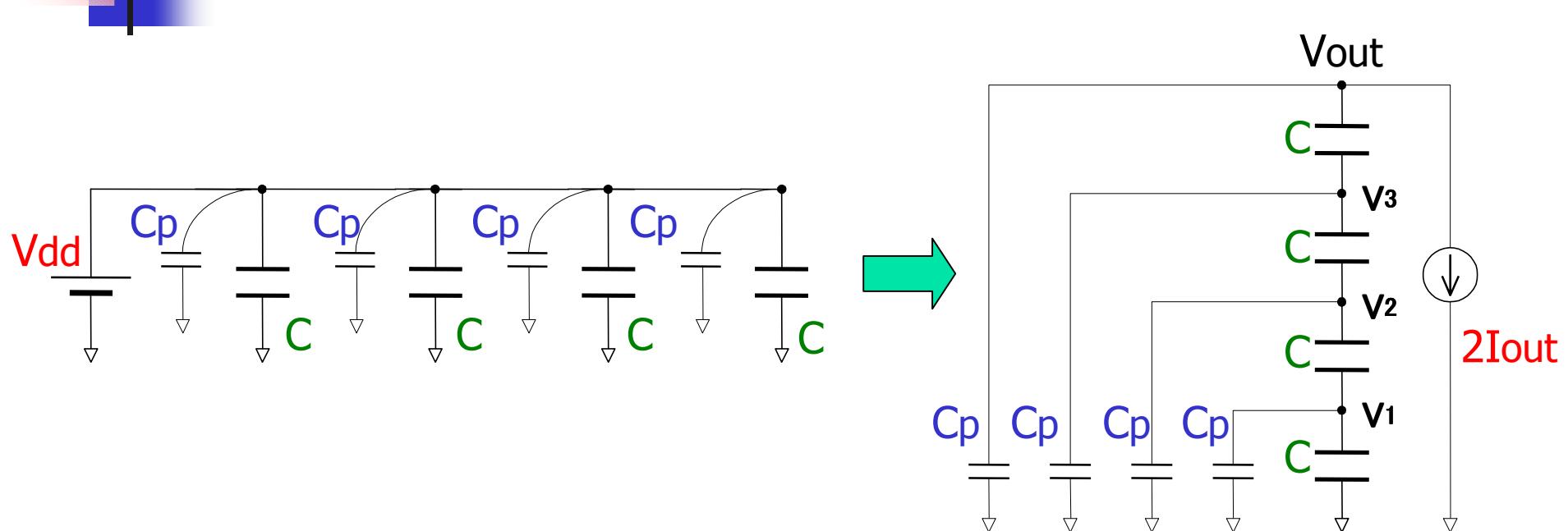Serial-type Charge Pump with Non-idealities



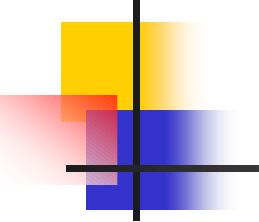- C_p : Parasitic capacitance to ground
- I_{out} : Output load current




Serial-type Charge Pump Output Voltage in Steady State

$$V_{out} = \frac{V_{dd}}{D} \left[(4 + 20\alpha + 21\alpha^2 + 8\alpha^3 + \alpha^4) - x(4 + 10\alpha + 6\alpha^2 + \alpha^3) \right]$$


Where

- $x := (T I_{out}) / (C V_{dd})$
- $\alpha := C_p / C$
- $D := 1 + 10\alpha + 15\alpha^2 + 7\alpha^3 + \alpha^4$

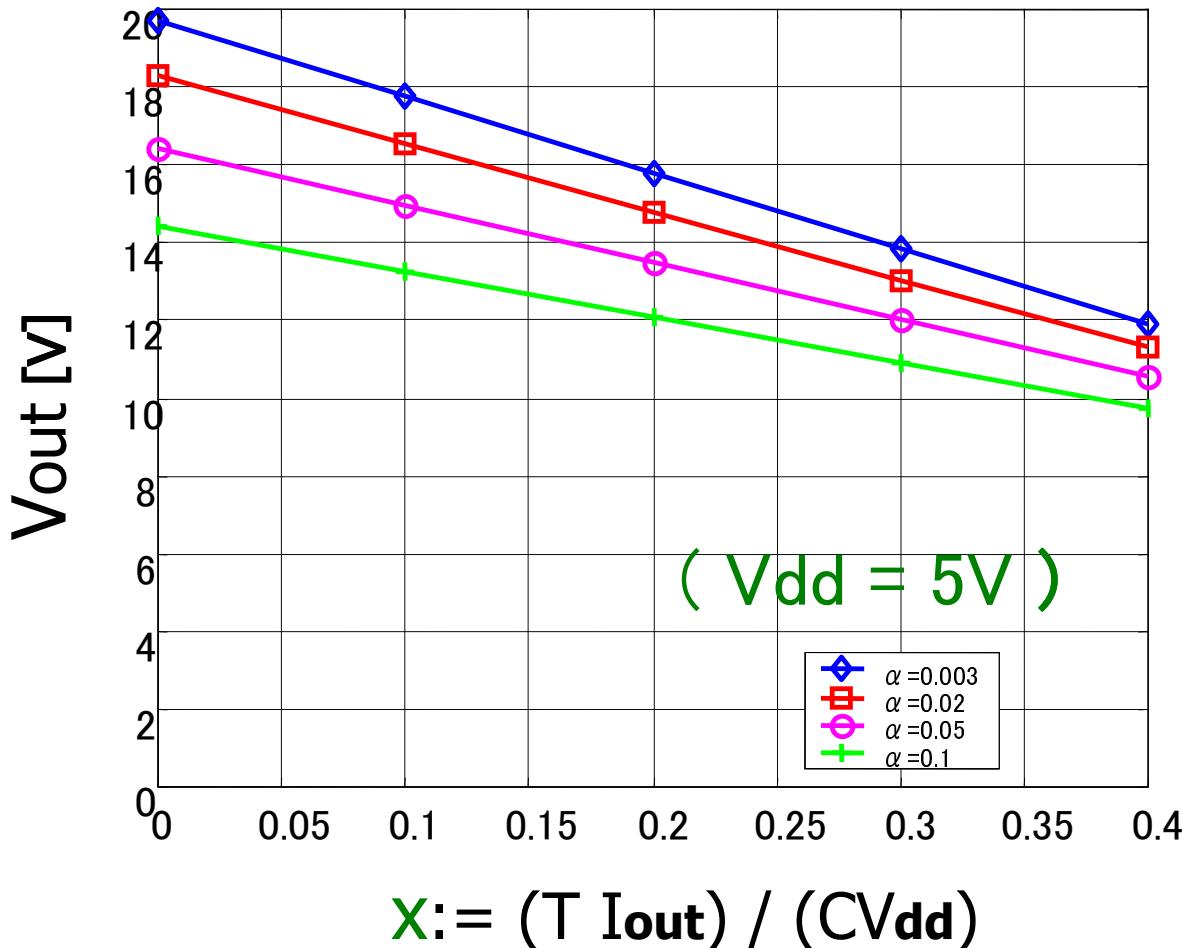Serial-type Charge Pump Output Voltage from Formula


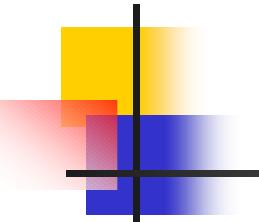
$$\alpha := C_p / C = 0.003, 0.02, 0.05, 0.1$$



Serial-type Charge Pump Efficiency η in Steady State

$$\eta = \frac{Fx - (Hx^2/2)}{G + 2Fx}$$

Where

$$x := (T I_{out}) / (C V_{dd})$$


$$F := 4 + 20\alpha + 21\alpha^2 + 8\alpha^3 + \alpha^4$$

$$G := 14\alpha + 34\alpha^2 + 19\alpha^3 + 3\alpha^4$$

$$H := 4 + 10\alpha + 6\alpha^2 + \alpha^3$$


$$\alpha := C_p/C$$

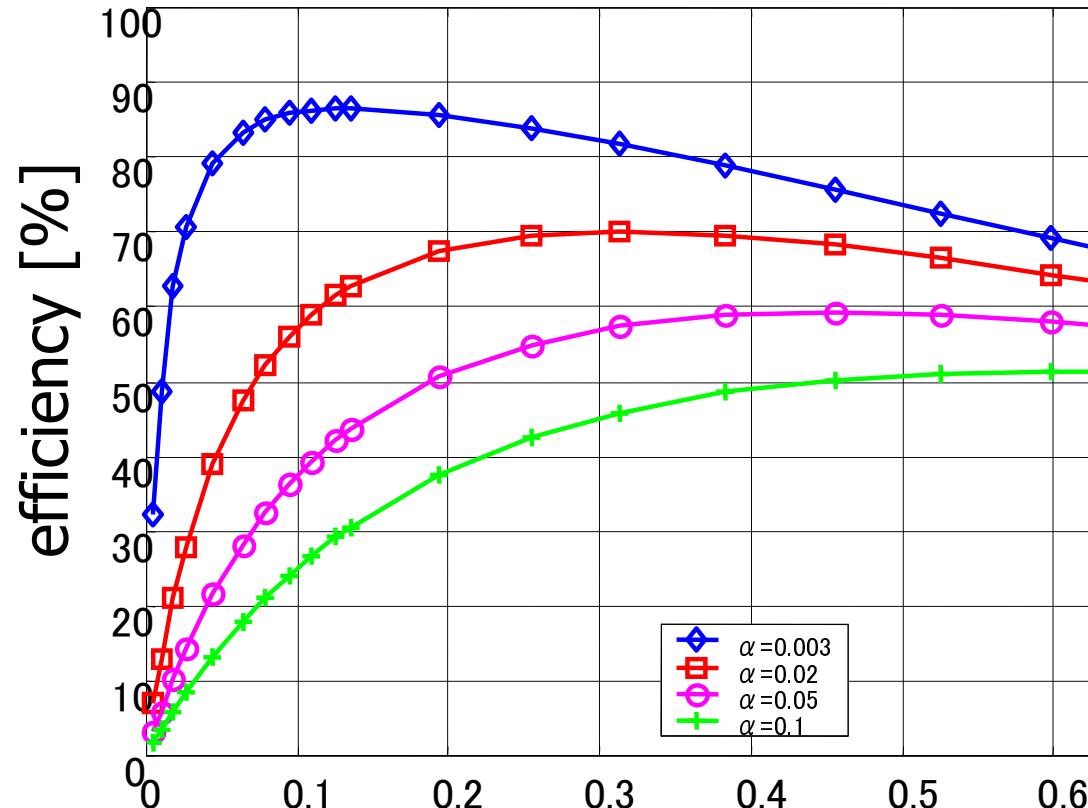Serial-type Charge Pump Efficiency from Formula



$$X := (T \ I_{out}) / (C V_{dd})$$

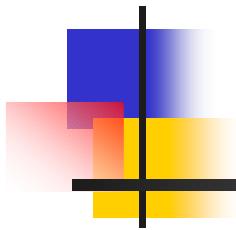$\alpha := Cp/C = 0.003, 0.02, 0.05, 0.1$



3. Serial-type Charge Pump Circuit

3.1 Steady State Analysis



- Output Voltage
- Efficiency

3.2 Comparison of Parallel and Serial-type Charge Pump Circuits

Output Voltage Comparison of Parallel- and Serial-types




Vdd=5V

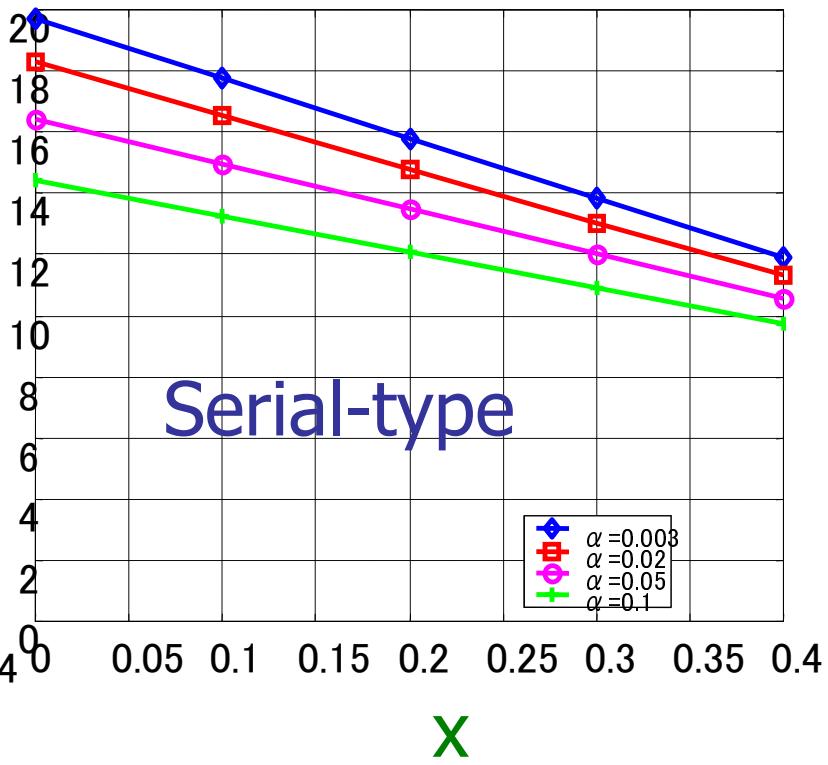
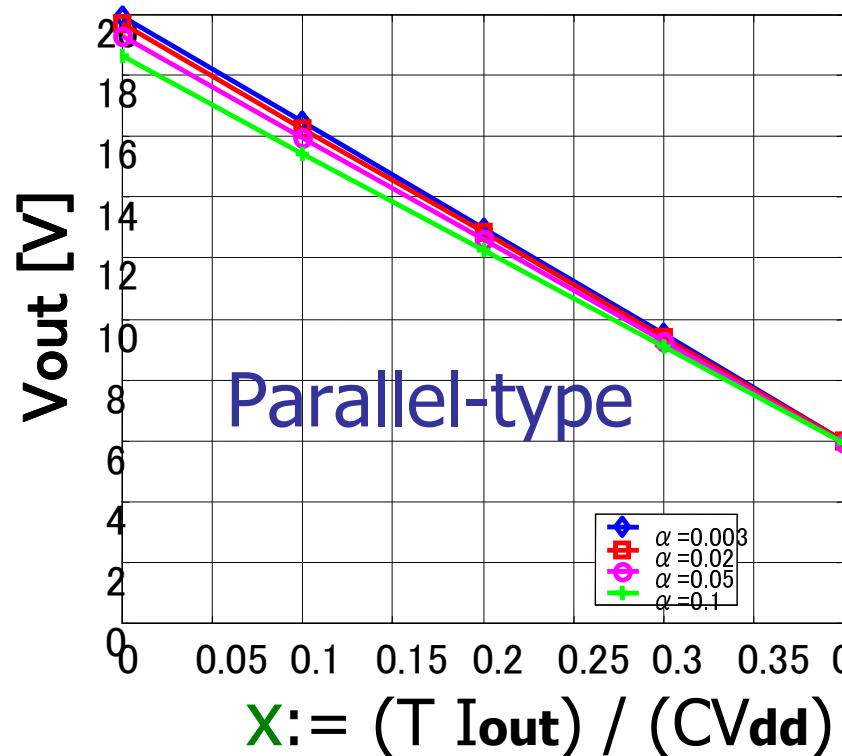


- For small x , the parallel-type is better.

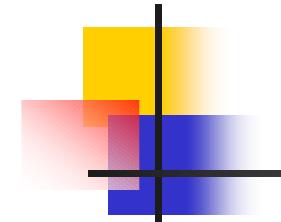
Efficiency Comparison of Parallel- and Serial-types



$$\beta = V_d / V_{dd} = 0$$

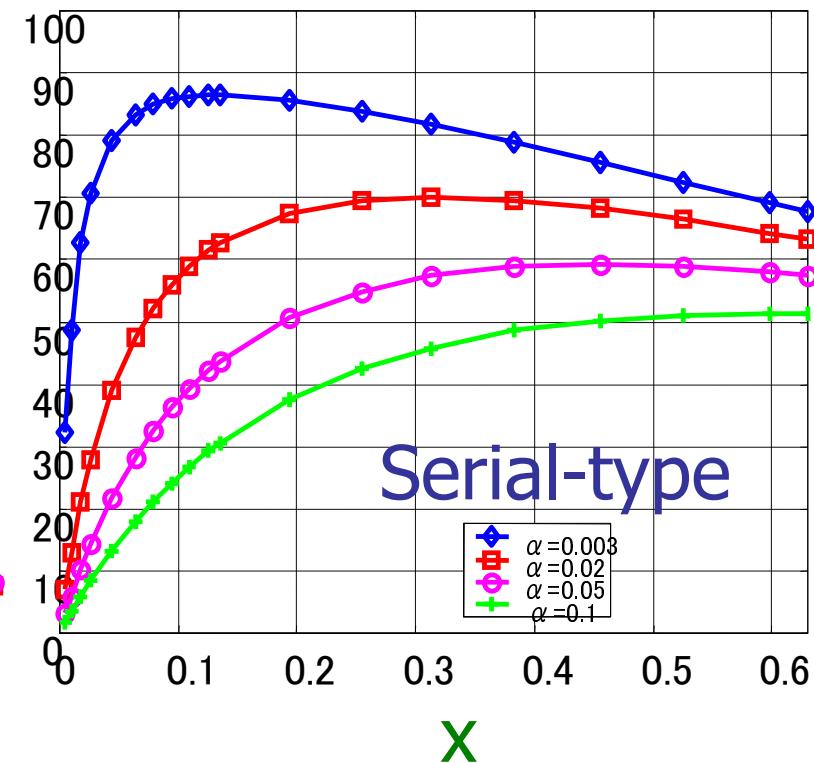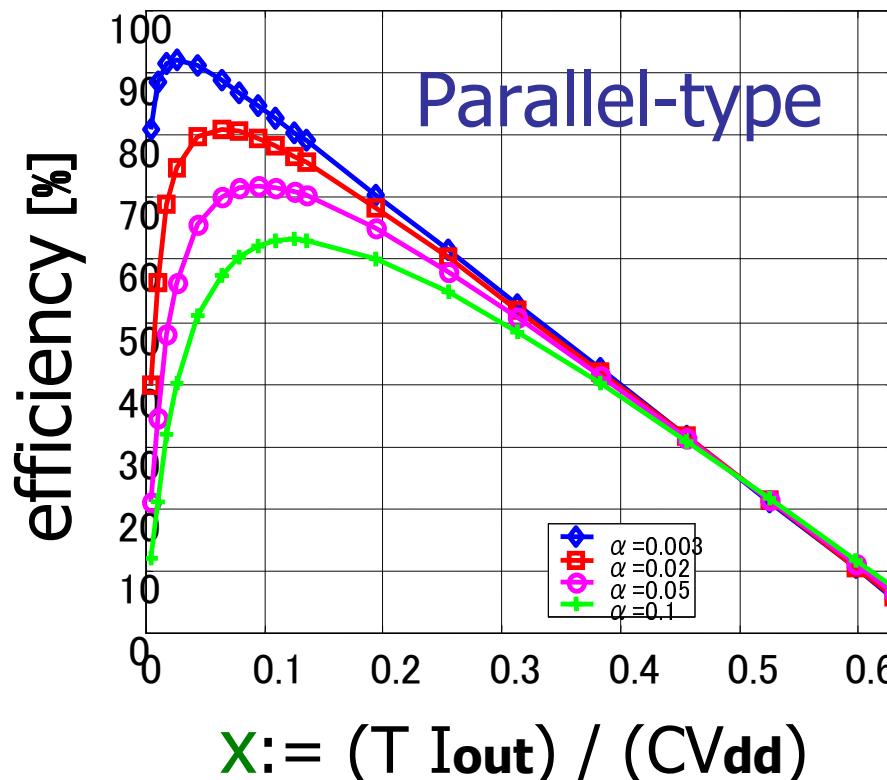

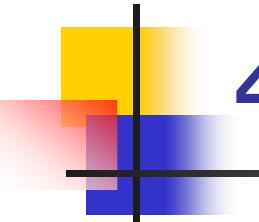- For small x , the parallel-type is better.



4. Summary

The followings are clarified:

- Parallel-type Charge Pump
 - In transient state,
Node voltage, Energy flow
 - In steady state
Output node voltage, Efficiency
- Serial-type Charge Pump
 - In steady state
Output node voltage, Efficiency