

Invited Paper

# Analog/Mixed-Signal Circuit Testing Technologies in IoT Era

Haruo Kobayashi

A. Kuwana, J. Wei, Y. Zhao, S. Katayama

T. M. Tri, M. Hirai, T. Nakatani, K. Hatayama

*Gunma University*

K. Sato, T. Ishida, T. Okamoto, T. Ichikawa

*Rohm Semiconductor*



# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion

# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- $\Delta\Sigma$  ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion

# Hot Applications in IC Industry

- Automotive application

ppm (parts per million) → ppb (parts per billion)

low quality → out of business



- IoT systems

A lot of sensors, interface analog circuits

High reliability, Low cost system



High quality, low cost testing of LSI is important !

# Test and Measurement are different

## LSI test and measurement

- Production Test :

Decision of “Go” or “No Go”


LSI testing → manufacturing engineering.



Today's focus

- Measurement / Characterization

 Accurate performance evaluation of circuit



# IC Testing Technologies

- **Analog/mixed-signal** portions continue to be difficult part of SoC test.
  - most troublesome parts
- LSI testing technology
  - reduces **cost** and improves **quality** simultaneously.
- Additional benefits of testing:
  - Improvement of
    - Yield
    - Reliability
    - Security
    - Diagnosis

# Contents

---

- Research Background
- **Analog/Mixed-Signal Circuit Testing**
- Operational Amplifier Testing
- $\Delta\Sigma$  ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion

# Management Strategy

- Strategy 1 :

Use low cost ATE and develop analog BIST/BOST to make testing cost lower.

- Strategy 2 :

Use high-end mixed-signal ATE as well as its associated services & know how. Fast time-to-market & no BIST can make profits much more than testing cost.

Save or Earn

ATE: Automatic Test Equipment

BIST: Built-In Self-Test, BOST: Built-Out Self-Test



# Low Cost Testing

- Low cost ATE


A penny saved is a penny earned.

## Digital ATE

- No analog option such as Arbitrary Waveform Generator: AWG
- Input/output are mainly digital.

- Short testing time
- Multi-site testing
- Minimum or no chip area penalty for BIST
- Extensive usage of BOST


# Sine Wave Generation with Digital ATE

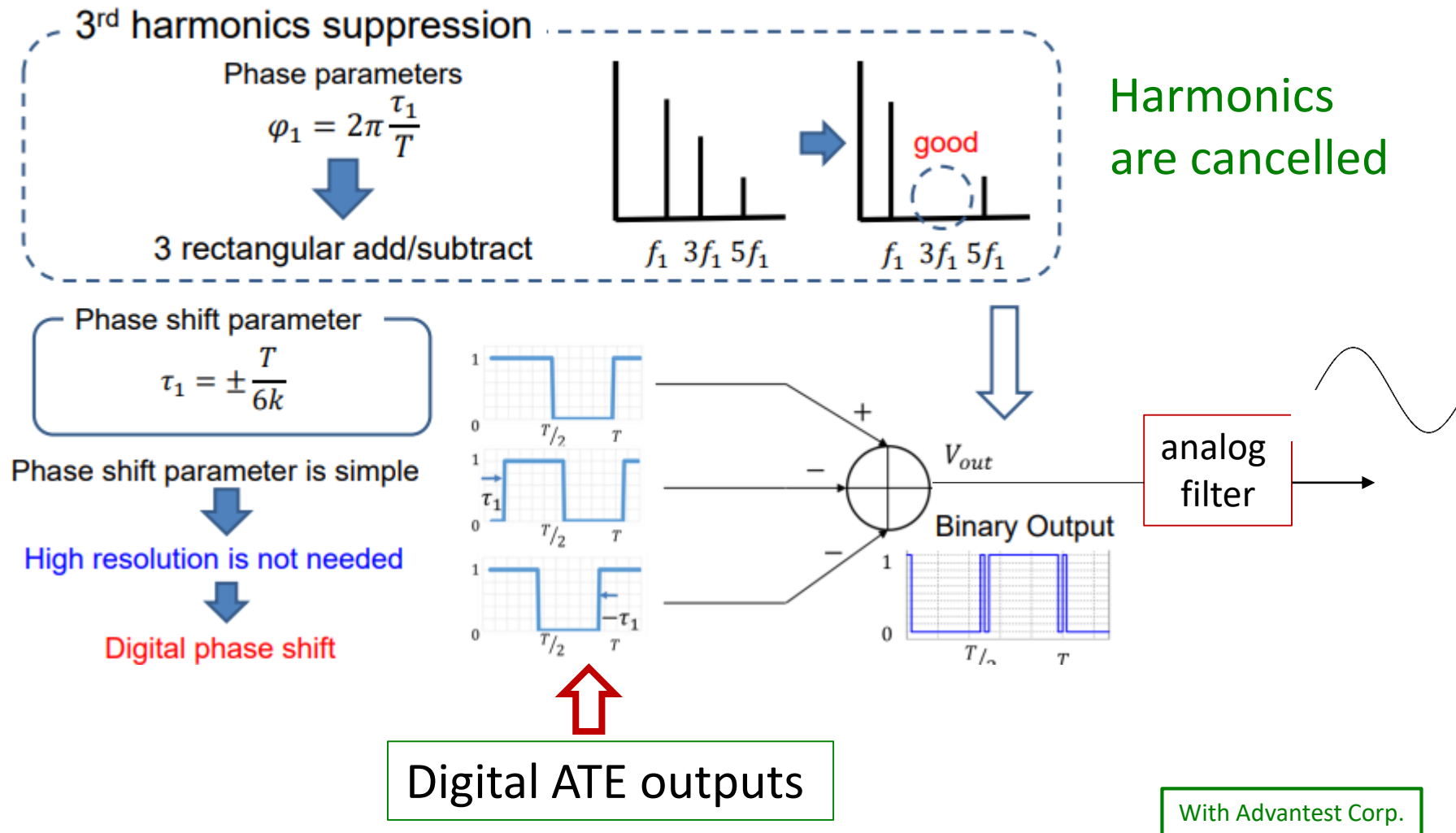

- [1] M. Kawabata, K. Asami, S. Shibuya, T. Yanagida, H. Kobayashi, "Low-Distortion Signal Generation for Analog/Mixed-Signal Circuit Testing Using **Digital ATE**", The First International Test Conference in Asia, Taipei, Taiwan (Sept. 2017)

# Hot Topics in Analog/Mixed-Signal Circuit Testing

- Analog fault model
- Analog fault simulation
- Analog test coverage
- Defect-based analog test

 

Analog IC



Very difficult,  
but automotive industry strongly demands



# Analog BIST

- BIST for digital : Successful  
BIST for analog : Not very successful  
➡ Challenging research
- Digital test : Functionality ➡ Easy  
Analog test : Functionality & Quality ➡ Hard


Analog: parametric fault as well as fatal fault.

Prof. A. Chatterjee

Specification-based Test ↔ Alternative Test ↔ Defect-based Test

- In many cases
  - Analog BIST depends on circuit.
  - No general method like scan path in digital.
  - One BIST, for one parameter testing

# Cooperation of Analog BIST and ATE

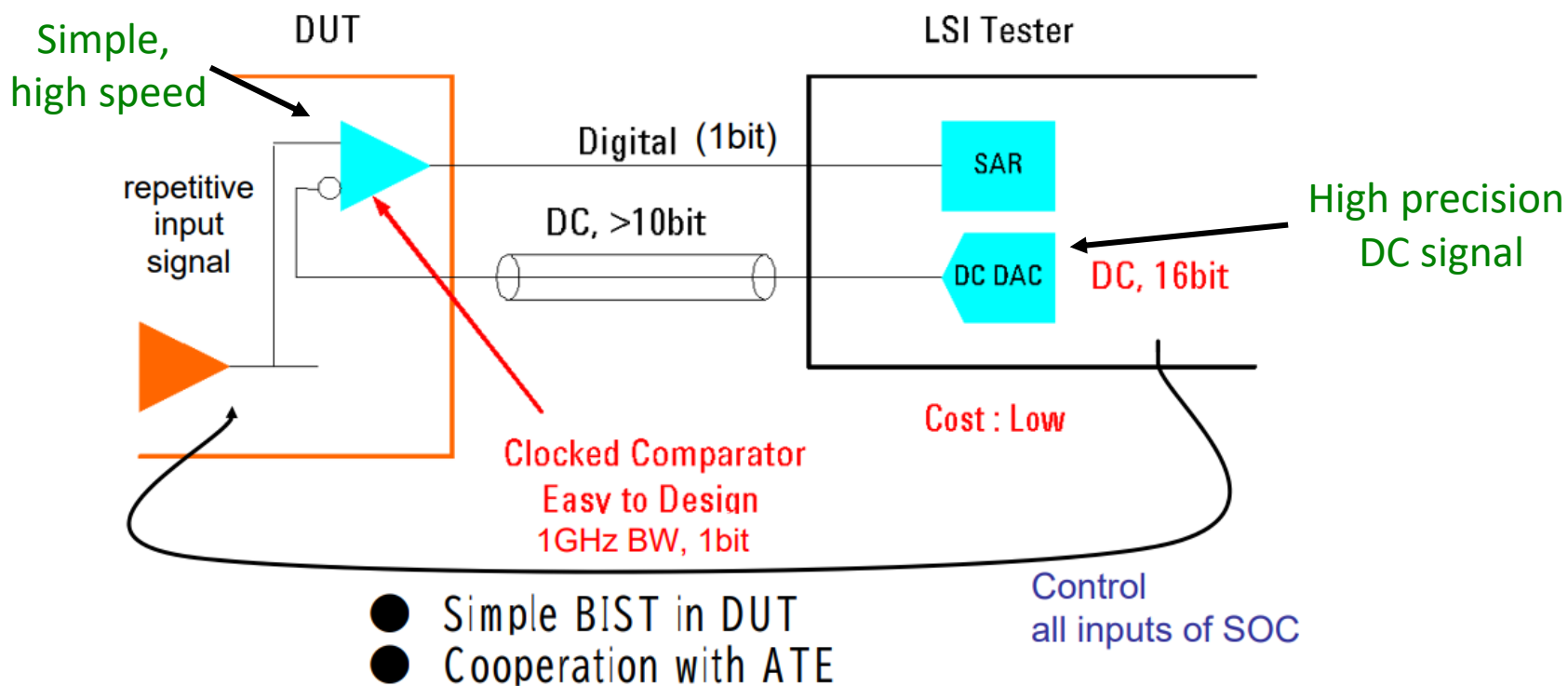

Output signals from SoC can be repetitive by controlling all inputs to SOC with ATE

→ No need for T/H circuit in front of SAR ADC


→ Wideband signal testing is possible

[2] T. Komuro, N. Hayasaka, H. Kobayashi, H. Sakayori,  
“A Practical BIST Circuit for Analog Portion in Deep Sub-Micron CMOS System LSI”,  
International Symposium on Circuits and Systems (ISCAS) (May.2005).
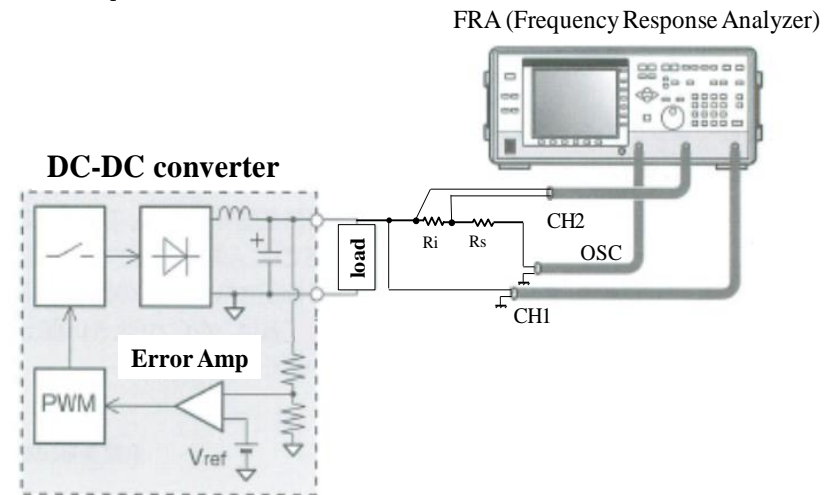
# RF / High-Speed IO / Power Circuit Testing

- RF / HSIO / Power circuit testing is different from each other as well as analog testing technology.
- These are also challenging areas.
- Power supply circuit test example:

- Power supply circuit stability test without breaking the loop




[3] N. Tsukiji, Y. Kobori, H. Kobayashi,

"A Study on Loop Gain Measurement Method Using Output Impedance in DC-DC Buck Converter ", IEICE Trans. Communications, (Sep. 2018).
 
# Robust Design and Testing

Robust design makes its testing difficult.

- Feedback suppresses parameter variation effects.
- **Self-calibration** and redundancy hide defects in DUT.
- **Secure** IC is difficult to test.




Trojan

[4] T. Yagi, H. Kobayashi, Y. Tan, S. Ito, S. Uemori, N. Takai, T. J. Yamaguchi, “Production Test Consideration for Mixed-Signal IC with **Background Calibration**”, IEEJ Trans. Electrical and Electronic Engineering (Nov. 2010).

# Redundancy SAR ADC Design Example

Reliable circuit ↔ Test difficulty

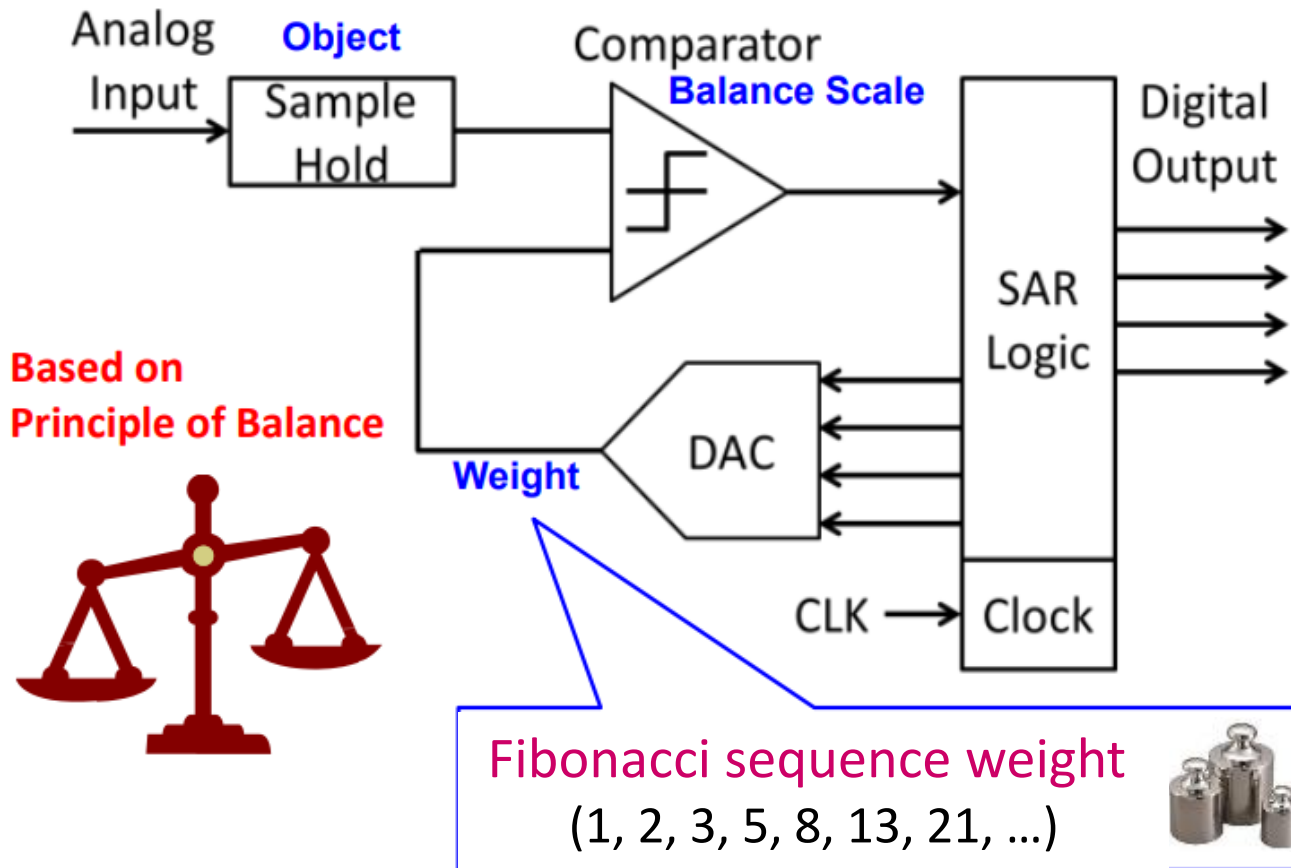

[5] Y. Kobayashi, H. Kobayashi, et. al.,

“Redundant SAR ADC Algorithms for Reliability Based on Number Theory”,

First IEEE International Workshop on Automotive Reliability & Test- ART Workshop (Nov. 2016)

[6] T. Ogawa, H. Kobayashi, “SAR ADC That is Configurable to Optimize Yield,”


IEEE Asia Pacific Conference on Circuits and Systems, Kuala Lumpur, Malaysia (Dec. 2010).


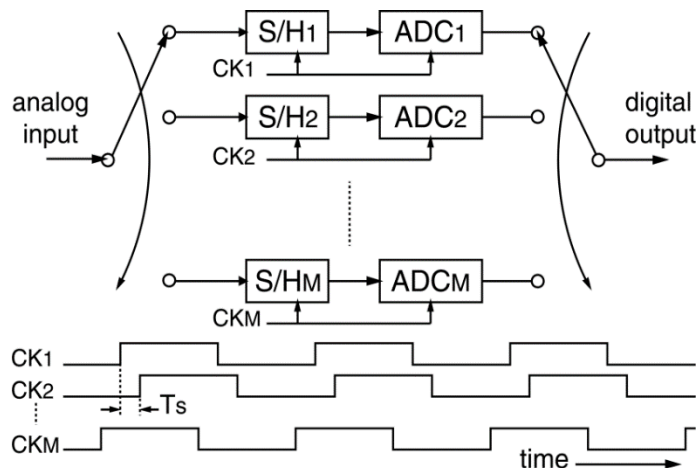
# ATE for Mixed-Signal IC Testing

- Analog part of ATE is costly for development.
- Analog BIST is also beneficial for mixed-signal ATE manufacturer
- ATE must be designed with today's technology for tomorrow's **higher performance** chip testing.

**Interleaved ADC** used in ATE to realize very high sampling rate with today's ADCs



[7] R. Yi, M. Wu, K. Asami, H. Kobayashi, et. al.,  
“Digital Compensation for Timing Mismatches in **Interleaved ADCs**”,  
IEEE 22nd Asian Test Symposium, Yilan, Taiwan, (Nov. 2013)

# Contents

---


- Research Background
- Analog/Mixed-Signal Circuit Testing
- **Operational Amplifier Testing**
- ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion

# IoT System and OP amp

- OP amp with smaller than  $\mu\text{V}$ -order offset is a key component of IoT system




Its guarantee at production test

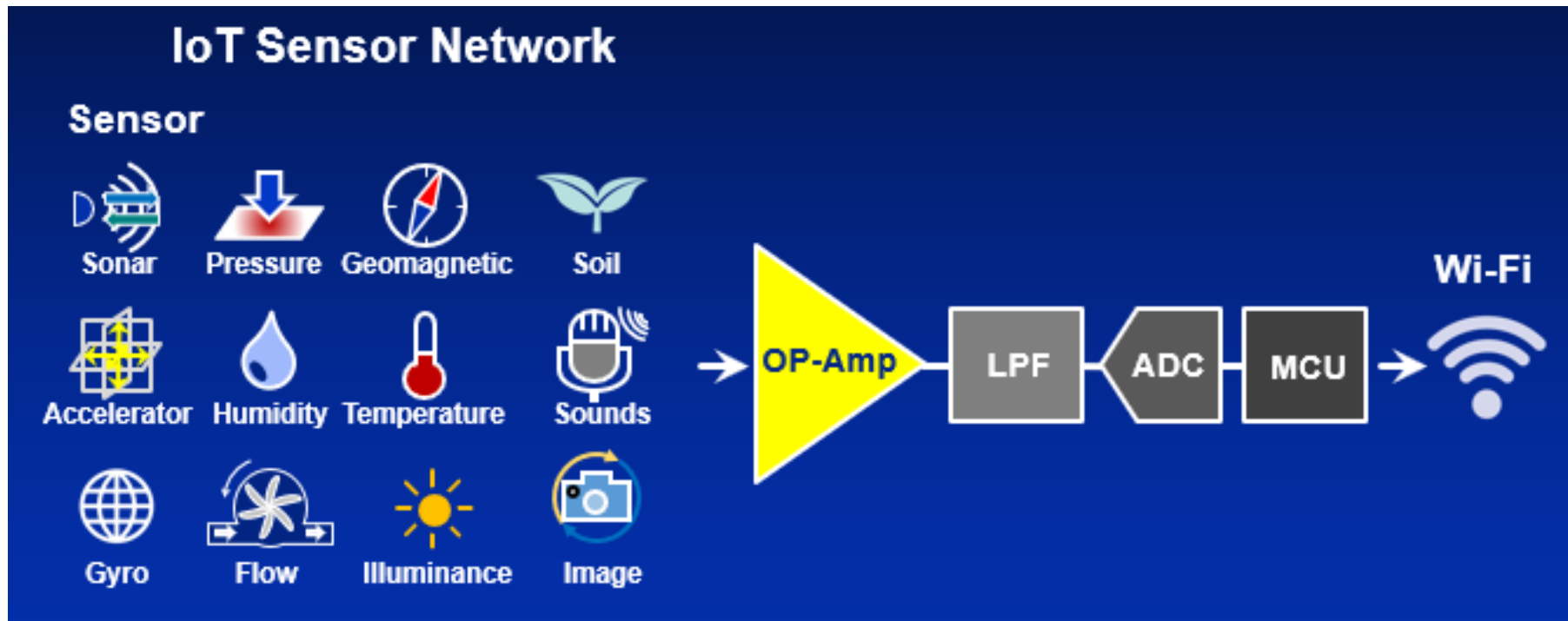

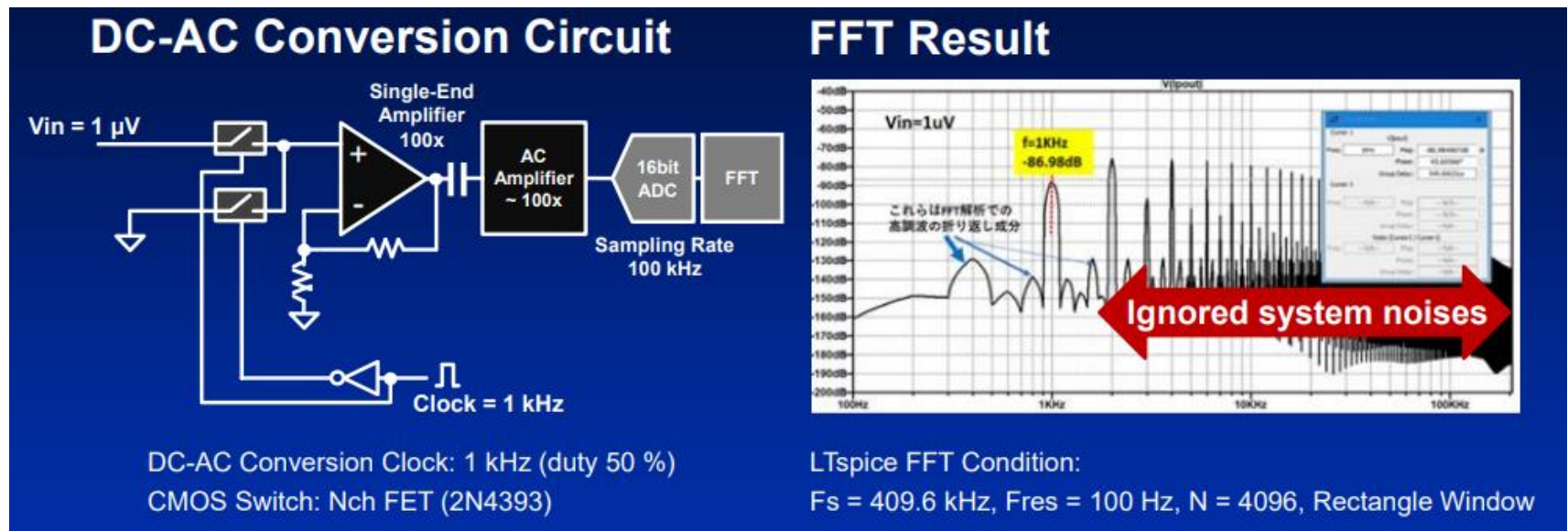
# $\mu\text{V}$ -order Voltage Measurement

- $\mu\text{V}$ -order OP amp offset voltage testing in short time at low cost.
- DC-AC conversion
  - ➔ No influence by DC noise, drift, thermal effects
- Applicable to multi-site testing



[8] Y. Sasaki, T. Nakatani, H. Kobayashi, et. al., "Accurate and Fast Testing Technique of Operational Amplifier DC Offset Voltage in  $\mu\text{V}$ -order by DC-AC Conversion", 3rd International Test Conference in Asia (Sept. 2019).

# OP amp test with Null Method

 

Low-cost , high-quality testing of operation amplifier

Goal

Null Method → Apply for mass production testing

Null Method

Measurement time : Long




Mass production testing : **Difficult**



1 second test time for  
1 US dollar chip

Good capacitor value selection → **Fast, stable operation**

# Null Method Circuit

 

## Switches (S1,..., S6)

- Offset
- Bias Current
- DC gain
- AC gain
- DC CMRR
- DC PSRR
- AC CMRR
- AC PSRR etc.

can be measured accurately

Operational Amplifier Measurement Circuit using the Null Method

Source : Analog Dialogue Vol 45 Apr.2011 Analog Devices

Accurate but slow !

# Experiment & Simulation Verification

- Optimization of phase compensation constants

$$C_1=1\text{nF}, C_2=0.1\mu\text{F}$$




Null Circuit → Fast and Stable

- Null Circuit : Change of signal application point depending on the measurement item
- Switching  $C_1$  and  $C_2$  depending on the measurement item



Settling time reduction →  $\cong 1/10$

Null method → Production testing

 

Our prototype

# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- **ADC Linearity Testing**
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion



# ADC Testing (DC Linearity)

- DC linearity test is the most important in many cases of ADC under test.
  - Precise ramp generation is challenging.
  - High resolution ADC → long testing time
- DC testing time is proportional to  $\frac{\text{number of codes}}{\text{sampling frequency}}$ 
  - large
  - slow

# ADC Testing (AC Performance)

- ADC AC performance testing
  - Sampling clock jitter
  - High frequency input signal
- We have to build low clock jitter system and apply high frequency input signal.  
**No alternative method so far.**

# ΔΣADC INL Test

Target

Product :24bit 6.8sps Delta-Sigma ADC

Test Item :INL


Final Product



INL: Integral Non-Linearity

Problems of direct method


## All Code Testing

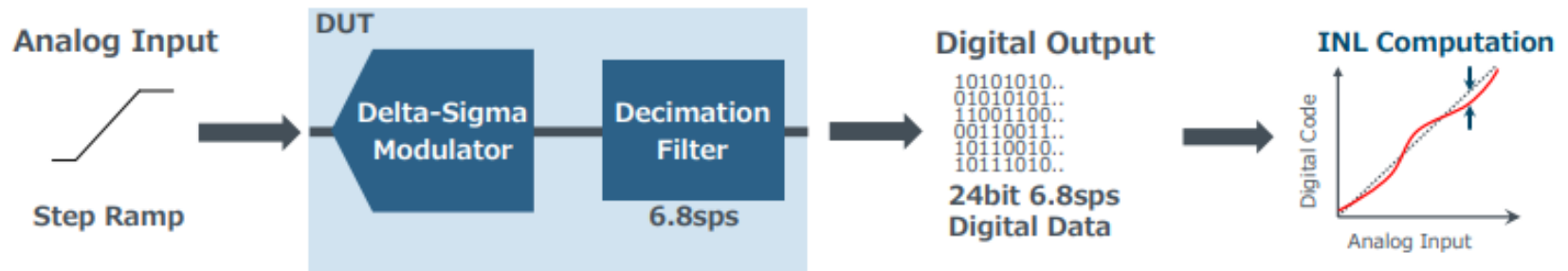

$$TestTime = 2^{24} * \frac{1}{6.8} * n = 685[h] * n \quad n = \frac{Samples}{Code}$$

Test Time will be 685[h]. Is it acceptable?
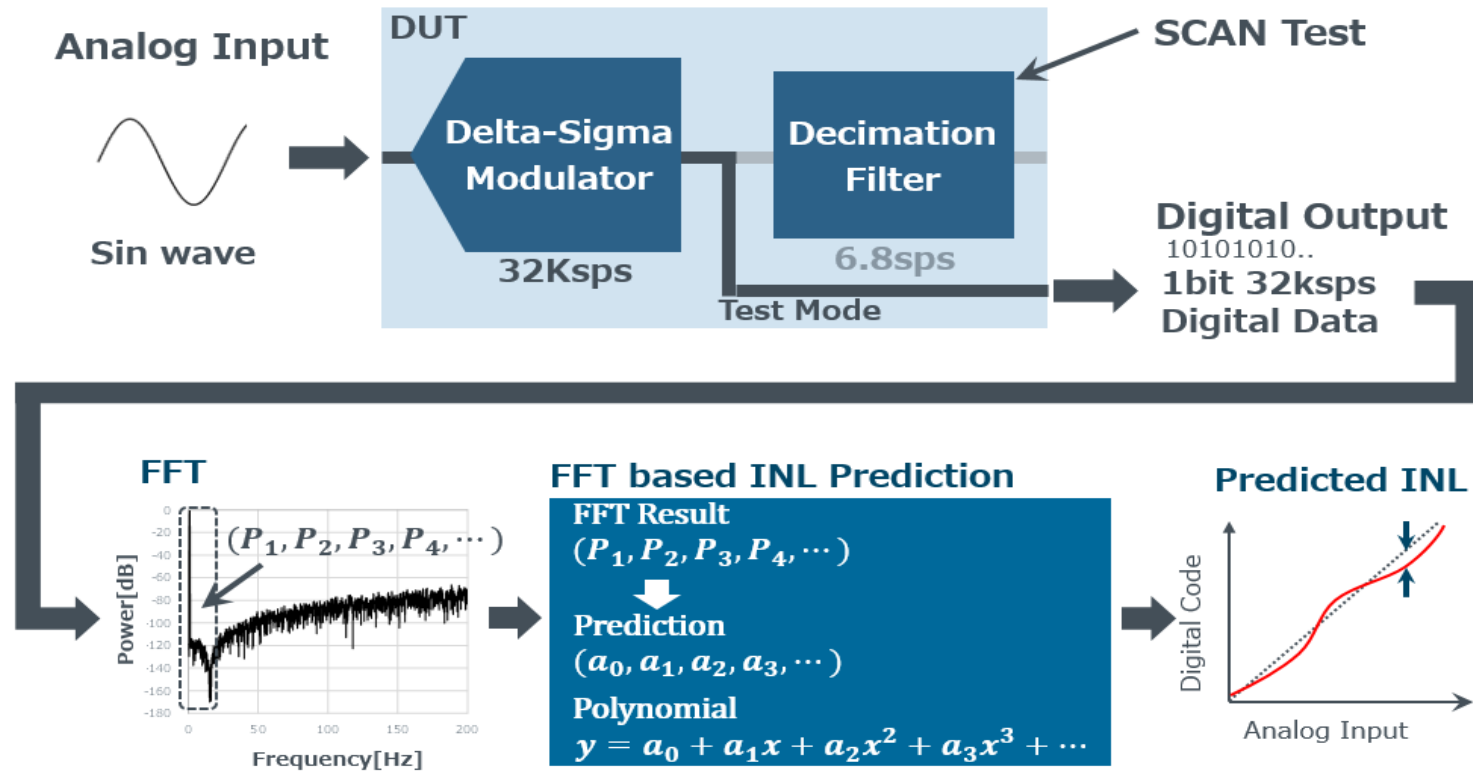
# Proposed $\Delta\Sigma$ ADC INL Test Method



## Test Time Estimation

Conventional  $TestTime = 685[h]$

Proposed  $TestTime = 34[sec](2^{20}point)$

# DFT for SAR ADC Linearity



A high-resolution, low-sampling rate ADC requires a long test time for its linearity.

Shorten SAR ADC linearity test time.

For a 12-bit SAR ADC, its linearity test time  
→ 1/4


DFT: Design for Testability

 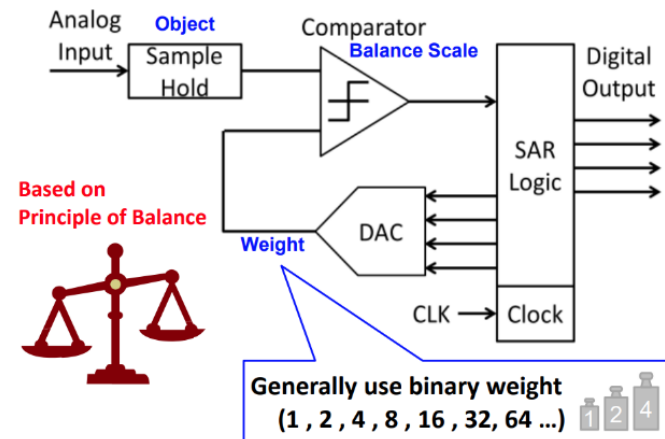[11] T. Ogawa, H. Kobayashi, et. al., "Design for Testability That Reduces Linearity Testing Time of SAR ADCs", IEICE Trans. Electronics (June 2011).





Our SAR ADC  
TSMC 180nm  
1.2mmx1.2mm

# Analog Signal Generation for ADC Histogram Test

- In mixed-signal SoCs, ...
  - Accurate ADC linearity evaluation
  - “around **the middle of its input range**” is required
  - Single sine wave is unsuitable 

 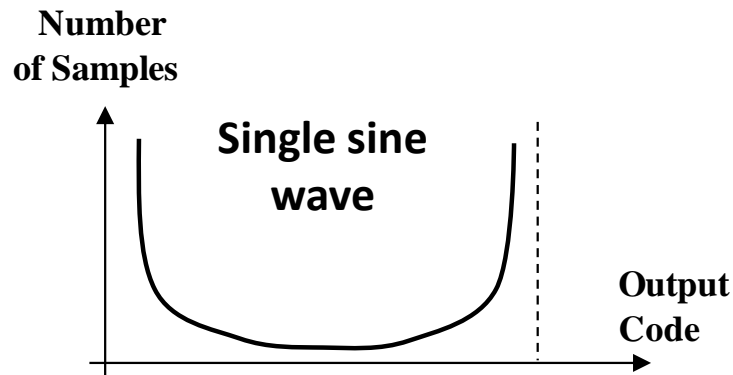**This Work**

- **Middle range** of histogram increases 



# ADC Histogram Test with Multi-tone



Proposed

$$V_n = \frac{\cos((2n-1)\omega t)}{(2n-1)^2} \quad n=1,2,\dots$$

$$V_{in} = \frac{4}{\pi} (V_1 + 2.6 \cdot V_2 + 1.8 \cdot V_3 + 1.4 \cdot V_6 + 1.2 \cdot V_7)$$




Linearity test time reduction

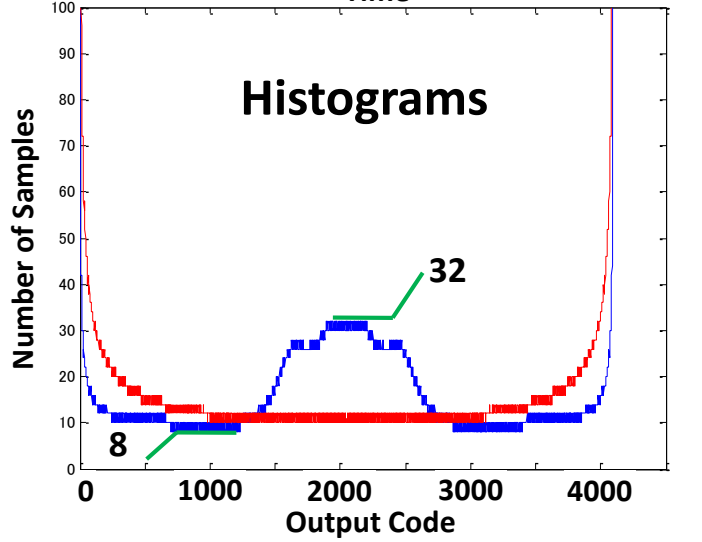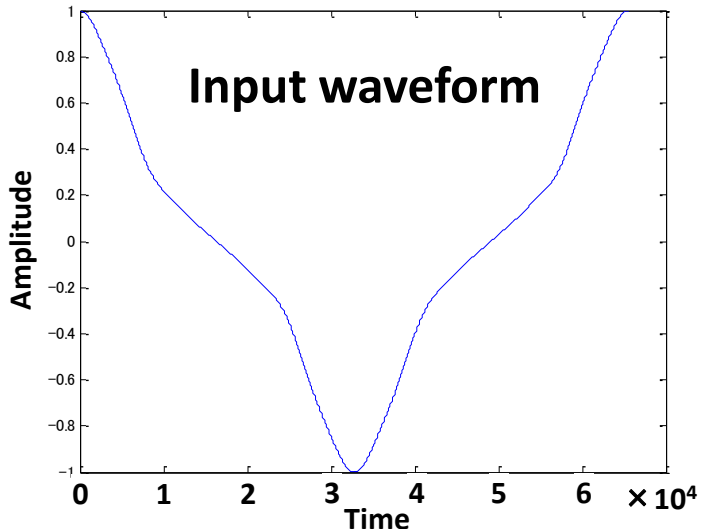

[12] S. Uemori, H. Kobayashi, et. al., "ADC Linearity Test Signal Generation Algorithm", IEEE Asia Pacific Conference on Circuits and Systems, Kuala Lumpur, Malaysia (Dec. 2010)

# Architecture for Generating Proposed Test Signal

AWG: Arbitrary Waveform Generator

 

- DSP program : Multi-tone sine wave
- Analog filter : Harmonics removal

**As a result ...**



- Histogram for the middle of ADC input range can be high.

ADC linearity test time → 1/2




# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- $\Delta\Sigma$  ADC Linearity Testing
- **Analog Signal Generation with AWG**
- Waveform Sampling Technique
- Timing Testing
- Challenges and Conclusion

# Signal Generation for Analog Circuit Test

## Problem with Conventional Method


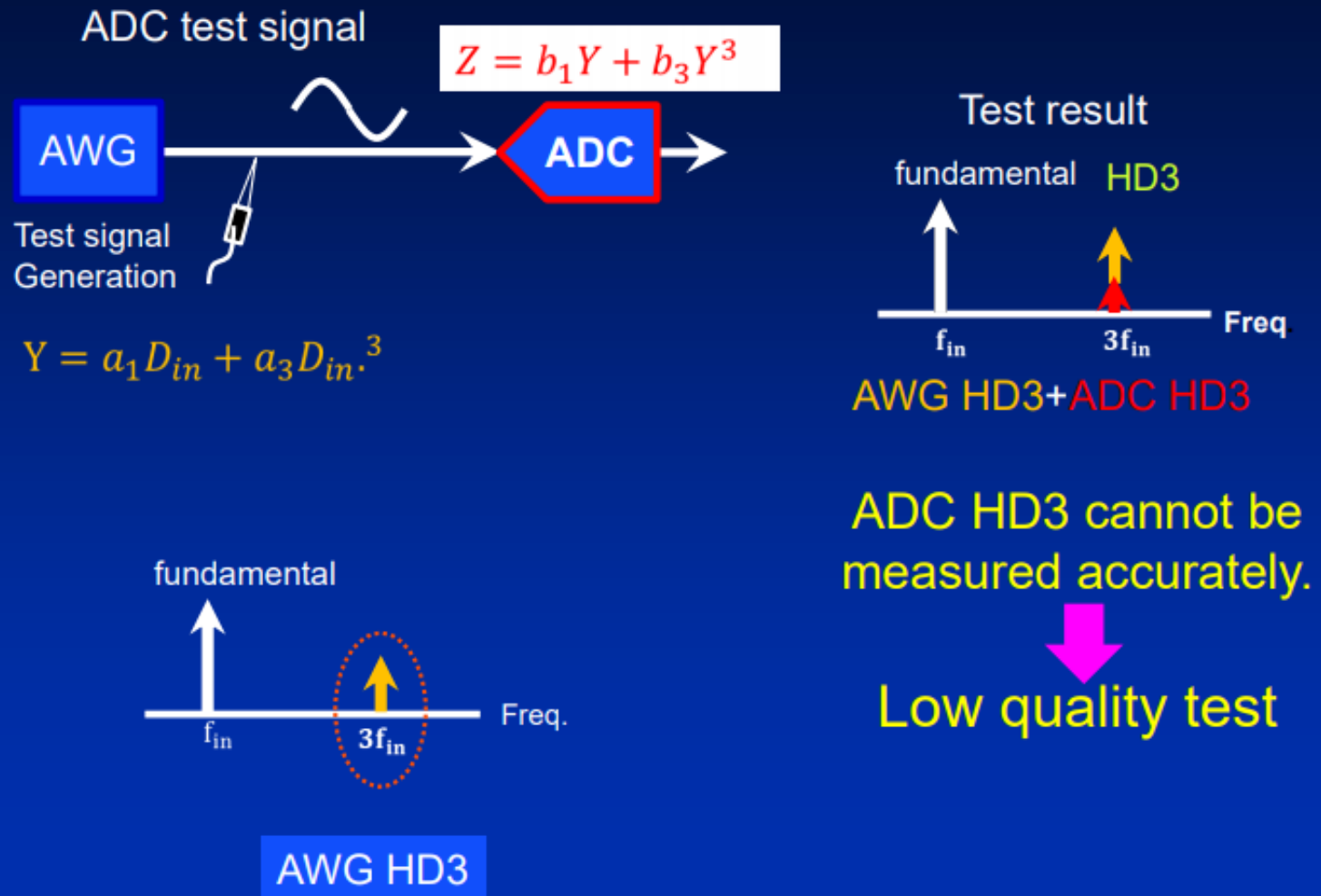


AWG: Arbitrary Waveform Generator

# Low-Distortion Sine Wave Generation

- Low-distortion sine-wave generation using Arbitrary Waveform Generator (AWG)
- Compensation of AWG nonlinearity by digital pre-distortion
- ADC test signal


## Phase switching method

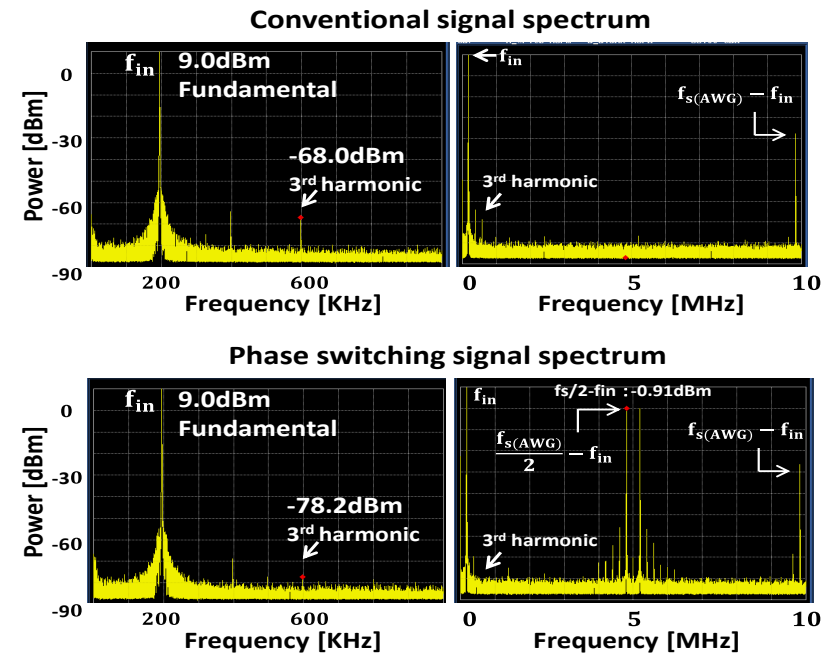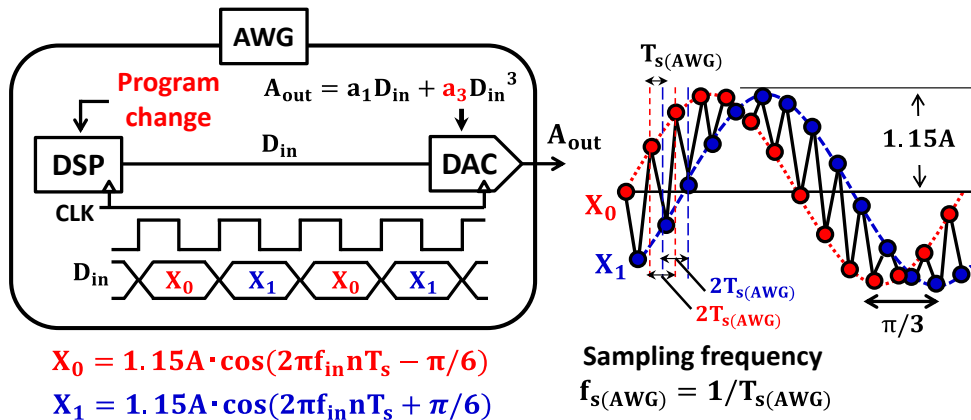

[13] F. Abe, Y. Kobayashi, K. Sawada, K. Kato, O. Kobayashi, H. Kobayashi, "Low-Distortion Signal Generation for ADC Testing," IEEE International Test Conference (Oct. 2014).

# Low IMD3 2-Tone Signal Generation with AWG for Communication Application ADC Testing

IMD: Intermodulation Distortion

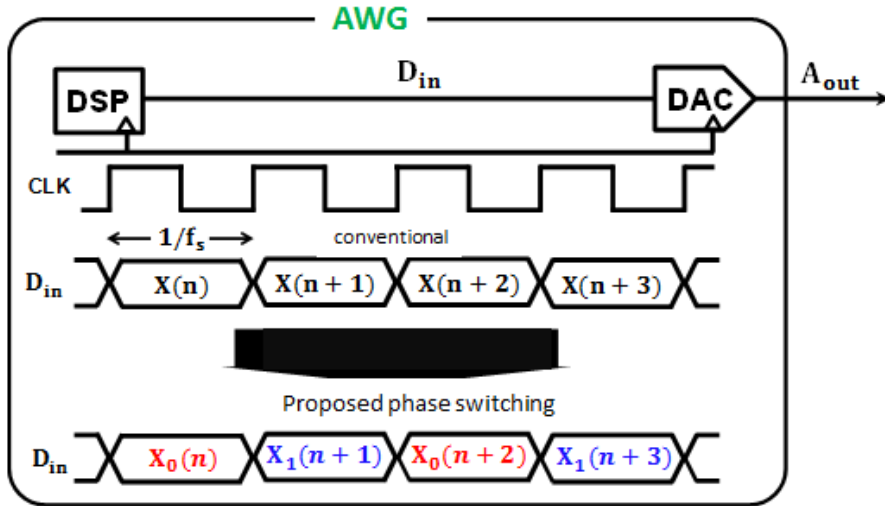

Conventional


$$X(n) = A\cos(2\pi f_1 n T_s) + A\cos(2\pi f_2 n T_s)$$

Proposed phase switching

$$X_0(n) = B\cos(2\pi f_1 n T_s + \pi/6) + B\cos(2\pi f_2 n T_s - \pi/6)$$

$$X_1(n) = B\cos(2\pi f_1 n T_s - \pi/6) + B\cos(2\pi f_2 n T_s + \pi/6)$$

Measurement Results (AWG 2-tone output)


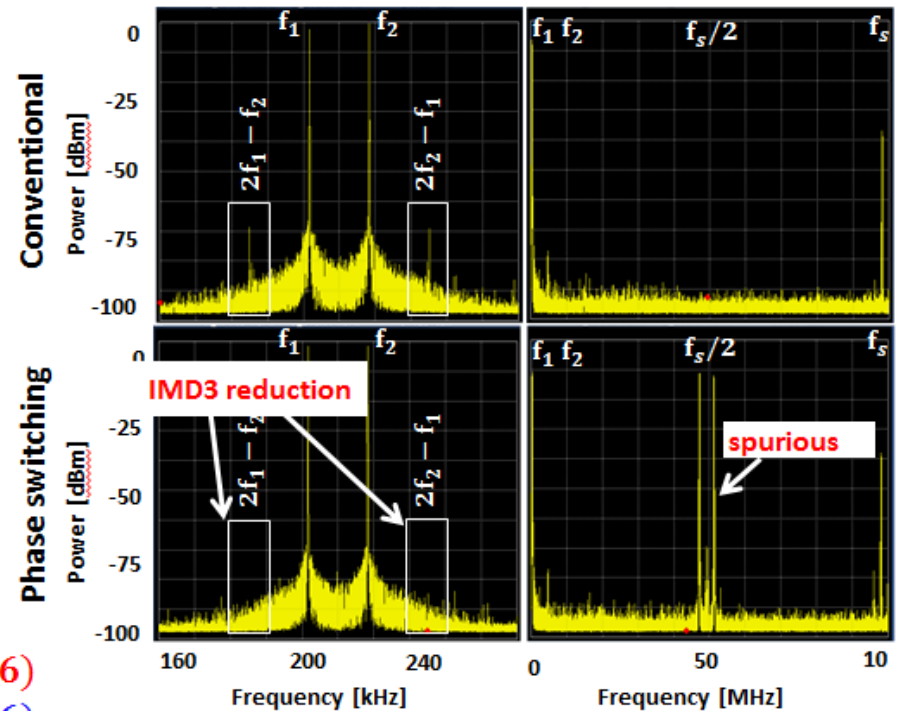


[14] K. Kato, H. Kobayashi, et. al.,

“Two-Tone Signal Generation for Communication Application ADC Testing”,

The 21st IEEE Asian Test Symposium, Niigata, Japan (Nov. 2012).
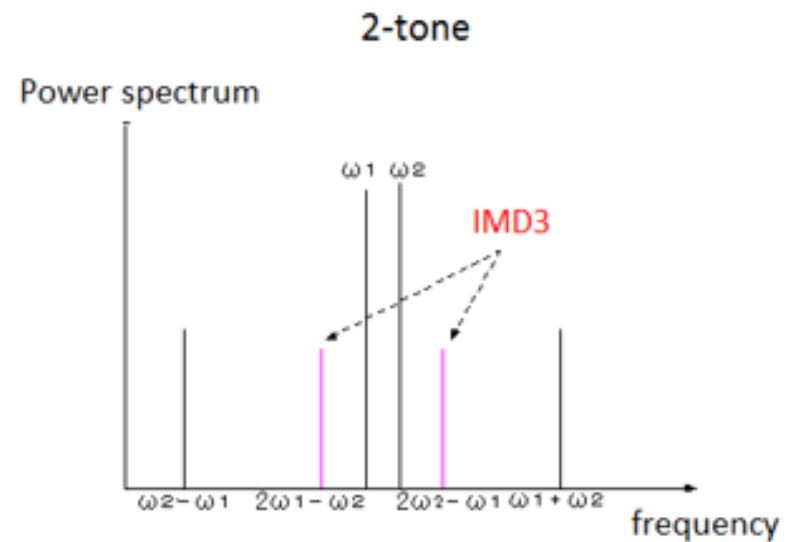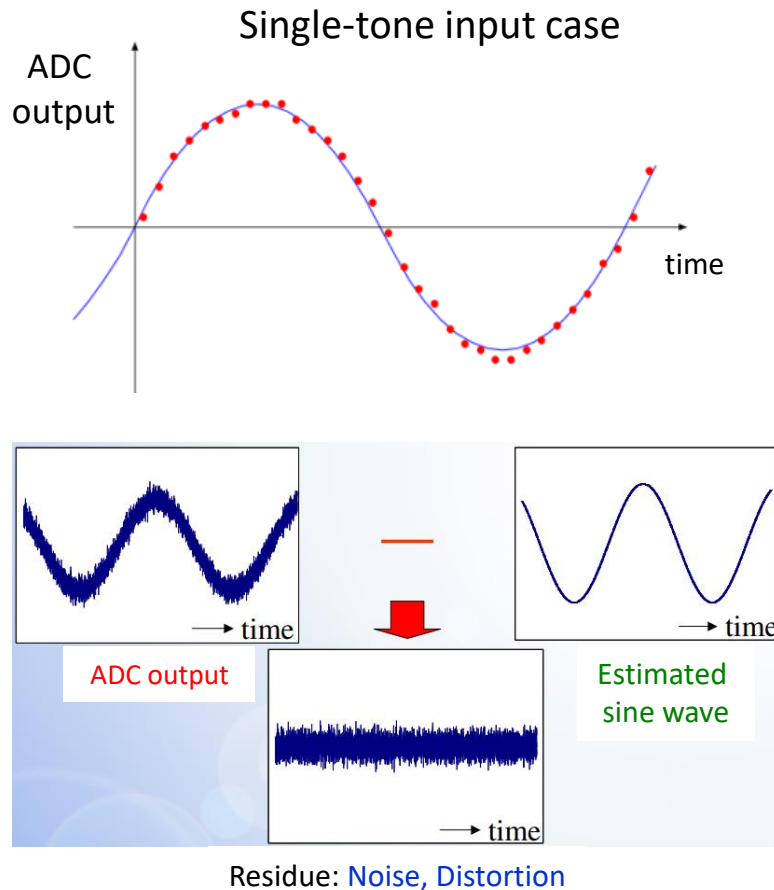
# Two-tone Curve Fitting Algorithm for Communication Application ADC Testing



- [15] Y. Motoki, H. Sugawara, H. Kobayashi, et. al.,  
“Multi-Tone Curve Fitting Algorithms for Communication Application ADC Testing”,  
Electronics and Communication in Japan: Part 2, Wiley Periodicals Inc. (2003).

# Complex Multi-Bandpass $\Delta\Sigma$ Modulator for I-Q Signal Generation



- Generation of high quality analog I-Q signals
- Testing of communication application ICs
- Digital rich

(Suitable to the realization with nano CMOS → **Low cost**)

$\Delta\Sigma$   
modulation

Complex signal  
processing

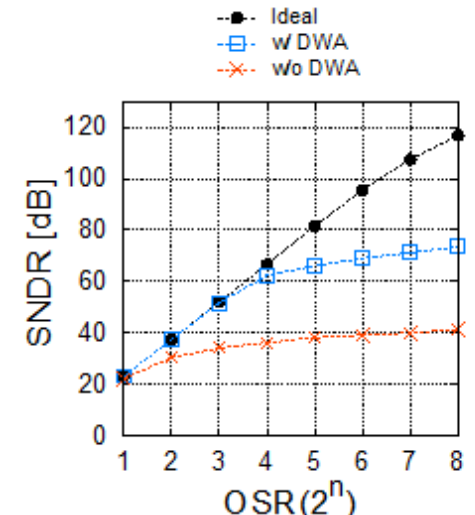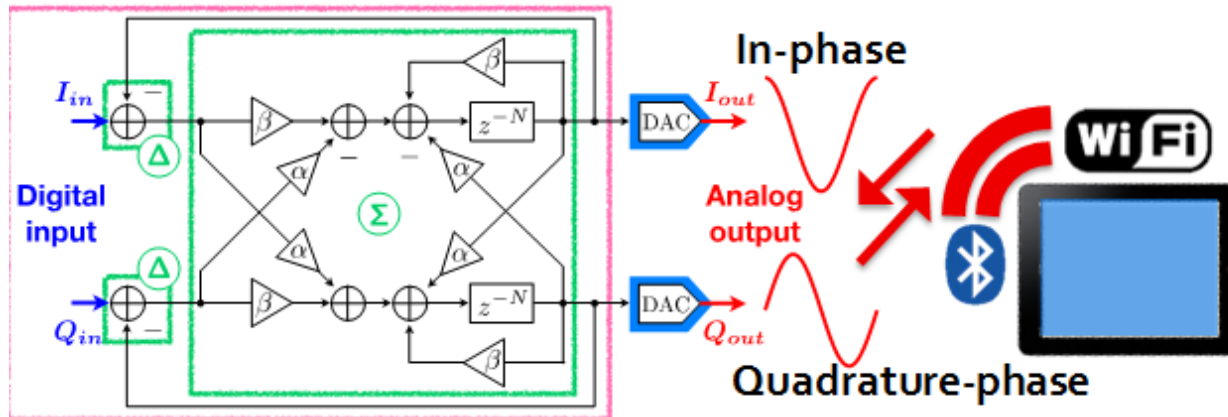Non-linear correction algorithm  
for Multi-bit DAC



[16] M. Murakami, H. Kobayashi, et. al.,  
“I-Q Signal Generation Techniques for Communication IC Testing and ATE Systems”,  
IEEE International Test Conference, Fort Worth, TX (Nov. 2016).

# Contents

---


- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- ADC Linearity Testing
- Analog Signal Generation with AWG
- **Waveform Sampling Technique**
- Timing Testing
- Challenges and Conclusion

# Waveform Sampling Technology

- Waveform sampling is important for analog signal test.
- Many issues for high performance sampling circuit
  - Noise, Distortion
  - Bandwidth
  - Jitter, Aperture time
  - Sampling clock rate
  - Power

## ■ Open-loop S/H circuit:


Switch and Capacitor

 


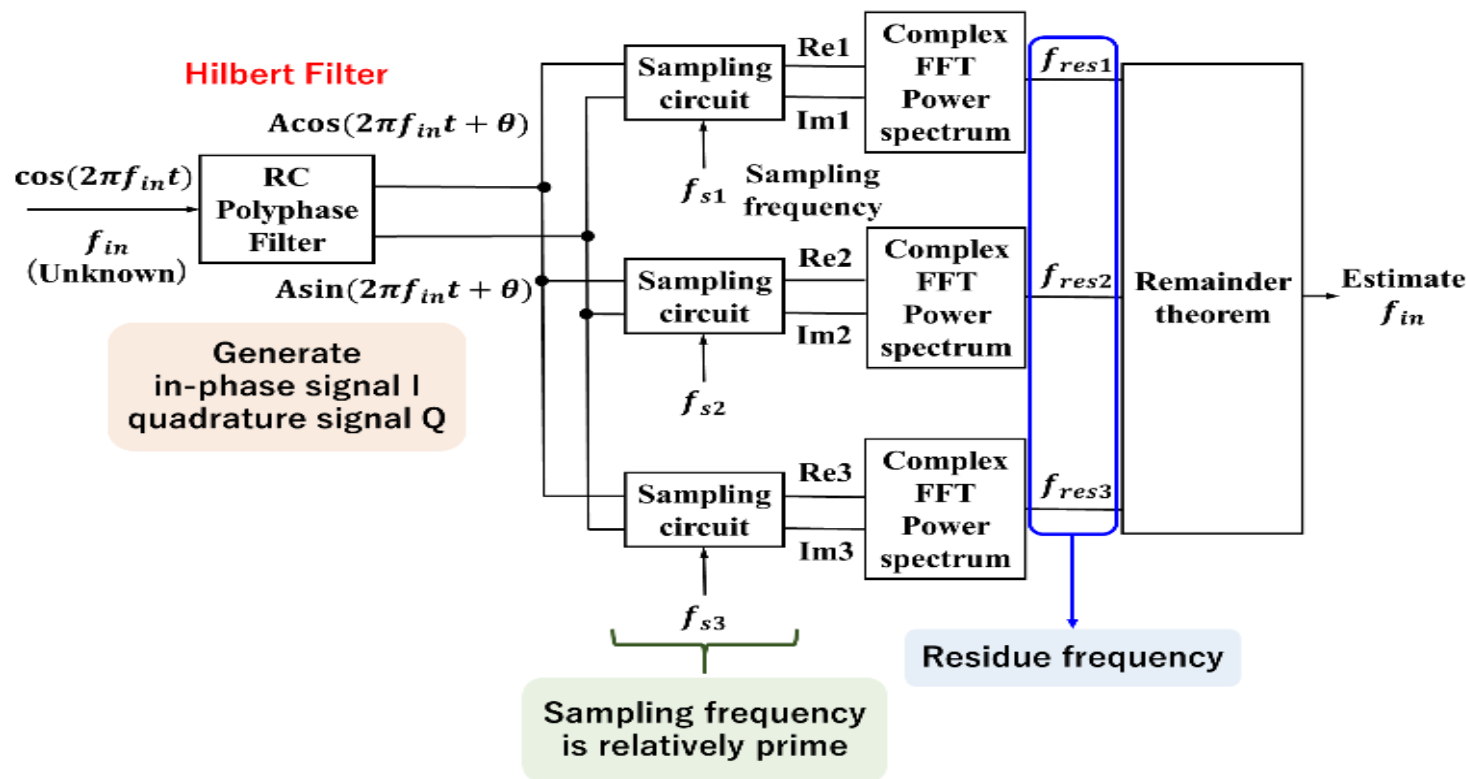
# Residue Sampling Circuit

- Proactive usage of aliasing by waveform sampling
  - Multiple **low-rate sampling** circuits
- **High-frequency waveform** sampling




[17] Y. Abe, S. Katayama, C. Li, A. Kuwana, H. Kobayashi, "Frequency Estimation Sampling Circuit Using Analog Hilbert Filter and Residue Number System", 13th IEEE International Conference on ASIC, Chongqing, China (Oct. 2019).

# Equivalent-Time Sampling in Testing

- **Production Test :**

Input signal is controllable

 
Waveform reconstruction of repetitive signal



Sampling oscilloscope

- **Measurement :** Input signal is unknown

# Waveform Missing Phenomena






 


Toothless waveform appears

# Waveform Missing Conditions


$$f_{CLK} \gg f_{sin} \quad f_{CLK} \approx \frac{1}{\alpha} f_{sin} \quad \left( \alpha = 1, \frac{1}{2}, \frac{1}{3}, \frac{2}{3}, \dots, \frac{1}{6}, \dots \right)$$

$$f_{CLK} \approx f_{sin}$$

      

Sampling points move little  $\rightarrow$  Requires long time

# Waveform Sampling Condition

 



$$T_{CLK} = ? \times T_{sig}$$

- [18] Y. Sasaki, Y. Zhao, A. Kuwana, H. Kobayashi,  
"Highly Efficient Waveform Acquisition Condition in Equivalent-Time Sampling System"  
27th IEEE Asian Test Symposium, Hefei, Anhui, China (Oct. 2018)
  
# Proposed Golden Ratio Sampling

$$f_{CLK} = \varphi \times f_{sig}$$





$\varphi$  : Golden ratio ( = 1.6180339887... )



Sampling points disperse uniformly through measurement

# Golden Ratio is Everywhere !

The most beautiful ratio

    


# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- **Timing Testing**
- Challenges and Conclusion



# Time-to-Digital Converter (TDC)

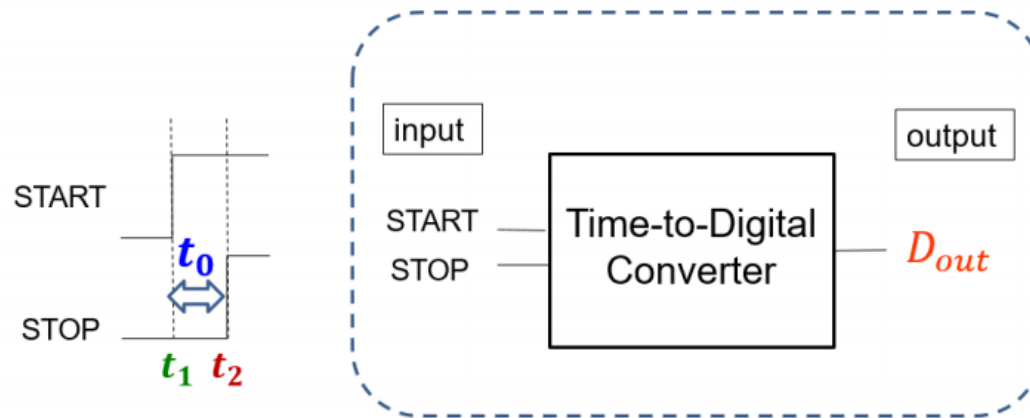

This section details the SAR TDC architecture and its timing characteristics. It includes a timing diagram for two clock signals, CLK1 and CLK2, with a period  $T$ . A photograph of a printed circuit board (PCB) is shown. A timing diagram for a memory interface shows CLK, Command (READ), DQS, and Data signals. The SAR TDC circuit diagram shows CLK1 and CLK2 inputs, a MUX, and SAR Logic, with a 3-bit digital output  $D_{out}$ .

**High-speed I/O interface signal timing testing**

- ✓ Small circuit
- ✓ Full digital
- ✓ High linearity
- ✓ High resolution

**SAR TDC**

- [19] Y. Ozawa, H. Kobayashi, et. al.,  
“SAR TDC Architecture with Self-Calibration Employing Trigger Circuit,”  
The 26th IEEE Asian Test Symposium, Taipei, Taiwan (Nov. 2017)

 
# TDC BOSTs for Timing Signal Testing



Single-bit  $\Delta\Sigma$  TDC with analog FPGA



Multi-bit  $\Delta\Sigma$  TDC with analog FPGA



Flash-type TDC with analog FPGA




Flash-type TDC with digital FPGA

## BOST: Built-Out Self-Test

[20] T. Chujo, H. Kobayashi, et. al., "Timing Measurement BOST With Multi-bit Delta-Sigma TDC", 20th IEEE International Mixed-Signal Testing Workshop, Paris, France (June, 2015).

# Phase Noise Test with $\Delta\Sigma$ TDC

## Phase noise in oscillator

 

## Malfunction of electronic systems

- RF circuit & system
- ADC



Phase noise test **at low cost**, in short time


### Conventional



- **Expensive** : Spectrum analyzer
- **Long** : test time ( ~10seconds)



### Proposed


Simple circuit 

$\Delta\Sigma$  Time-to-Digital Converter




[21] Y. Osawa, D. Hirabayashi, N. Harigai, H. Kobayashi, K. Niitsu, O. Kobayashi, "Phase Noise Measurement Techniques Using Delta-Sigma TDC", IEEE International Mixed-Signals, Sensors and Systems Test Workshop, Porto Alegre, Brazil (Sept. 2014).

# On-Chip Jitter Measurement Circuit

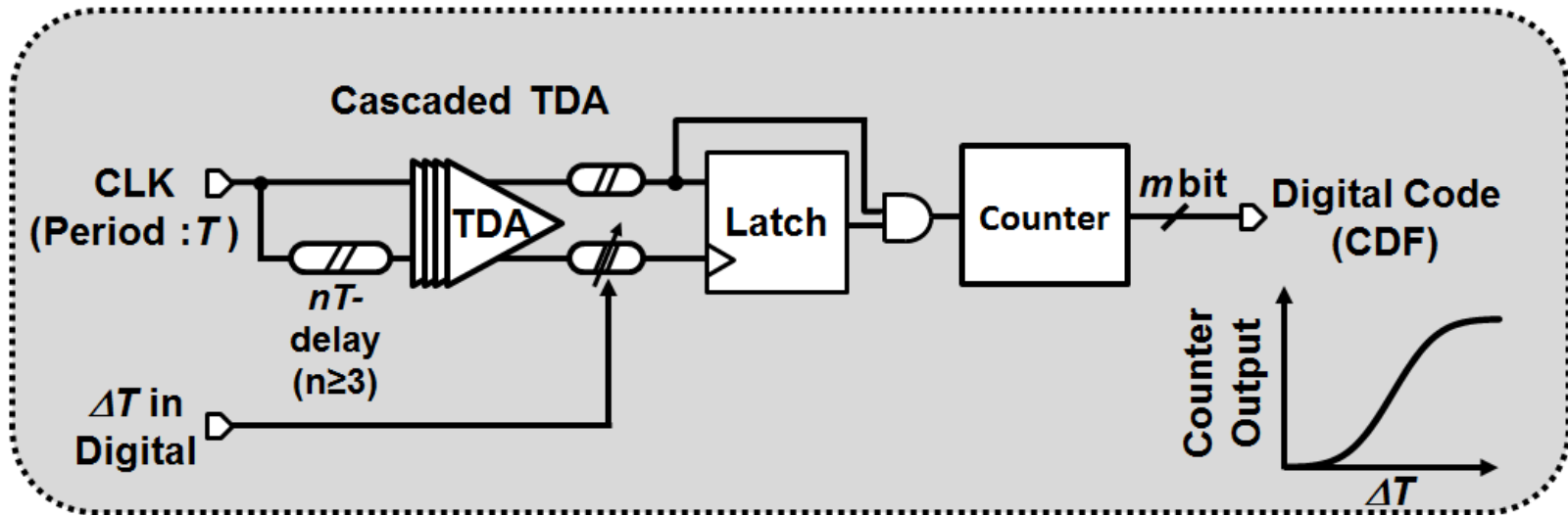

Experiments show that  
1.67 ps RMS timing jitter  
can be measured

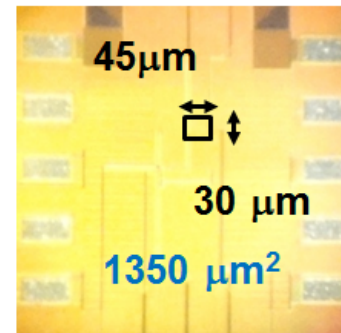Process : 65 nm CMOS  
Supply Voltage : 1.2 V



- [22] K. Niitsu, M. Sakurai, N. Harigai, T. Yamaguchi, H. Kobayashi,  
"CMOS Circuits to Measure Timing Jitter Using a Self-Referenced Clock and  
a Cascaded Time Difference Amplifier with Duty-Cycle Compensation,"  
IEEE Journal of Solid-State Circuits, (Nov. 2012)


# Contents

---

- Research Background
- Analog/Mixed-Signal Circuit Testing
- Operational Amplifier Testing
- ADC Linearity Testing
- Analog Signal Generation with AWG
- Waveform Sampling Technique
- Timing Testing
- **Challenges and Conclusion**
 
# Challenges of Analog Testing

- Analog part testing is important for mixed-signal SOC cost reduction.
- Cost is the most important criterion.
- Its research is not easy.
- Analog BIST technique progress may be slow but it is steady.
- Solve the problems one by one.  
No general or systematic method
- Should be practical.
- Use engineering sense, as well as science.



愚公移山

# Future Perspective

- Use all aspects of technologies
  - Circuit technique
  - Cooperation among BIST, BOST & ATE as well as software & network
  - Signal processing algorithm
  - Use resources in SOC such as  $\mu$ P core, memory, ADC/DAC



Aristotelēs

「学問無王道」

There is no science without measurement.

There is no production without test

No royal road to analog testing

# Acknowledgements

---

Special thanks to  
all of Kobayashi Lab members and  
research collaborators  
who have contributed the research results  
presented here