

# Multi-Band CMOS Low Noise Amplifiers Utilizing Transformers

Masataka Kamiyama Daiki Oki Satoru Kawauchi  
Congbing Li Nobuo Takahashi  
Toru Dan Seiichi Banba Haruo Kobayashi



*Gunma University*  
*ON Semiconductor*    *Toyohashi University of Technology*

# Outline

---


- Research Background & Objective
- Dual Band LNA
  - Circuit Structure & Principle
  - Simulation
- Triple-Band LNA
  - Circuit Structure & Principle
  - Simulation
- Consideration
  - Layout of Inductor & Transformer
- Conclusion

# Outline

- **Research Background & Objective**
- Dual Band LNA
  - Circuit Structure & Principle
  - Simulation
- Triple-Band LNA
  - Circuit Structure & Principle
  - Simulation
- Consideration
  - Layout of Inductor & Transformer
- Conclusion

# Research Background & Objective

## Radio Transceiver

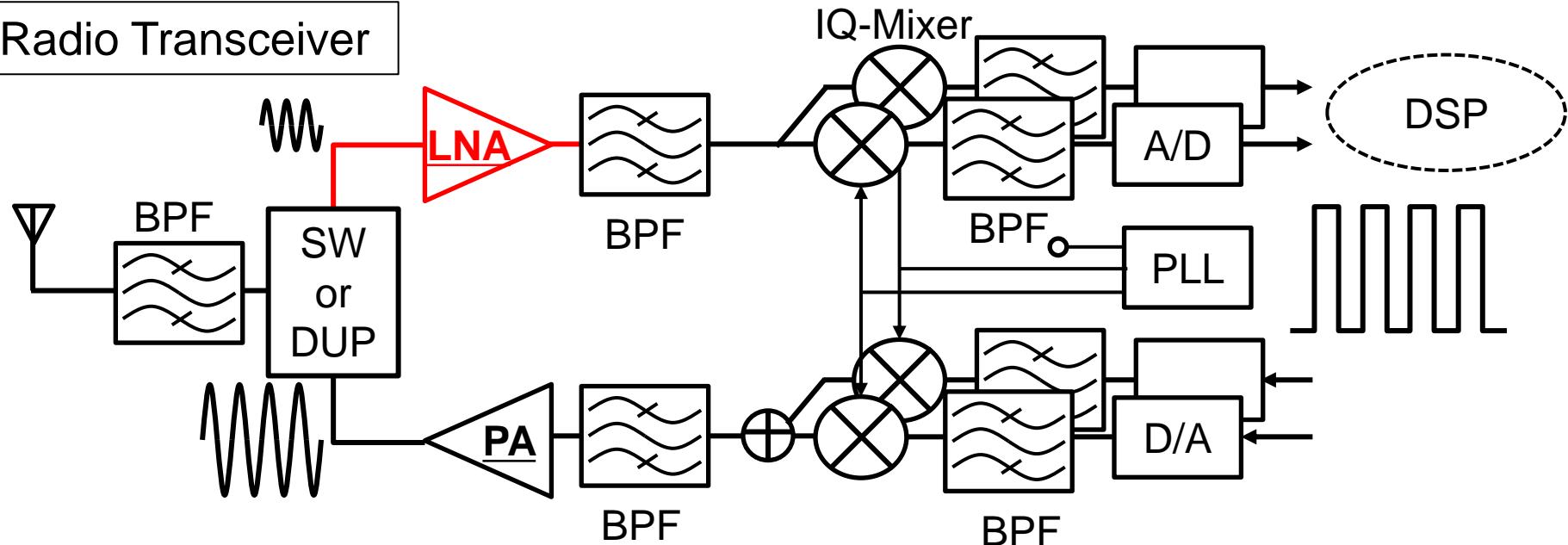

## Receiver Side

### Low Noise Amplifier(LNA)


••• Amplify small signal without noise & distortion

## Challenge

Multi-Band performance for many wireless standards

# Research Goal

Radio Transceiver

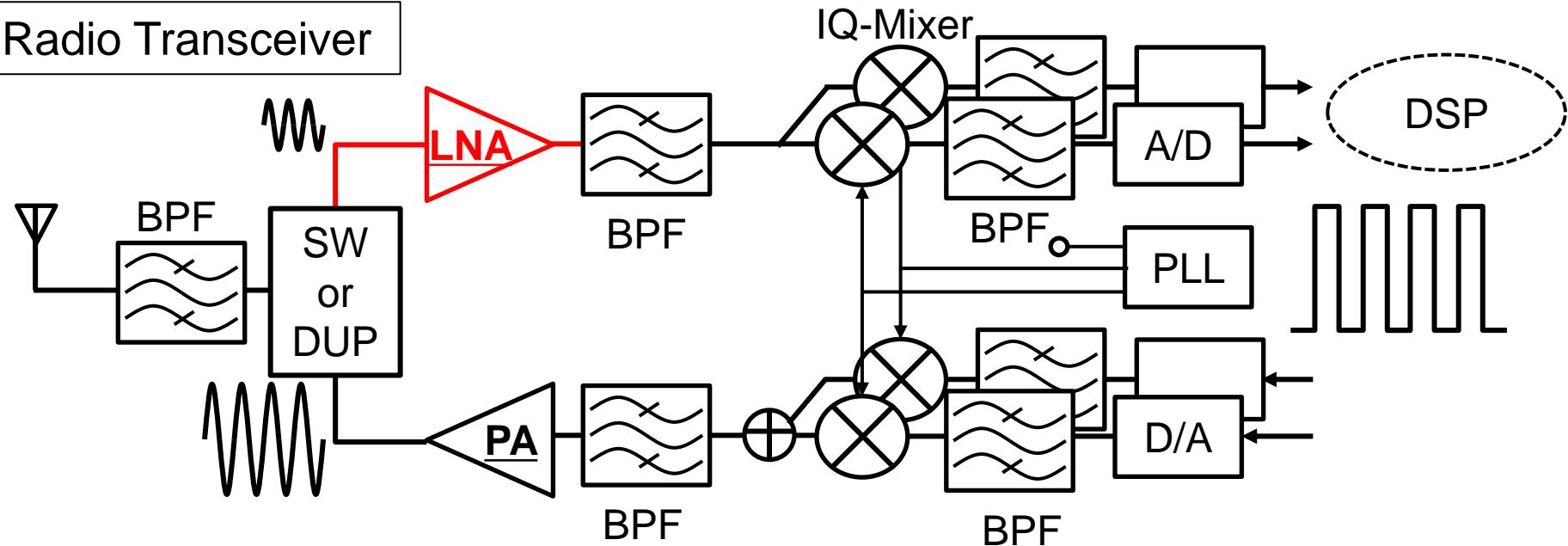

Reference

Dual-Band LNA

extension

Proposal

Triple-Band LNA

# Outline

---

- Research Background & Objective
- **Dual Band LNA**
  - Circuit Structure & Principle
  - Simulation
- Triple-Band LNA
  - Circuit Structure & Principle
  - Simulation
- Consideration
  - Layout of Inductor & Transformer
- Conclusion

# Research Paper

**Objective** Extend Multi-Band for Narrowband Amplifier

## Technique of Dual-Band LNA Utilizing Transformers

- Paper Title

A Dual-Band 2.45/6 GHz CMOS LNA Utilizing a Dual-Resonant Transformer-Based Matching Network

- Author

N. M. Neihart with Iowa University


J. Brown

X. Yu

- Journal

IEEE Trans. on Circuits and Systems I, (Aug. 2012)


# Neihart's Dual-Band LNA

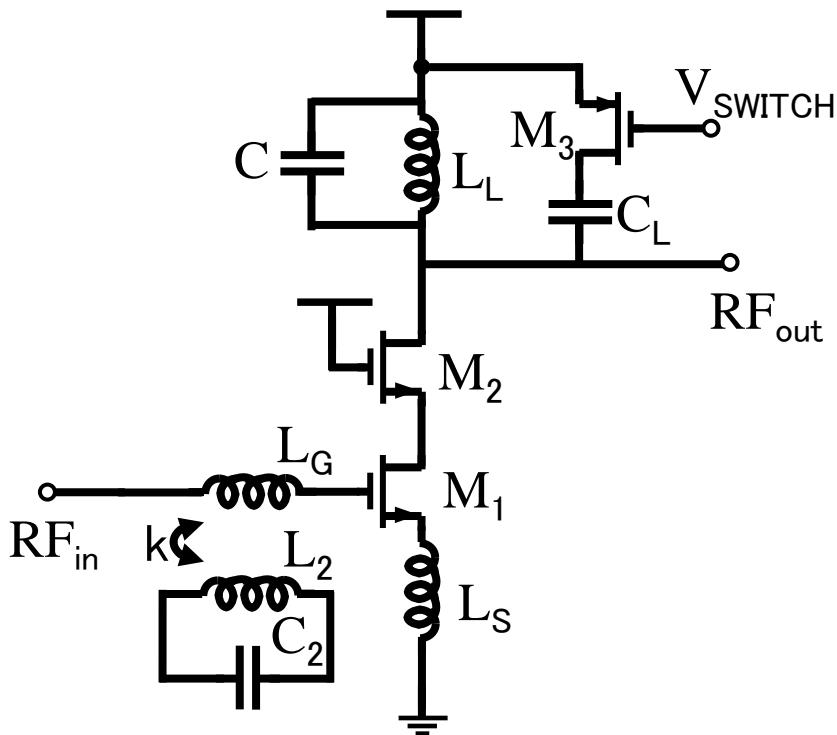

## Dual-Band LNA Utilizing Transformers

- $L_G$ ,  $L_2$  : Transformer-coupled with coupling coefficient  $k$
- **Load side**  
Switch 2 resonance frequencies by  $M_3$
- **Input matching side**  
Realized 2 matching points by transformer-coupling


# Neihart's Dual-Band LNA

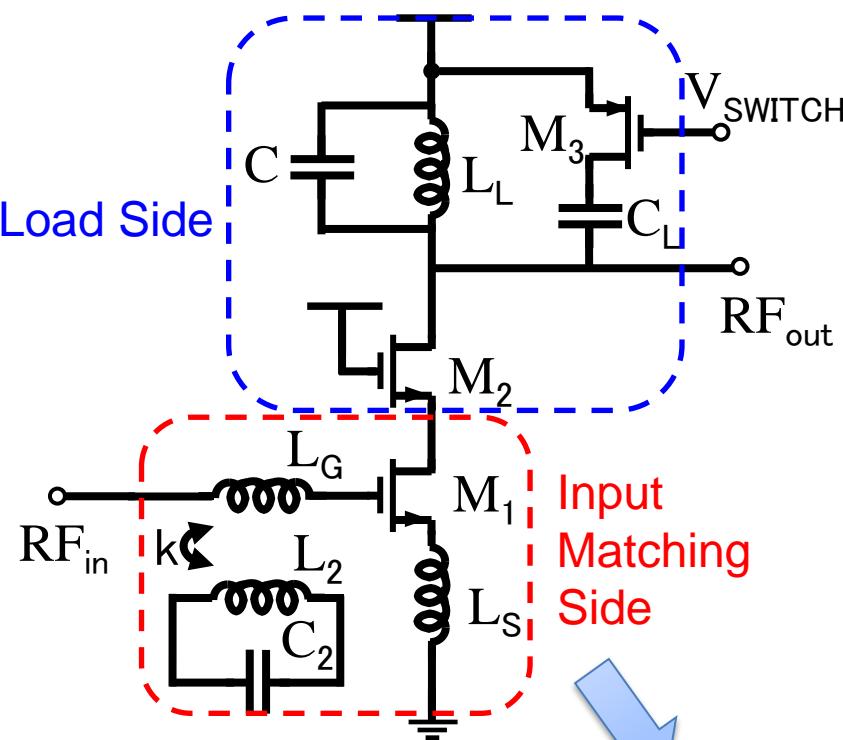


## Dual-Band LNA Utilizing Transformers

- $L_G, L_2$  : Transformer-coupled with coupling coefficient  $k$
- **Load side**  
Switch 2 resonance frequencies by  $M_3$
- **Input matching side**  
Realized 2 matching points by transformer-coupling

## Small-Signal Equivalent Model

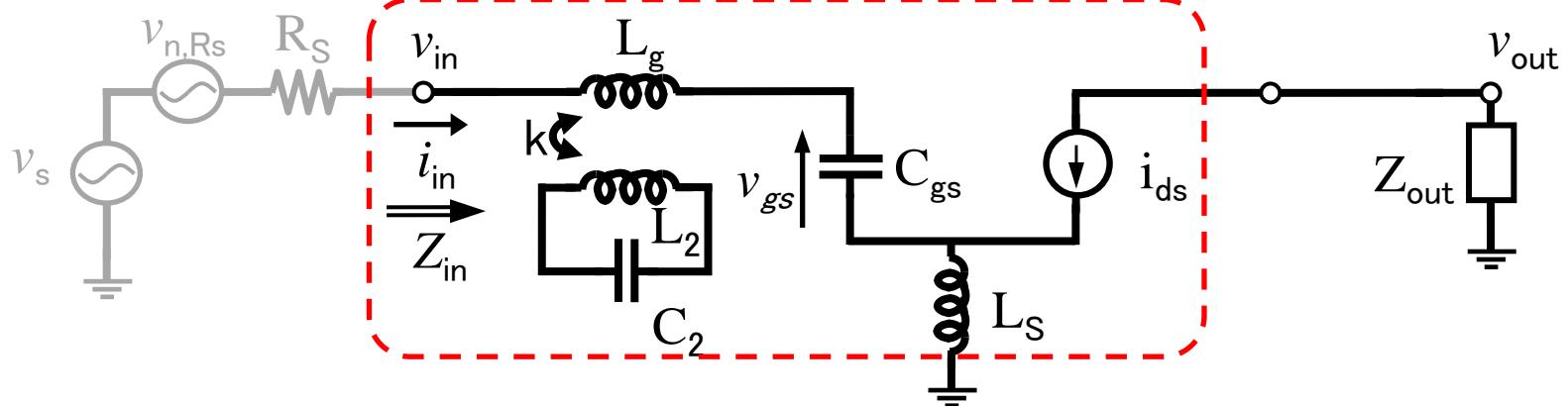

# Neihart's Model Circuit Analysis

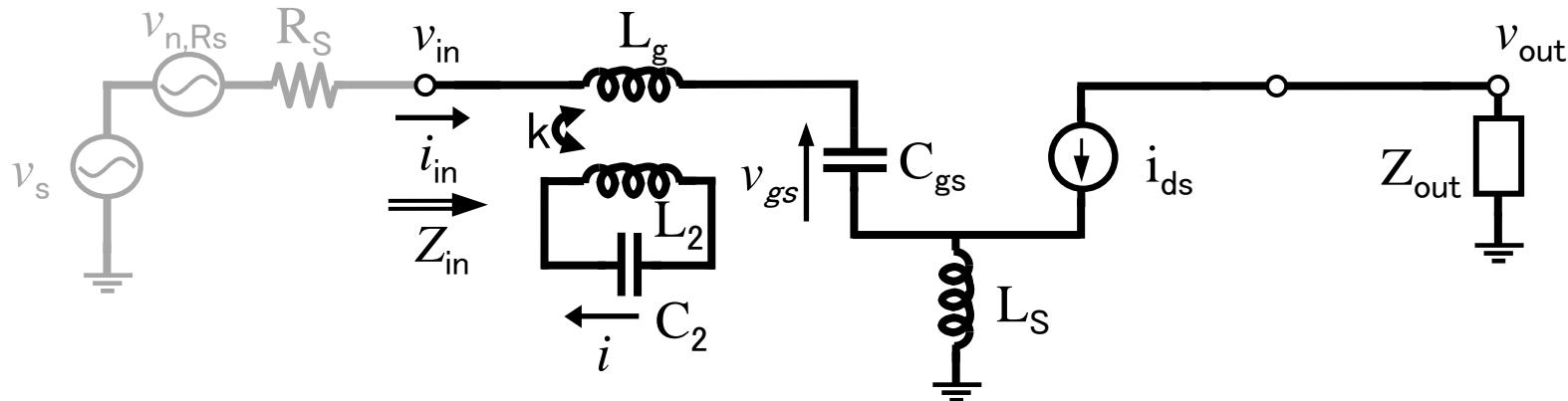

Input impedance  $Z_{in}$

$$Z_{in} = \frac{g_m L_s}{C_{gs}} + j \left\{ \omega(L_g + L_s) - \frac{1}{\omega C_{gs}} + \frac{\omega^3 M^2 C_2}{1 - \omega^2 L_2 C_2} \right\} \quad M = k \sqrt{L_g L_2}$$

Real Part  $\Rightarrow R_s(50\Omega)$

Imaginary Part  $\Rightarrow 0$   
 $\omega$ : resonance frequency

Solving  $Im(Z_{in}) = 0$


$$\omega = \pm \sqrt{\frac{a^2 + b^2 \mp \sqrt{a^4 + b^4 + a^2 b^2 (4k^2 - 2)}}{2(1 - k^2)}} \quad a = \frac{1}{\sqrt{L_1 C_{gs}}} , b = \frac{1}{\sqrt{L_2 C_2}}$$

4 solutions (2 positive numbers, 2 negative numbers)


↳ resonance frequencies
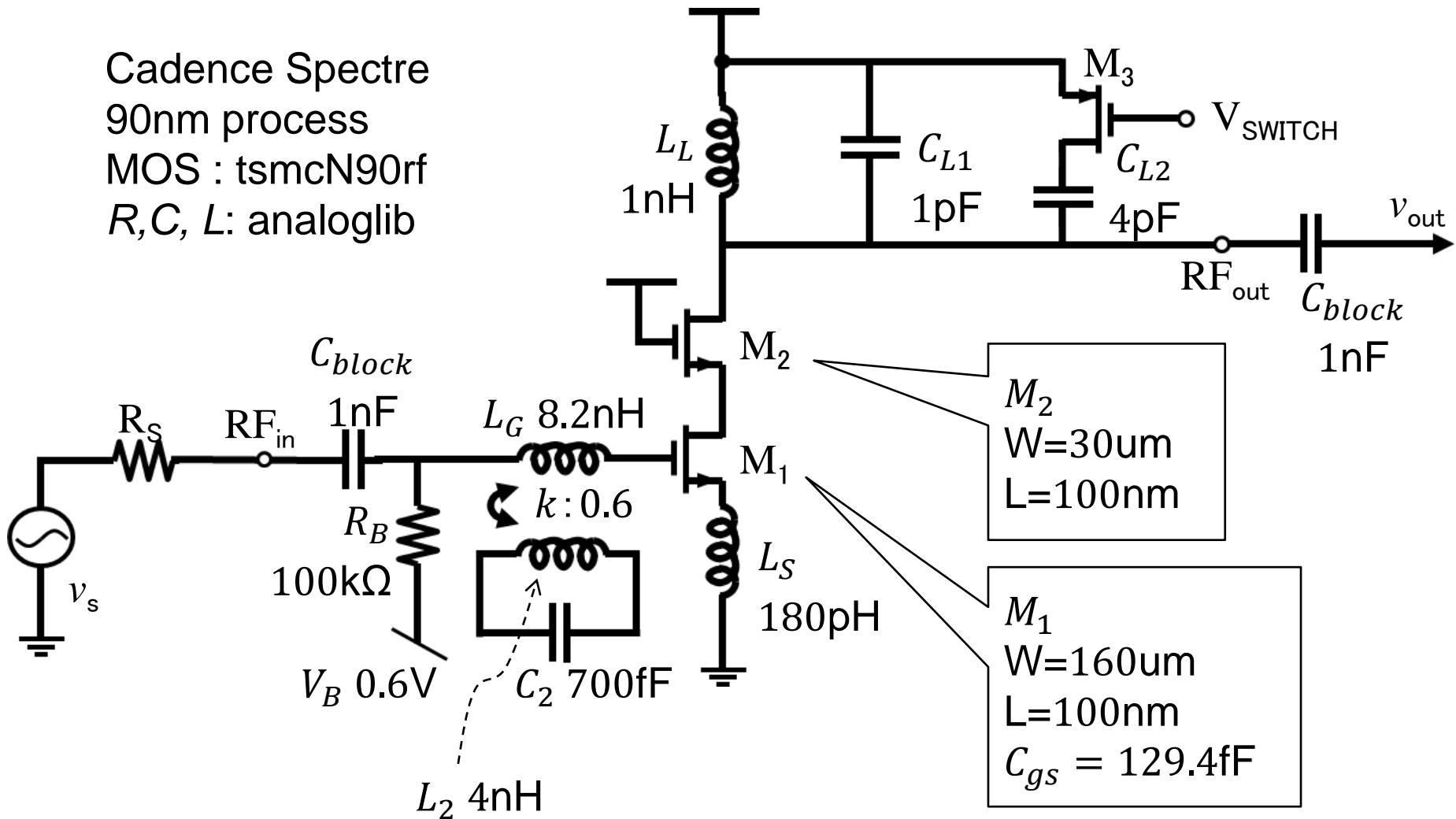
# Simulation Circuit

Cadence Spectre  
90nm process  
MOS : tsmcN90rf  
 $R, C, L$ : analoglib





# Simulation Results SP Analysis

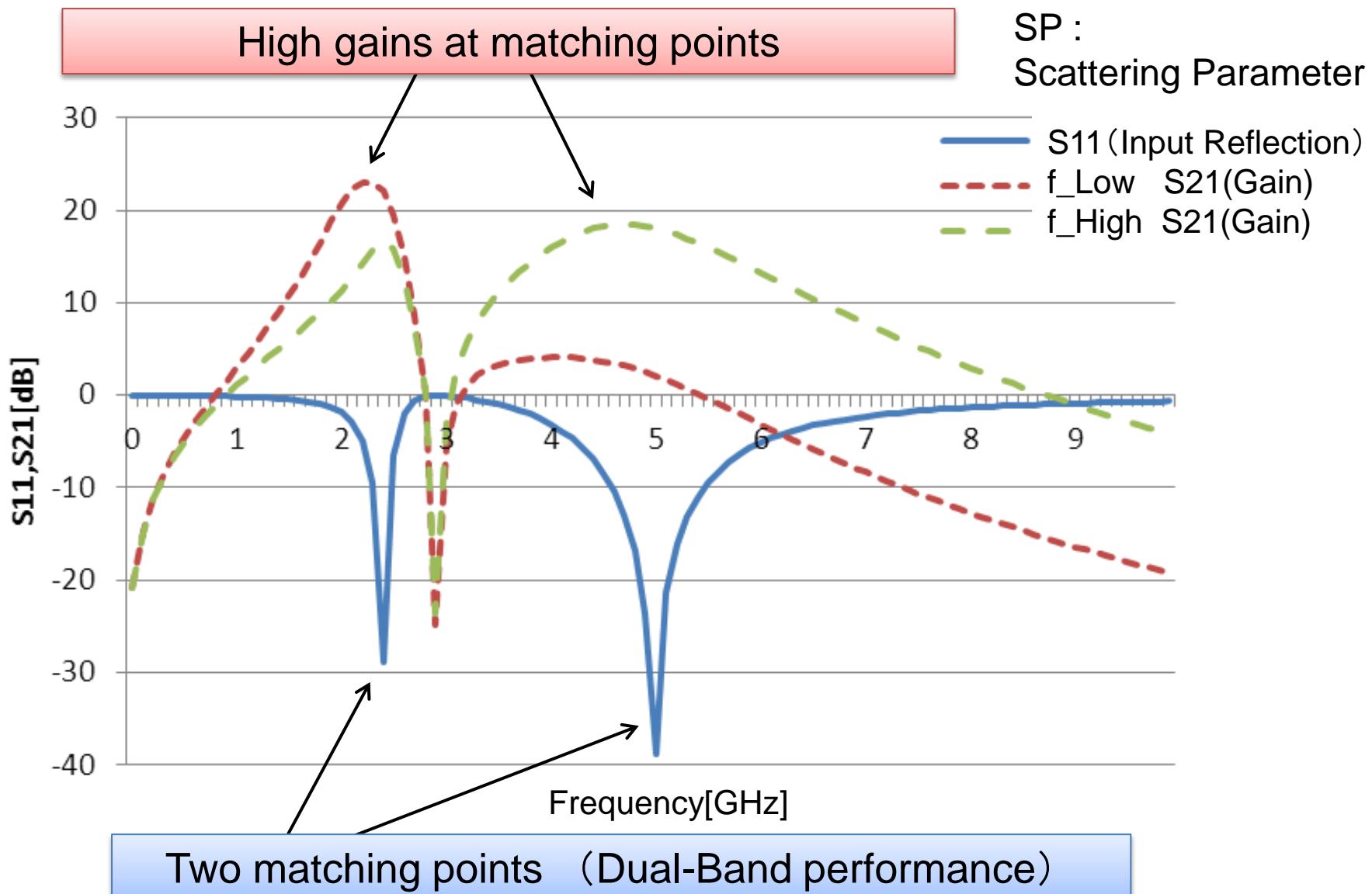

# Outline

- Research Background & Objective
- Dual Band LNA
  - Circuit Structure & Principle
  - Simulation
- **Triple-Band LNA**
  - **Circuit Structure & Principle**
  - **Simulation**
- Consideration
  - Layout of Inductor & Transformer
- Conclusion

# Extension to Triple-Band

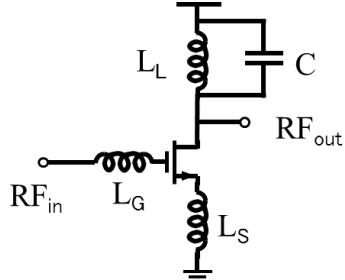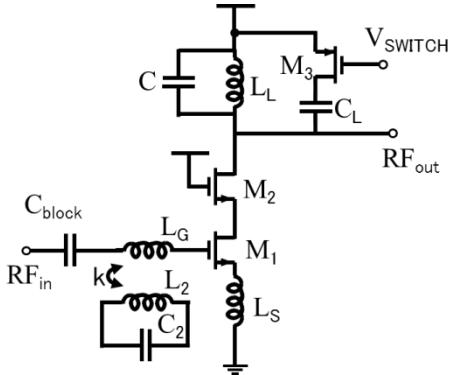	Number of Transformers	Number of Resonance Frequencies
	0	1 (Single-Band)
	1	2 (Dual-Band)
	2	Our challenge 3 (Triple-Band)



Expectation

Two transformers can realize Triple-Band

Our Design
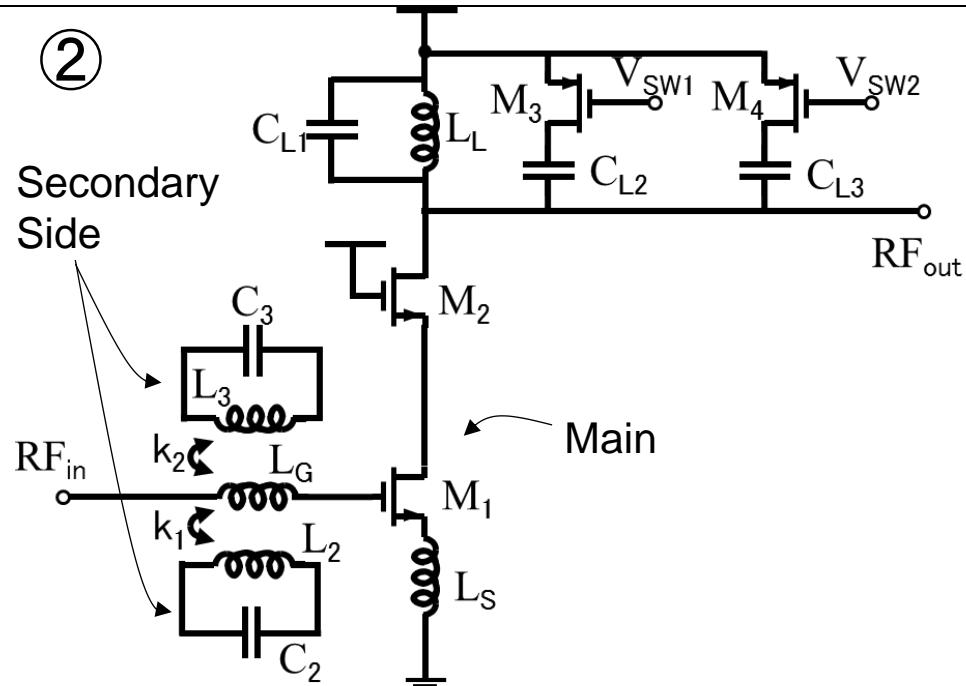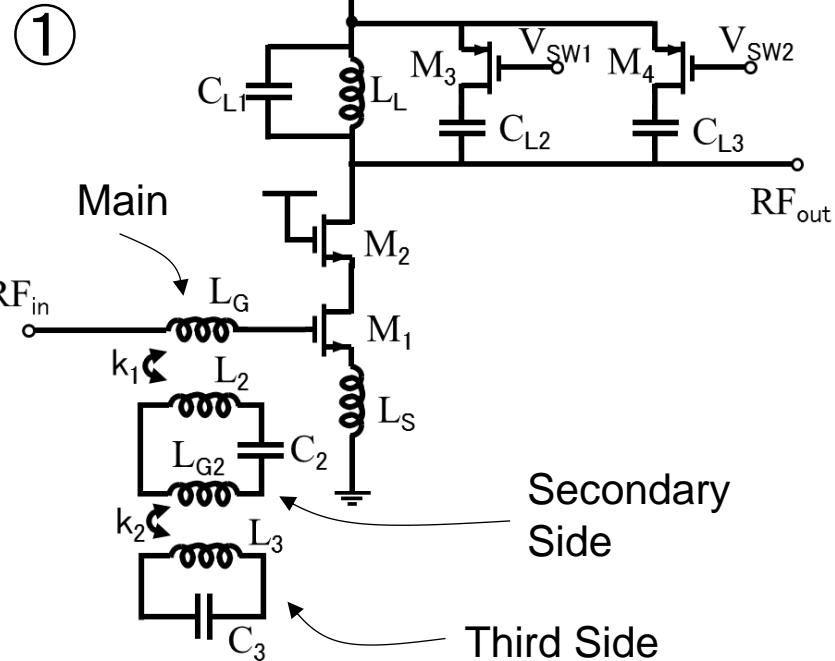
# Proposed Triple-Band LNA

Two types of Triple-Band LNA circuits ① ②




- Transformer-coupled  
 $L_G - L_2$        $L_{G2} - L_3$
- Structure  
 Main - Secondary Side - Third Side

- Transformer-coupled  
 $L_G - L_2$        $L_G - L_3$
- Structure  
 Main - Two Secondary Side
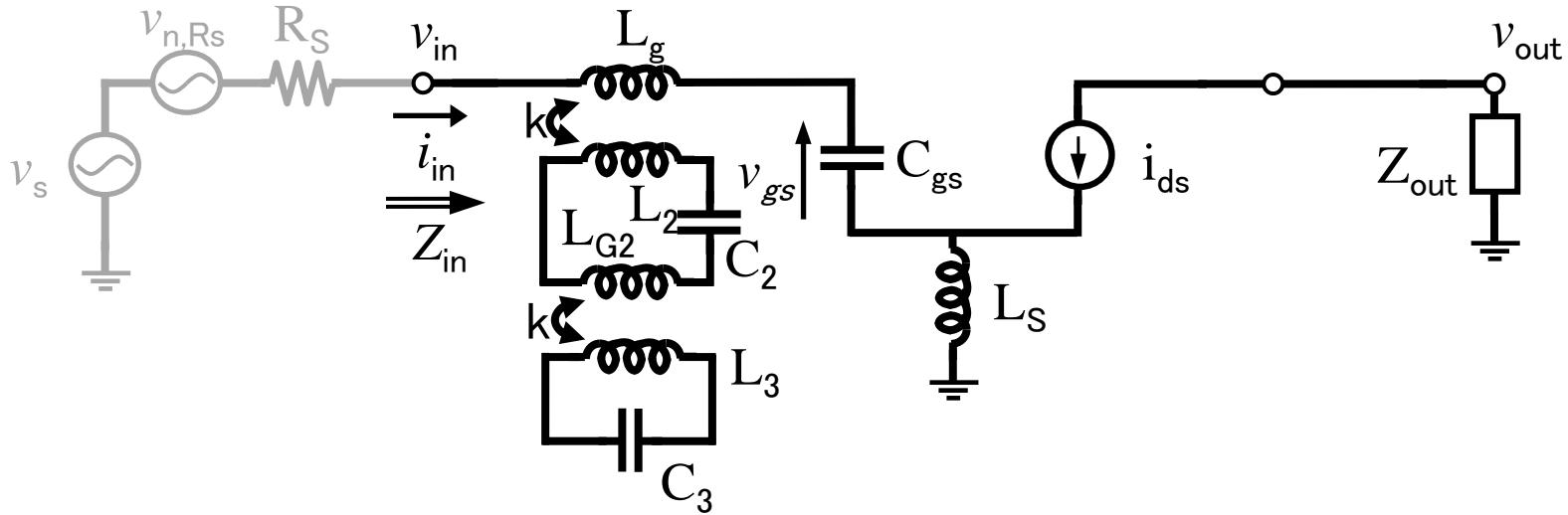
# Analysis of Triple-Band LNA①

Small-Signal Equivalent Model (Triple-Band LNA)




Input impedance  $Z_{in}$

$$\begin{aligned}
 Z_{in} = & \frac{g_m L_s}{C_{gs}} + j \left\{ \omega(L_g + L_s) - \frac{1}{\omega C_{gs}} \right. \\
 & \left. + \frac{j \omega^5 M_1^2 C_2 C_3 L_3 - j \omega^3 C_2 M_1^2}{\omega^4 \{C_2 C_3 M_2^2 - C_3 L_3 C_2 (L_2 + L_{g2})\} + \omega^2 \{C_3 L_3 + C_2 (L_2 + L_{g2})\} - 1} \right\} \\
 & \approx 0
 \end{aligned}$$

Imaginary Part  $\Rightarrow 0$
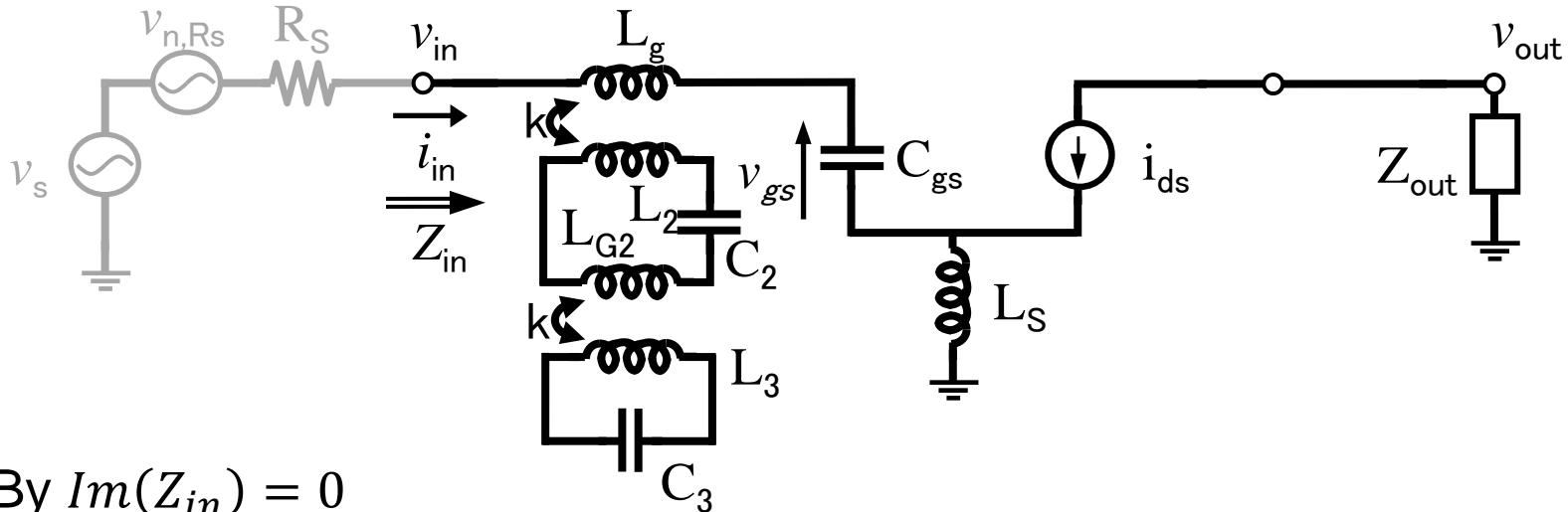
# Analysis of Triple-Band LNA①

Small-Signal Equivalent Model (Triple-Band LNA)




By  $\text{Im}(Z_{in}) = 0$

Calculate formula for determining resonance frequencies

$$\begin{aligned}
 & \omega^6 C_{gs} C_2 C_3 \{ (L_g + L_s)(L_2 + L_{g2})L_3 - (L_g + L_s)k_2^2 L_{g2} L_3 - k_1^2 L_g L_2 L_3 \} \\
 & + \omega^4 \{ -(L_g + L_s)C_{gs}(L_2 + L_{g2})C_2 - (L_g + L_s)C_{gs}L_3C_3 - (L_2 + L_{g2})C_2L_3C_3 \\
 & \quad + k_2^2 L_{g2}C_2L_3C_3 + k_1^2 L_g C_{gs}L_2C_2 \} \\
 & + \omega^2 \{ (L_g + L_s)C_{gs} + (L_2 + L_{g2})C_2 + L_3C_3 \} - 1 = 0
 \end{aligned}$$


6-th order equation (3 resonance frequencies)

# Simulation Circuit

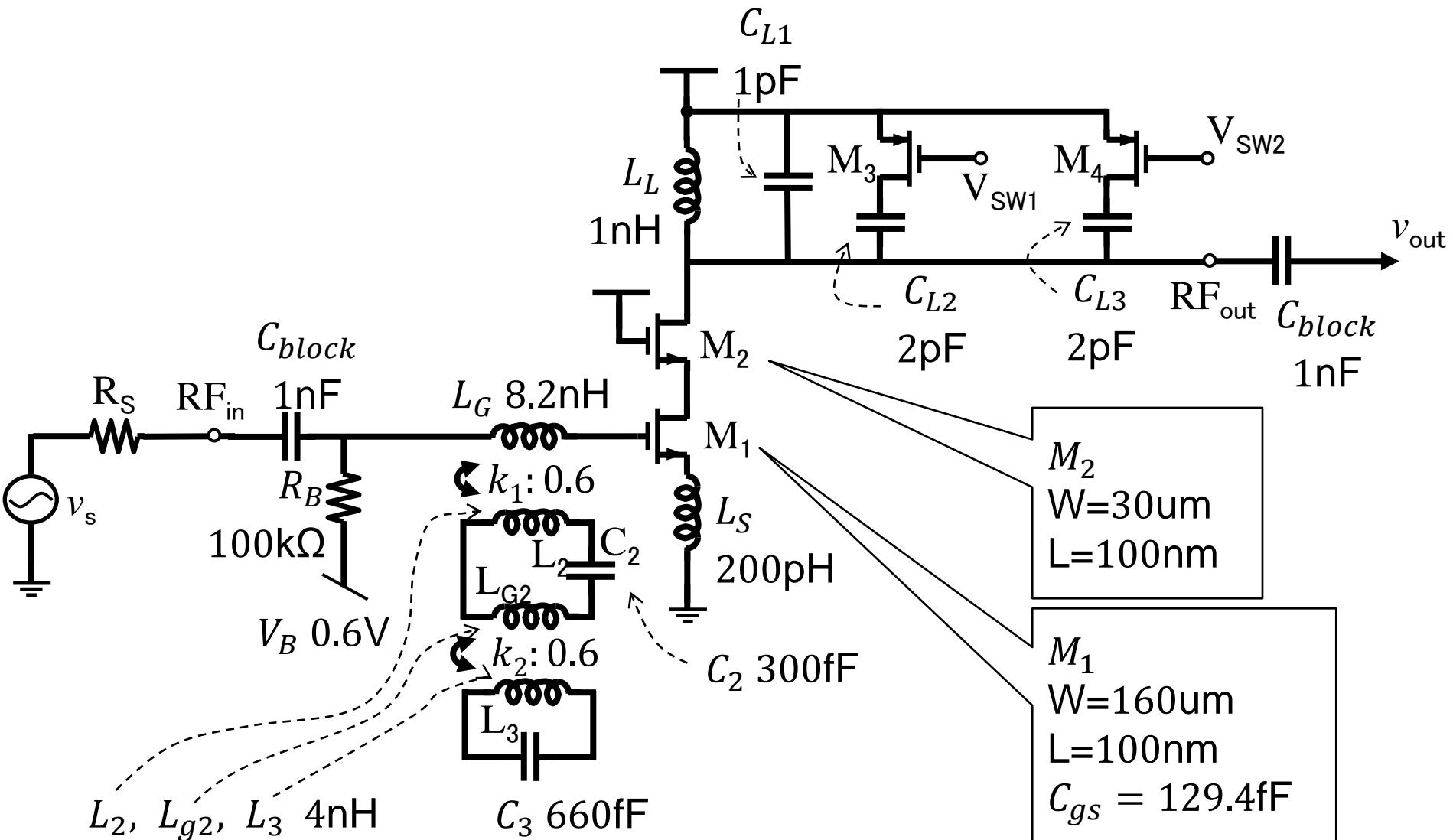

# Simulation Results SP Analysis


SP : Scattering Parameter

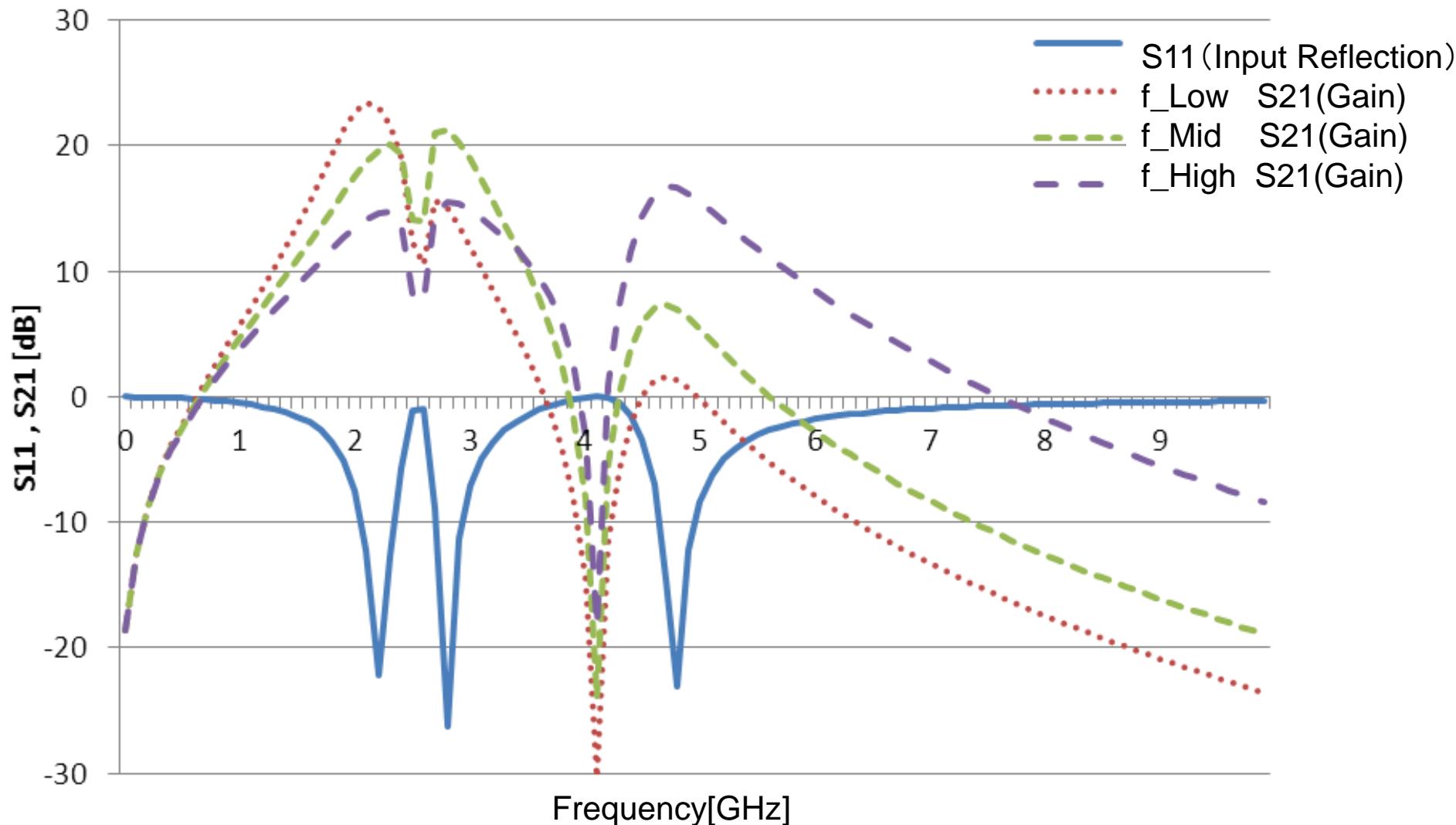

# Outline

- Research Background & Objective
- Dual Band LNA
  - Circuit Structure & Principle
  - Simulation
- Triple-Band LNA
  - Circuit Structure & Principle
  - Simulation
- **Consideration**
  - **Layout of Inductor & Transformer**
- Conclusion

# Problems when extending to Triple-Band

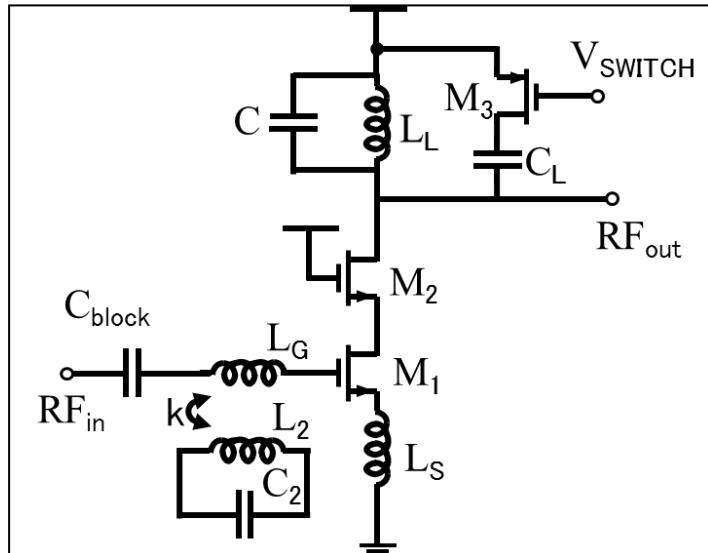


Dual-Band LNA

Dual-Band LNA

Adding Inductor

Triple-Band LNA

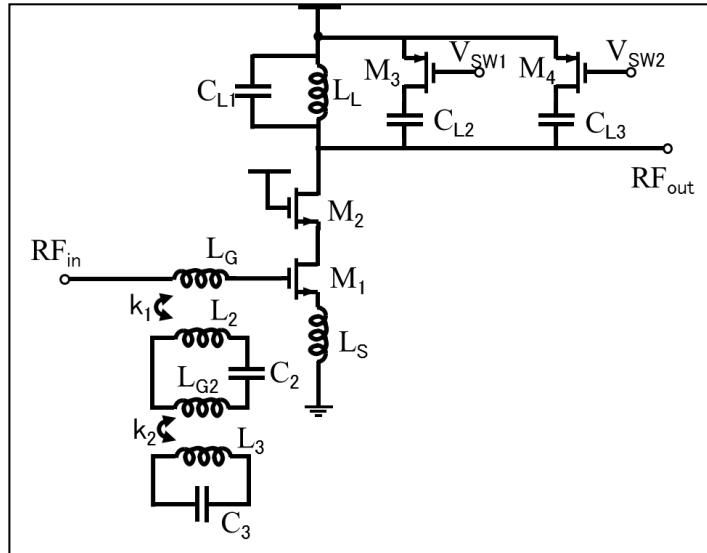


Triple-Band LNA

## Problems

- Area increase
- Noise increases  
(by associated circuits with inductor)

Consider inductor layout  
for solving these problems !!

# Realization of Inductor on chip

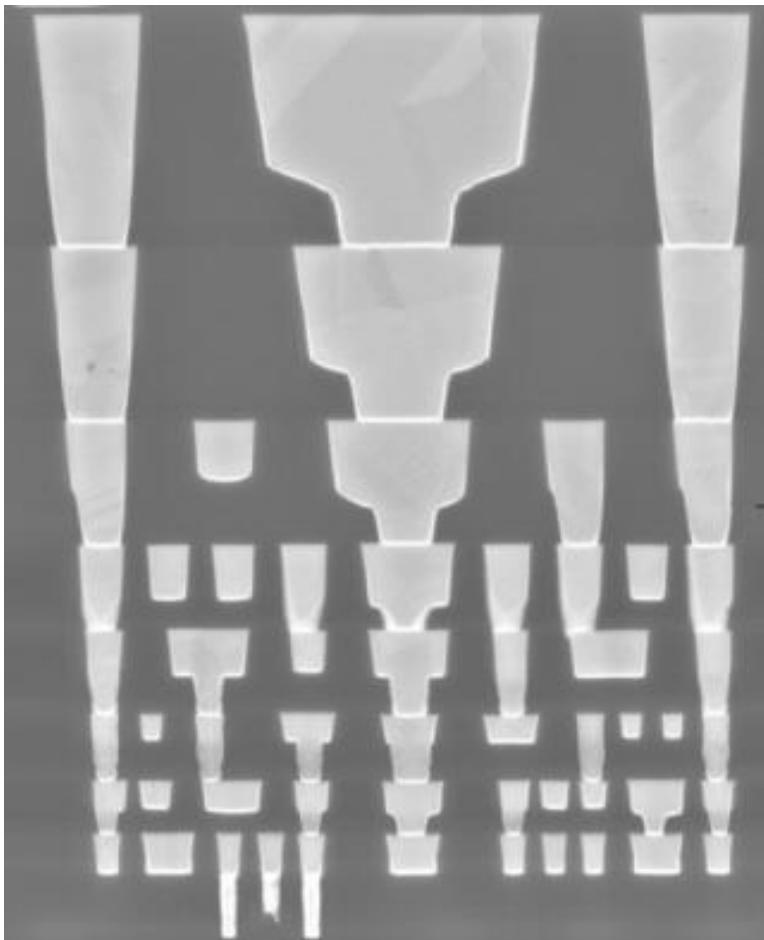

Thick Wiring  
at Top Layer

Inductor is realized in high Q value  
at top layer on chip


( Q value is high,  
inductor's parasitic resistance  
is small)

Section View of LSI

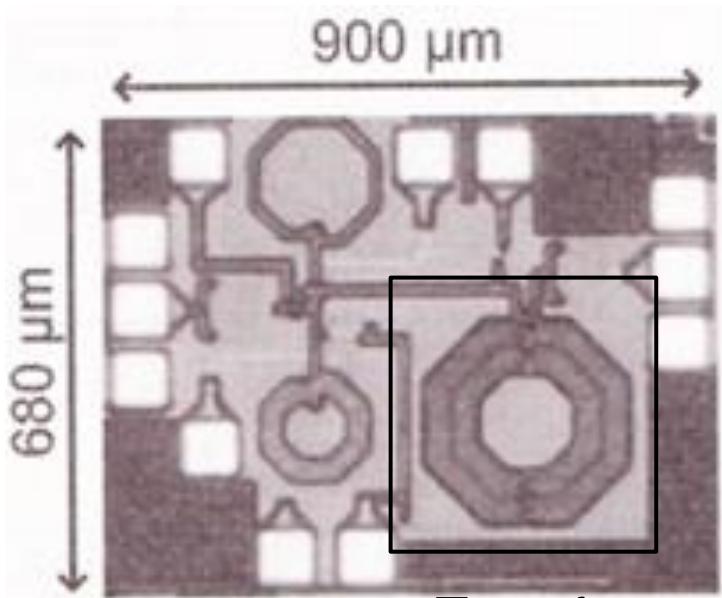
# Consideration of Layout

Schematic diagram of a transformer or inductors

Coupling coefficient is determined  
by shared area of 2 inductors





Implementation of  
Dual-Band LNA

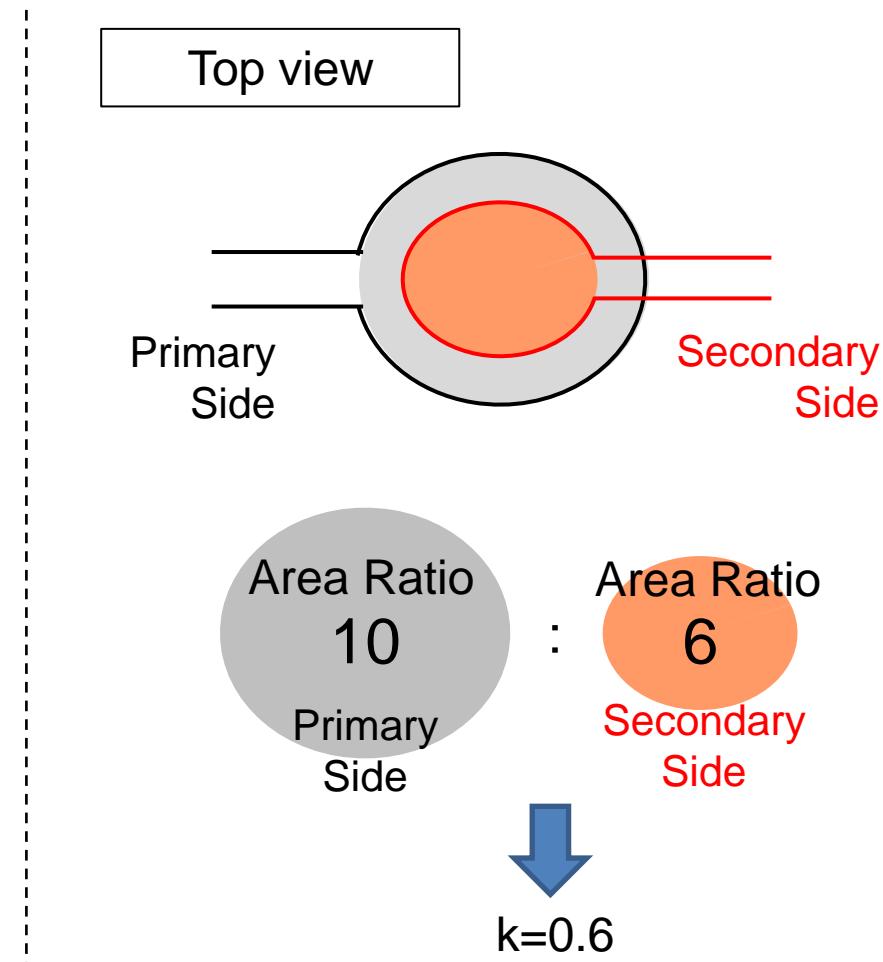



# Consideration of Layout

## Method 1

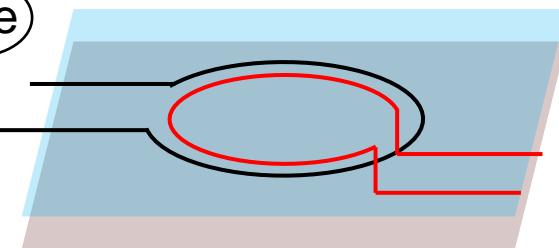
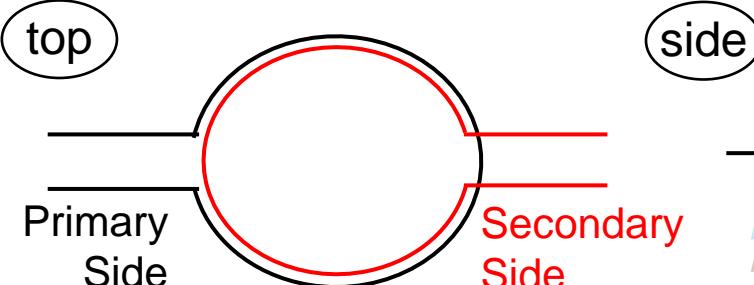


- High Q Value
- Large Area

Third Side

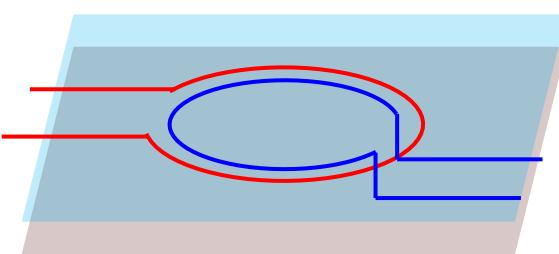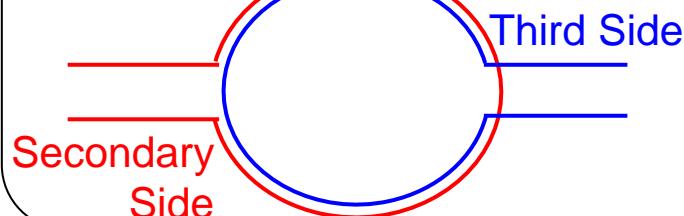


## Method 2

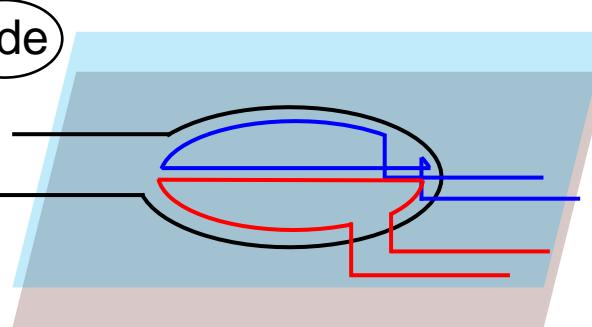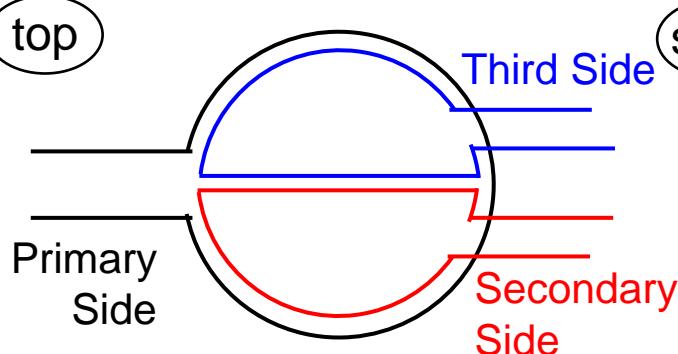


- High Q Value
- Small Area
- Feasible if coupling coefficient is small

# Triple-Band LNA

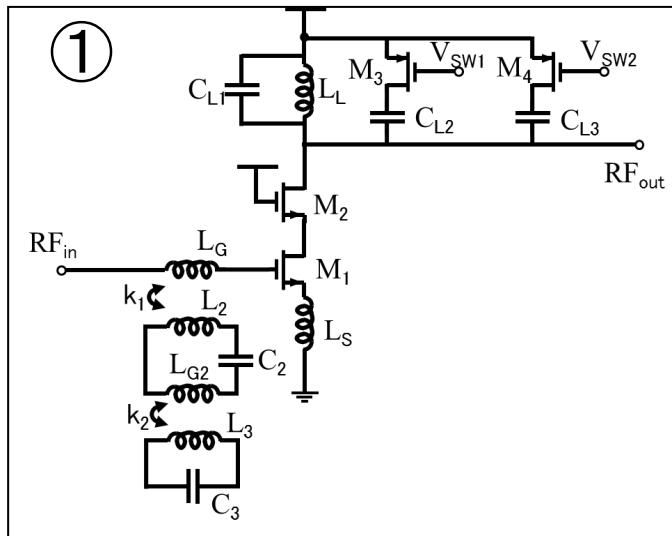

Proposed  
Circuit ①

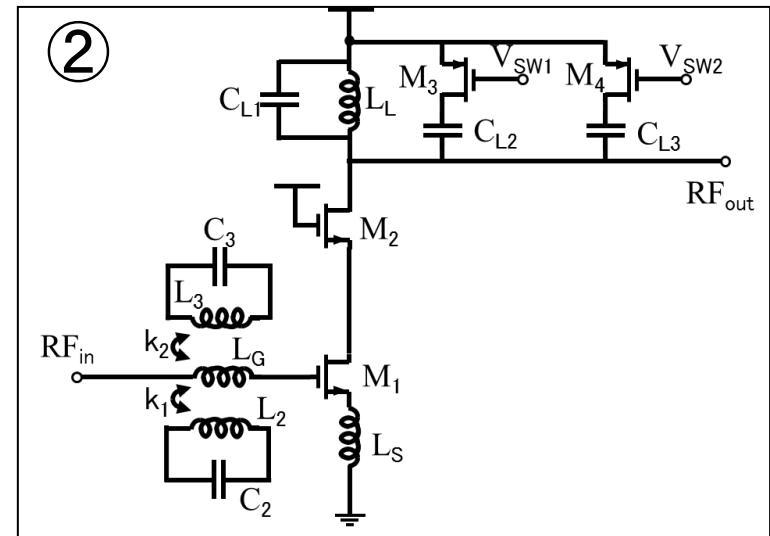


Proposed  
Circuit ②

Design circuits as follows:

- High resonant frequency up to 5 ~ 6GHz
- Area reduction

# Comparison of ① and ②

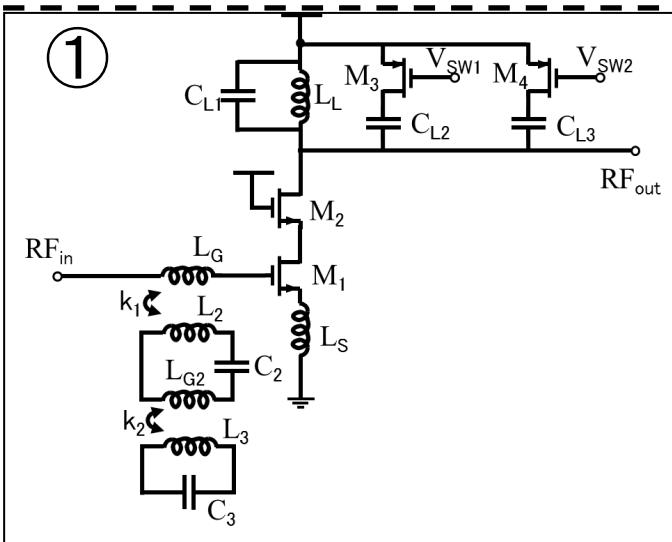

$$\underline{L_G = 8.2\text{nH}}$$

$$\underline{L_2 = 4\text{nH}}$$


$$\underline{L_{g2} = 4\text{nH}}$$

$$\underline{L_3 = 4\text{nH}}$$

$$C_2 = 300\text{fF}$$

$$C_3 = 660\text{fF}$$

$$\underline{k_1 = k_2 = 0.6}$$

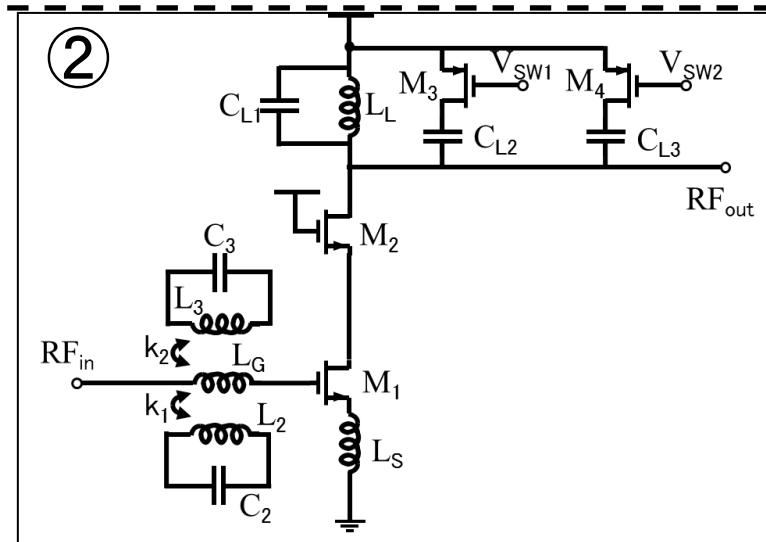

$$\underline{L_G = 4\text{nH}}$$

$$\underline{L_2 = 3\text{nH}}$$



$$\underline{L_3 = 5\text{nH}}$$

$$C_2 = 600\text{fF}$$

$$C_3 = 880\text{fF}$$

$$\underline{k_1 = k_2 = 0.4}$$


**reduce**

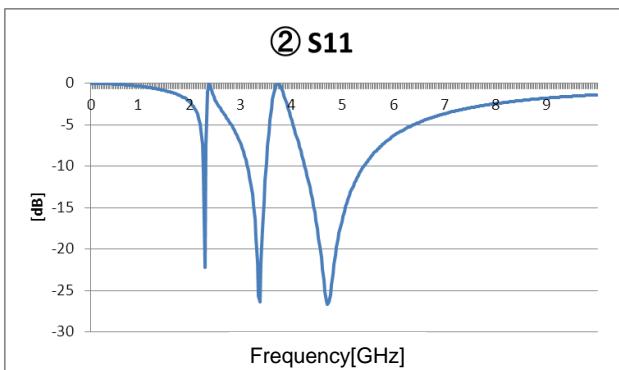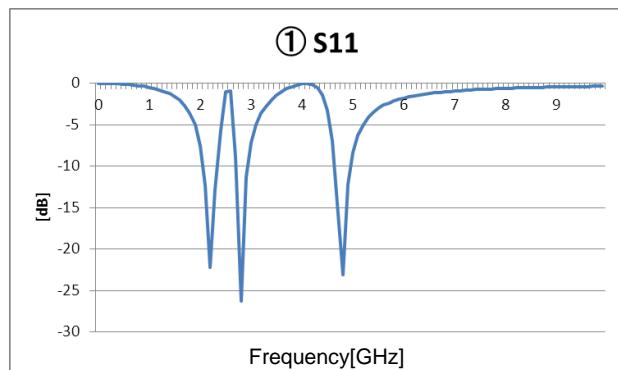

# Comparison of ① and ② Coupling Coefficients


Proposed Circuit ①

$k_1$ :varying  $k_2=0.6$

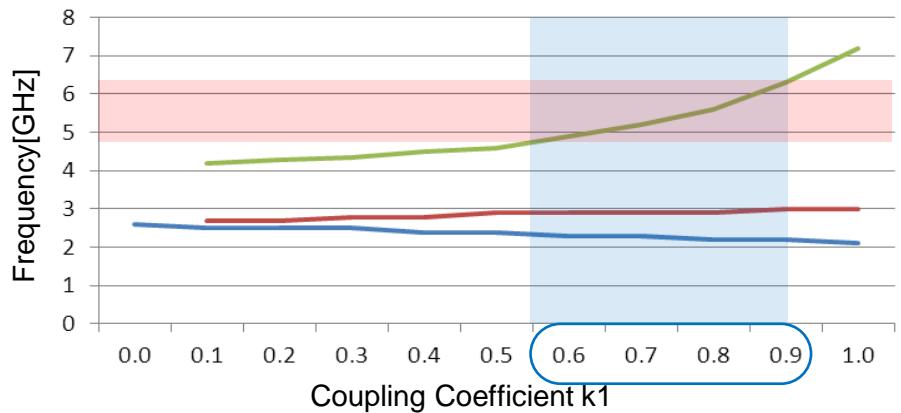


Proposed Circuit ②


$k_1$ :varying  $k_2=0.4$

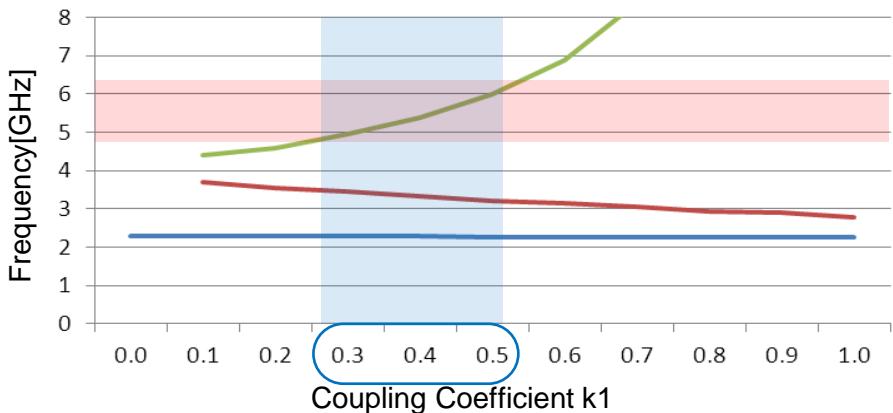

$k_1=0.6$   $k_2$ :varying


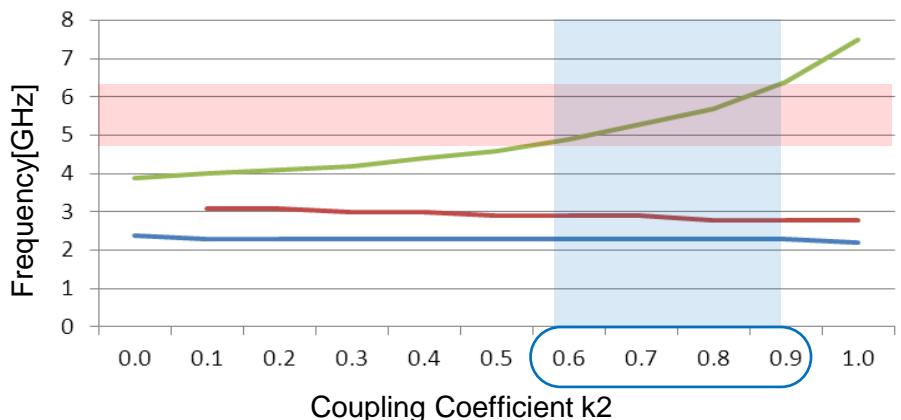


$k_1=0.4$   $k_2$ :varying

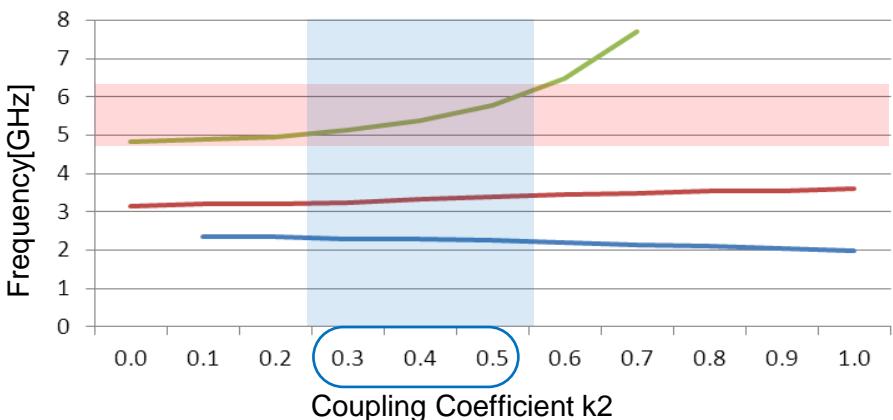

# Triple-Band LNA

Circuit

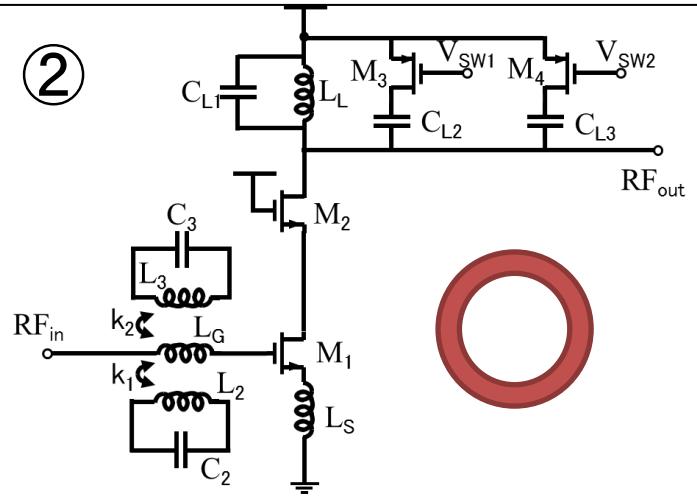
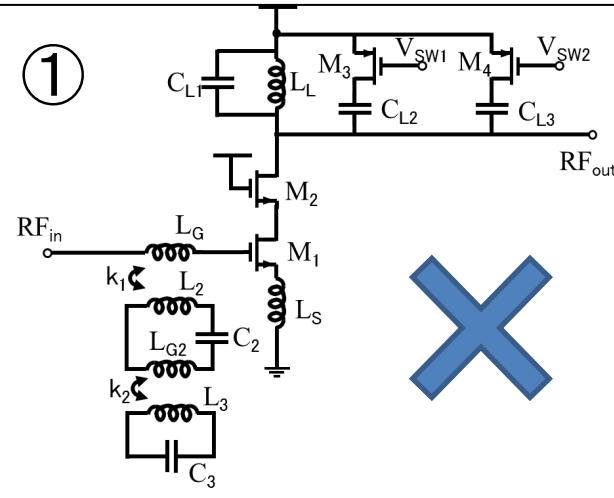


Coupling Coefficient

High  $k$   
 $k_1, k_2=0.6$

Low  $k$   
 $k_1, k_2=0.4$

Transformer Layout (Conceptual Diagram)

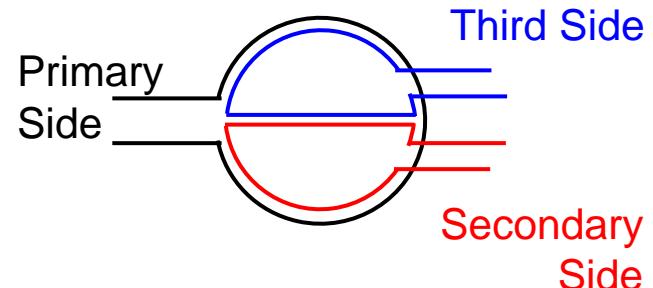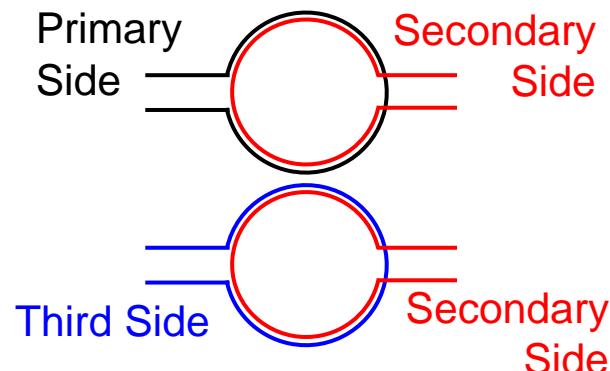

Area

Large Area 😞

Small Area 😊

# Outline

- Research Background & Objective
- Dual Band LNA
  - Circuit Structure & Principle
  - Simulation
- Triple-Band LNA
  - Circuit Structure & Principle
  - Simulation
- Consideration
  - Layout of Inductor & Transformer
- **Conclusion**

# Conclusion

## Conclusion

- Proposed & analyzed Triple-Band LNA
- Showed that proposed Triple-Band LNA circuit ② can meet higher frequency with small area


## Challenge for the future

- Detailed Triple-Band LNA design by electromagnetic field analysis of transformer
- Additional features of higher order multi-band.


# Appendix

---

# About LNA

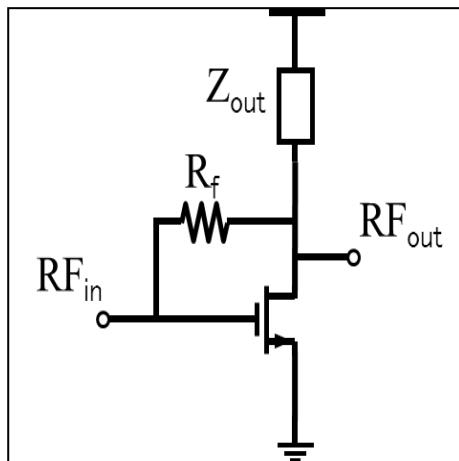

Resistance  
Feedback LNA

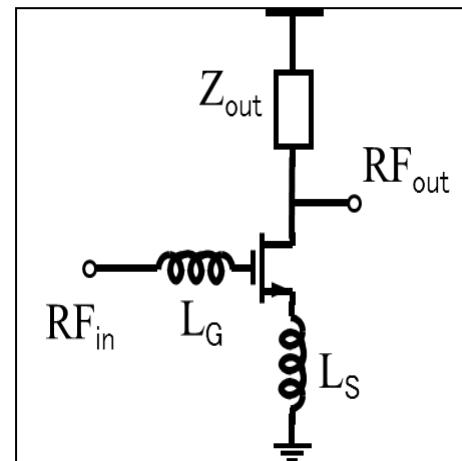

Inductive source  
degeneration LNA

Focused Method

Narrowband ☹

Frequency  
Bandwidth

Wideband ☺

Gain

Low ☹

High ☺




Noise

Bad ☹

Good ☺

# LNA with multiple bands

To include many narrowband in one

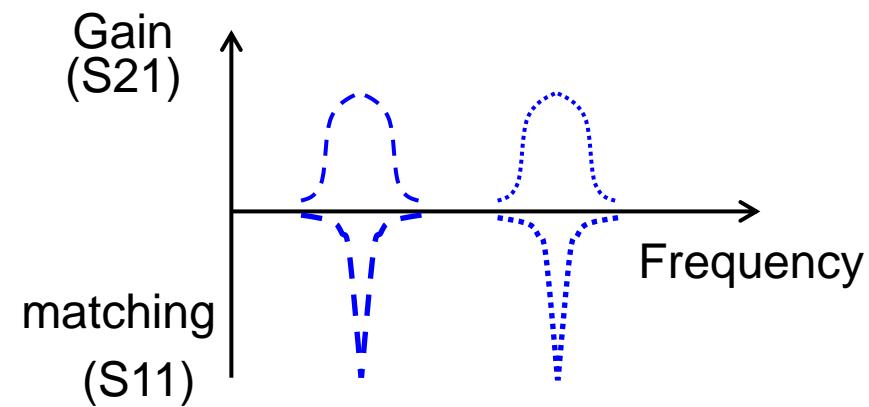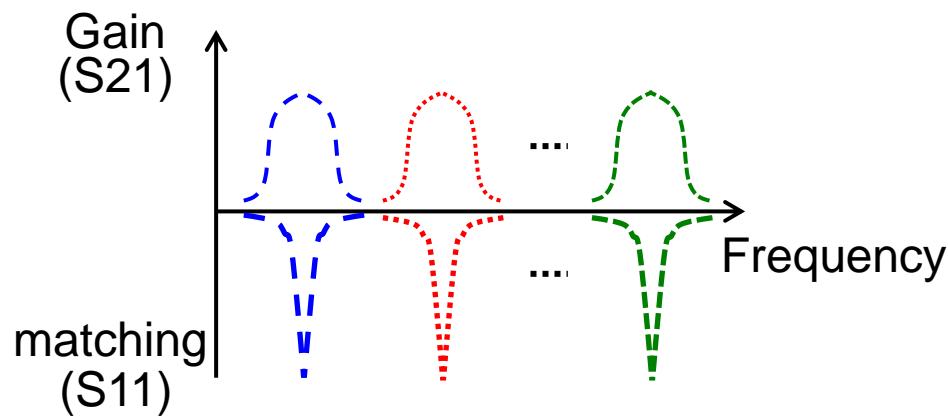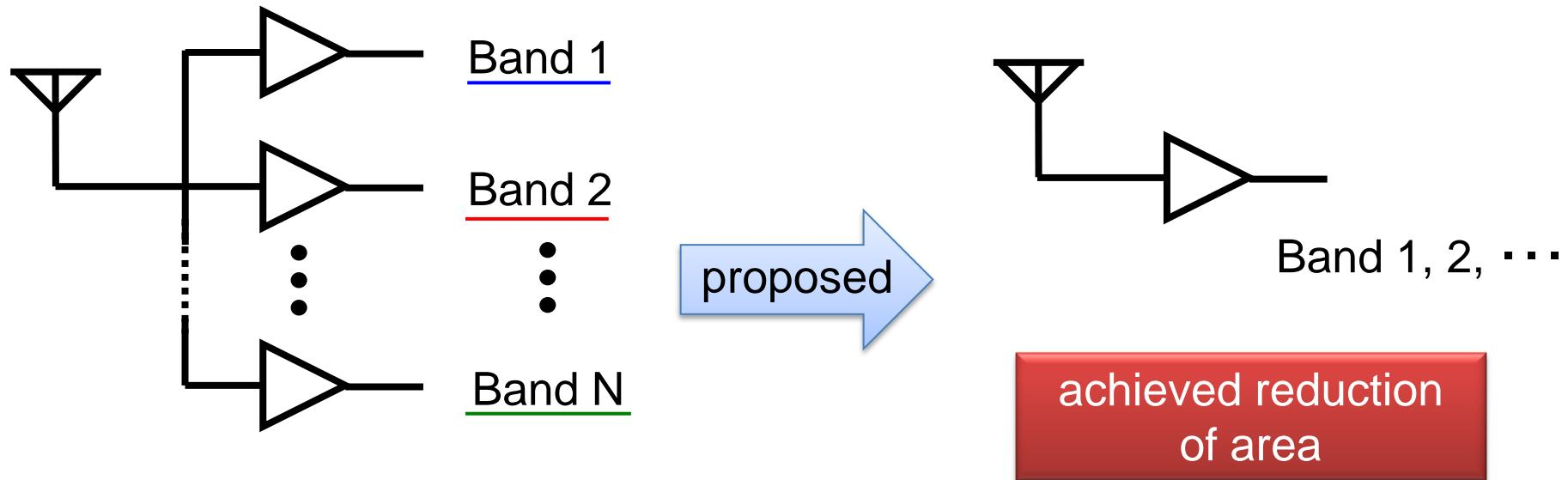

# Questions!

Q.発表資料には、高周波回路の解析に重要なパラメータであるNFについて載っていないのですが、どうですか？

A.論文には載っているのですが、資料には載っていません。  
高周波のマッチング点で約4dBです。

Q.どのようなアプリケーションを見越していますか？

A.携帯用端末の送受信

Q.インダクタの提案をしていますが、EMIシミュレーションはどうですか？

A.EMIシミュレーションはまだしていません。