

**ATS** ATS'18

The 27th IEEE Asian Test Symposium  
Oct.15-18,2018,Hefei,Anhui,China

Oct. 18, 2018

Session 6B-II

Mixed-Signal IC Designs  
and ATE

# Time-to-Digital Converter Architectures Using Two Oscillators With Different Frequencies

Kosuke Machida, Yuki Ozawa, Yudai Abe

Haruo Kobayashi

Gunma University



# Research Objective


Investigation of TDC architectures  
with Verner oscillators

- Analog centric one
  - Using trigger circuits
  - Two oscillators with different frequencies
  - No self-calibration required
- Digital centric one
  - Two ring oscillators  
with different frequencies

- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion


- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion

# Time-to-Digital Converter

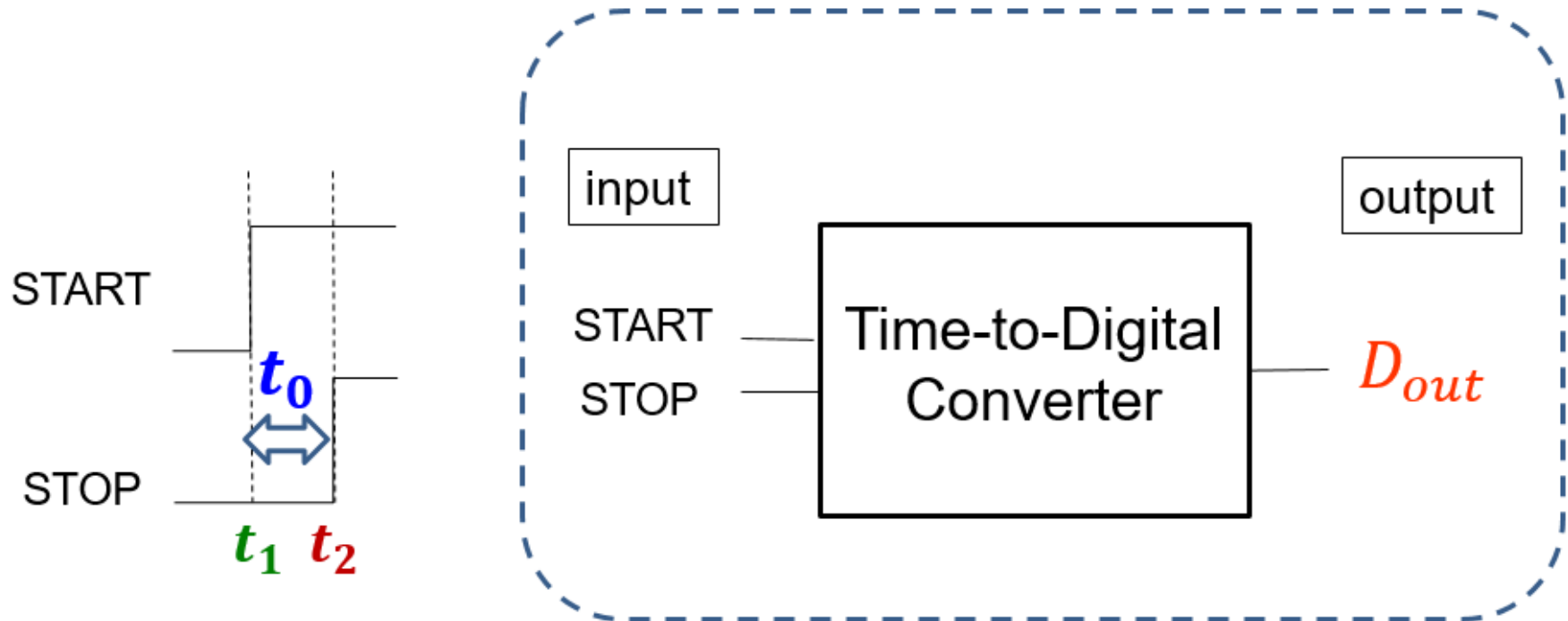

- Time-to-digital converter (TDC) measures **timing difference  $t_0$**  between  $t_1$ ,  $t_2$  as a **digital value  $D_{out}$**

# TDC Application Examples (1)

 


Inter-vehicular distance measurement



Satellite distance measurement

# TDC Application Example (2)

Multi channels

 

Large circuit × Large amounts



High test cost



Small circuit × Large amounts



Low test cost



# Comparison of TDC Architectures

	Conventional TDC	Proposed TDC
Circuit Architecture		
Delay Line	Necessary ☹️	Not necessary 😊
Self Calibration	Required ☹️	Not required 😊

Delay array have **variations** → Self-calibration is required



- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion

# Myth and Truth of Time Signal



## Myth



Voltage can be held



Time difference **cannot** be held

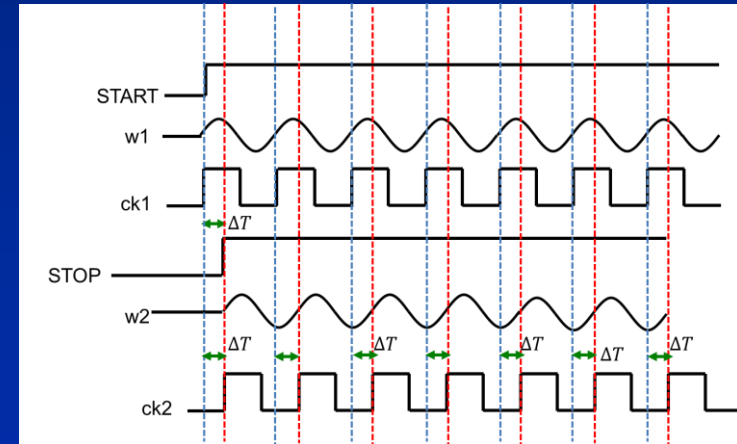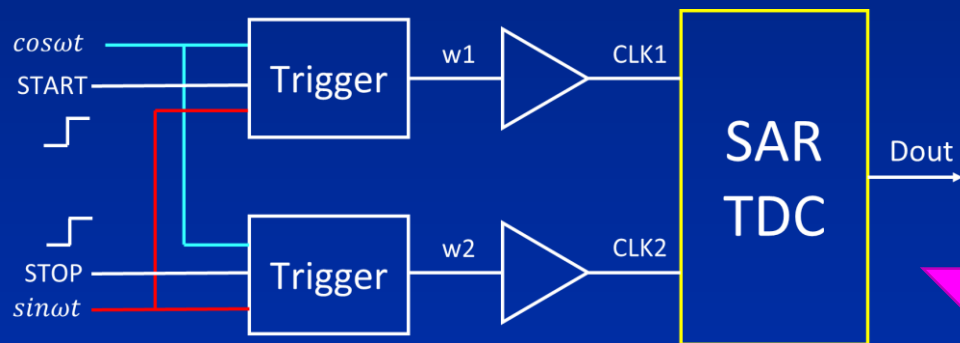


## Truth



Time difference can be held !




# Trigger Circuit

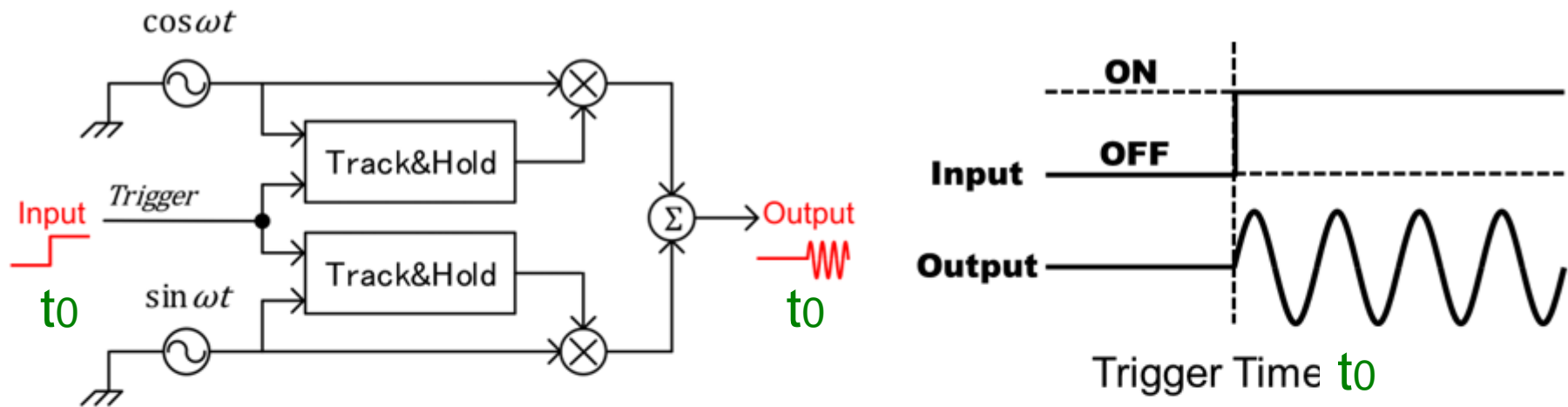


- ❑ Output starts to oscillate at rising timing edge of input
- ❑ Output waveform with no transient change

[1] M. Nelson ([Tektronics](#)) "A New Technique for Low-Jitter Measurements Using Equivalent-Time Sampling Oscilloscope", Automatic RF Techniques Group 56<sup>th</sup> Measurement Conference (Dec. 2000).

# T/H Circuit

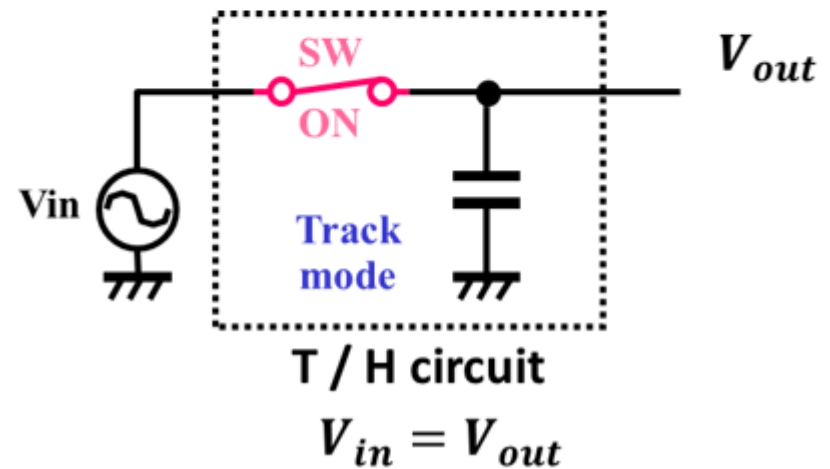  

# Trigger Circuit Waveforms

 

T/H circuit


## • track mode

$$\begin{aligned} V_{out} &= \cos(\omega t) \cos(\omega t) + \cos(\omega t + \pi/2) \cos(\omega t + \pi/2) \\ &= \cos^2(\omega t) + \sin^2(\omega t) \\ &= \underline{1} \end{aligned}$$

## • hold mode

$$\begin{aligned} V_{out} &= \cos(\omega t) \cos(\omega t_0) + \sin(\omega t) \sin(\omega t_0) \\ &= \underline{\cos(\omega(t - t_0))} \end{aligned}$$


⊗ **trigger time:  $t_0$**

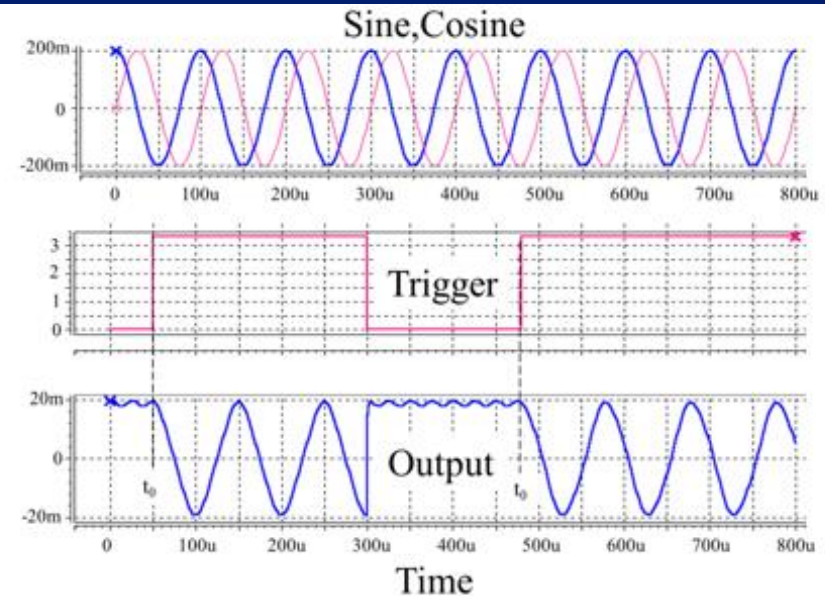


# One-shot Timing Measurement Using Trigger Circuit

## Proposal

Input START, STOP signal

 

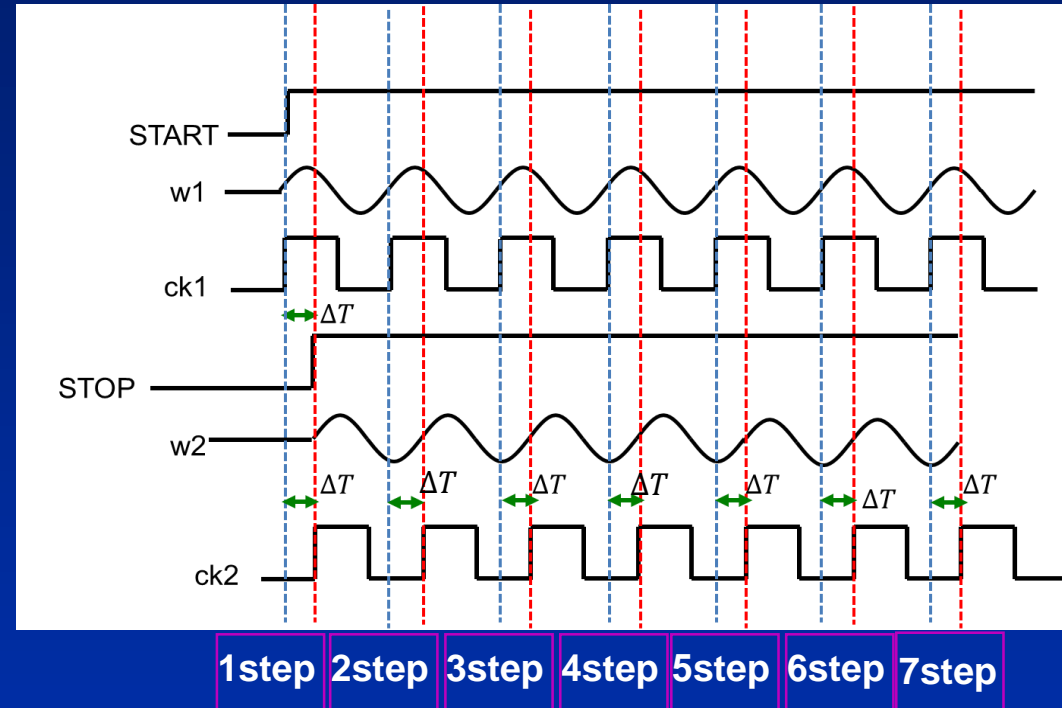Oscillate with initial phase at input timing




It can **hold the time difference** using two trigger circuits

# SAR-ADC VS. SAR-TDC

## SAR ADC :


- Comparator
- DAC

 

SAR-ADC

## SAR TDC :



- D-FF
- Delay line

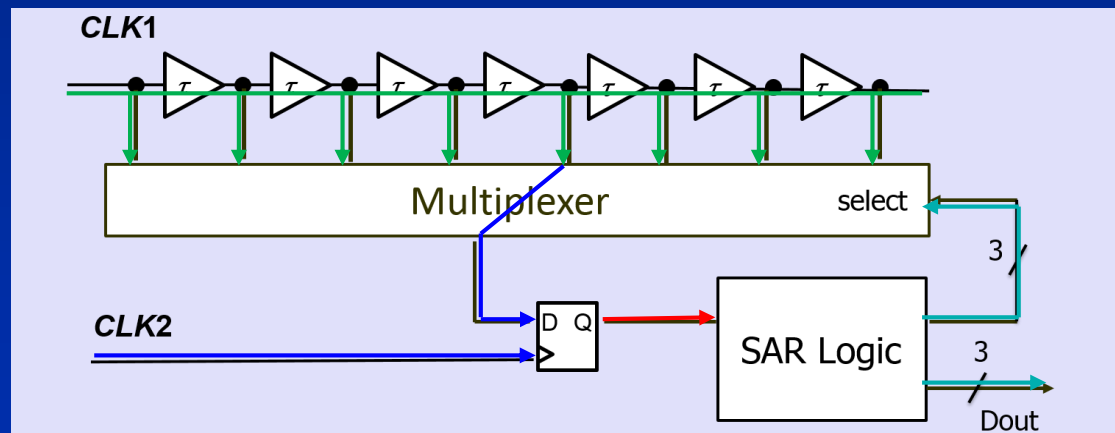

Y. Ozawa, H. Kobayashi, et. al.,  
 "SAR TDC Architecture with Self-Calibration Employing Trigger Circuit,"  
 IEEE Asian Test Symposium, Taipei (Nov. 2017).


# SAR TDC Operation

## STEP1

  

Example



$$\Delta T = 4.3 \tau$$

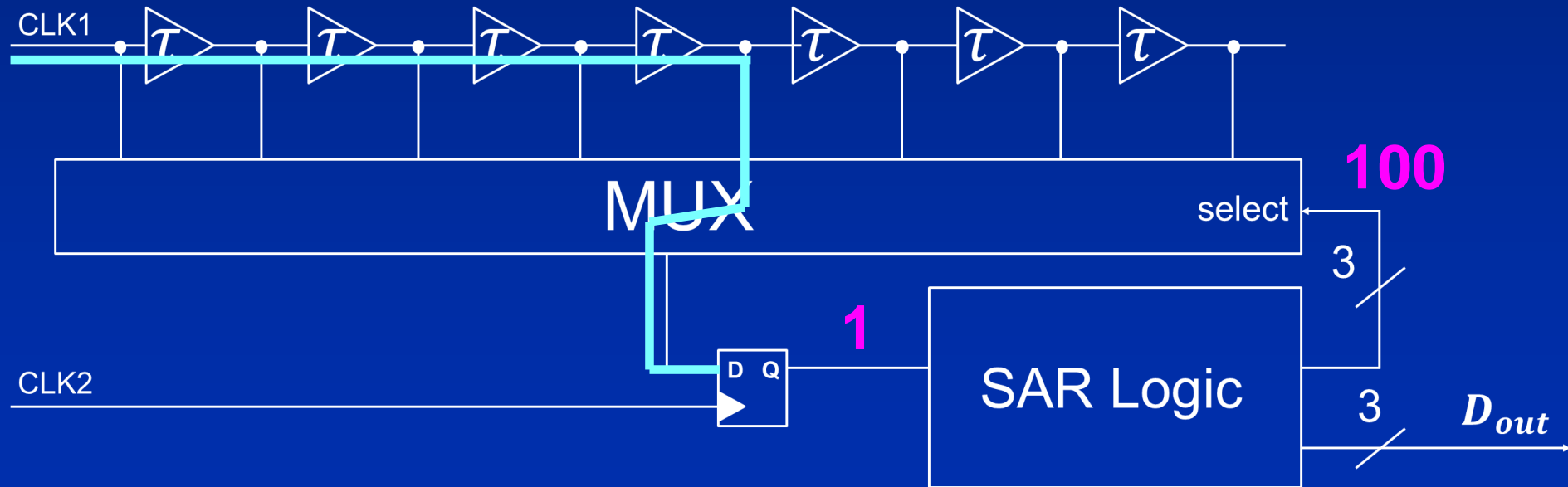




# SAR TDC Operation

## STEP2

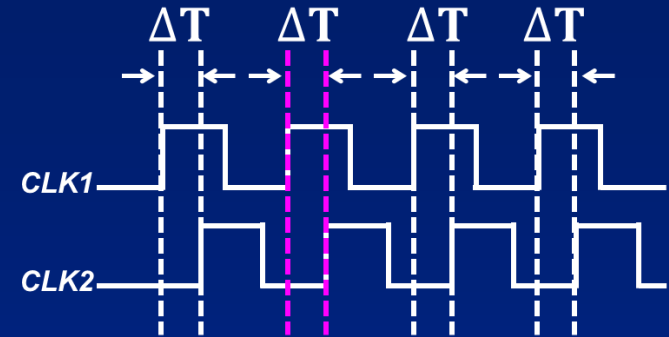 



Example

$$\Delta T = 4.3 \tau$$

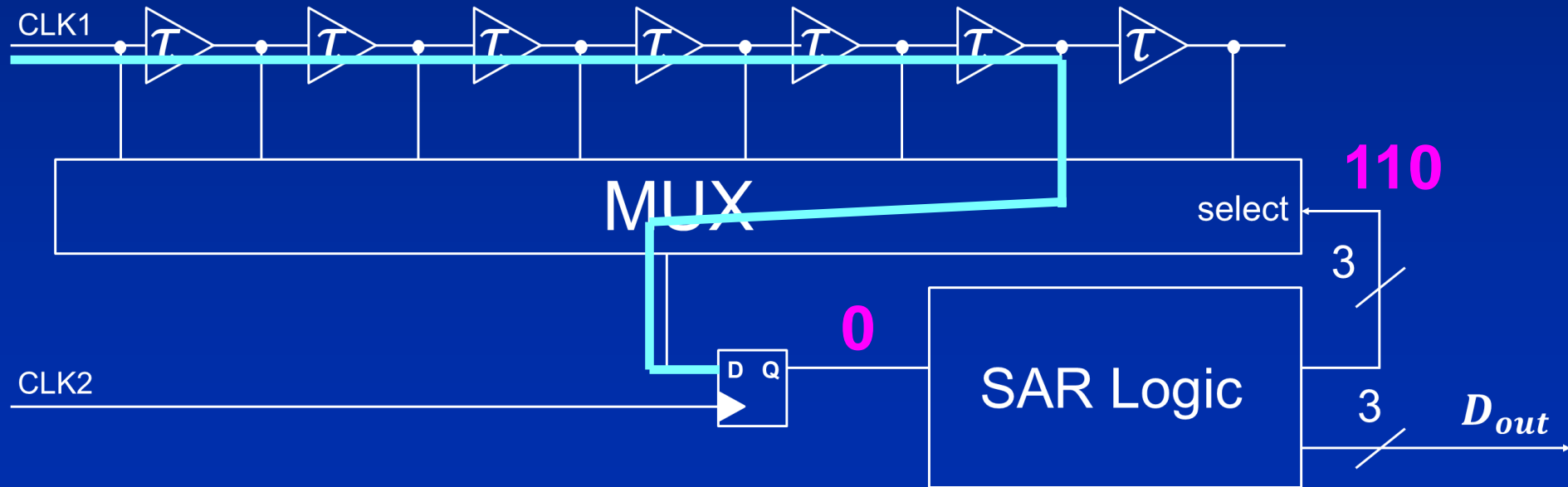


# SAR TDC Operation

## STEP3

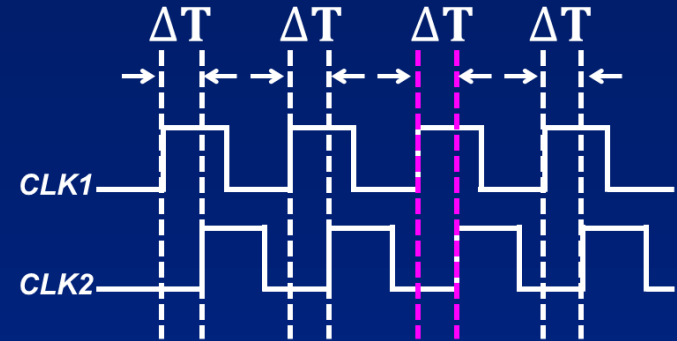 



Example

$$\Delta T = 4.3 \tau$$

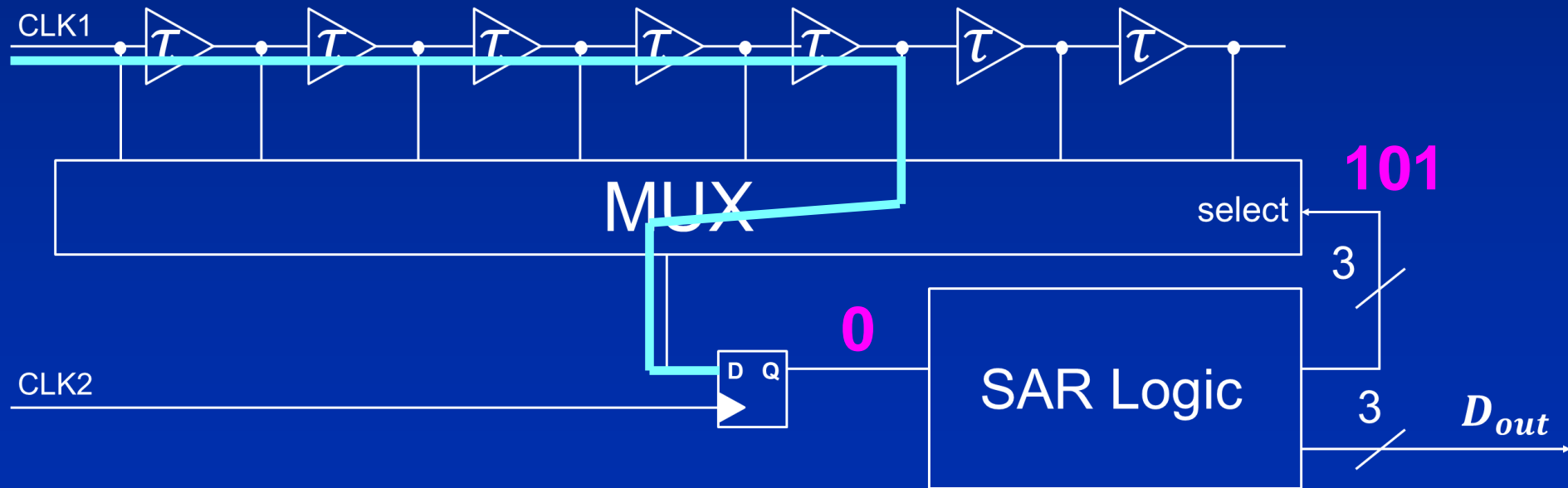


# SAR TDC Operation

## STEP4 (Stable)

 
 


Example

$$\Delta T = 4.3 \tau$$

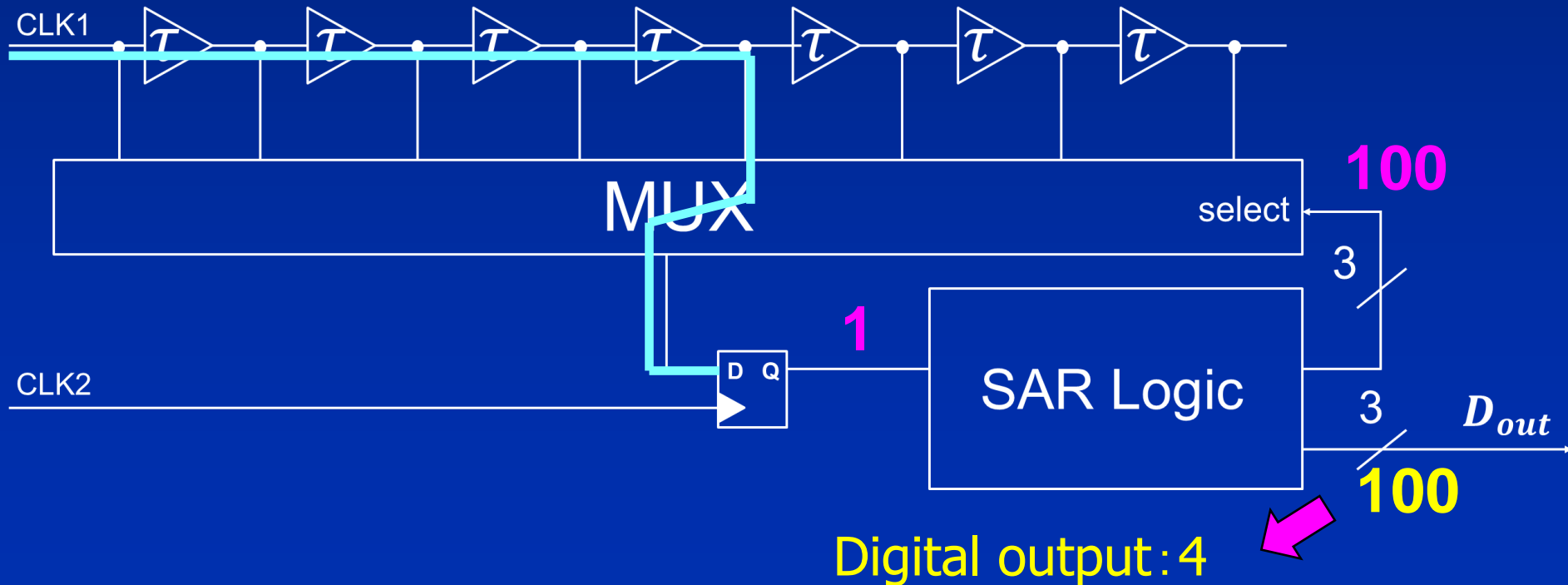


# Low Frequency Clock Measurement

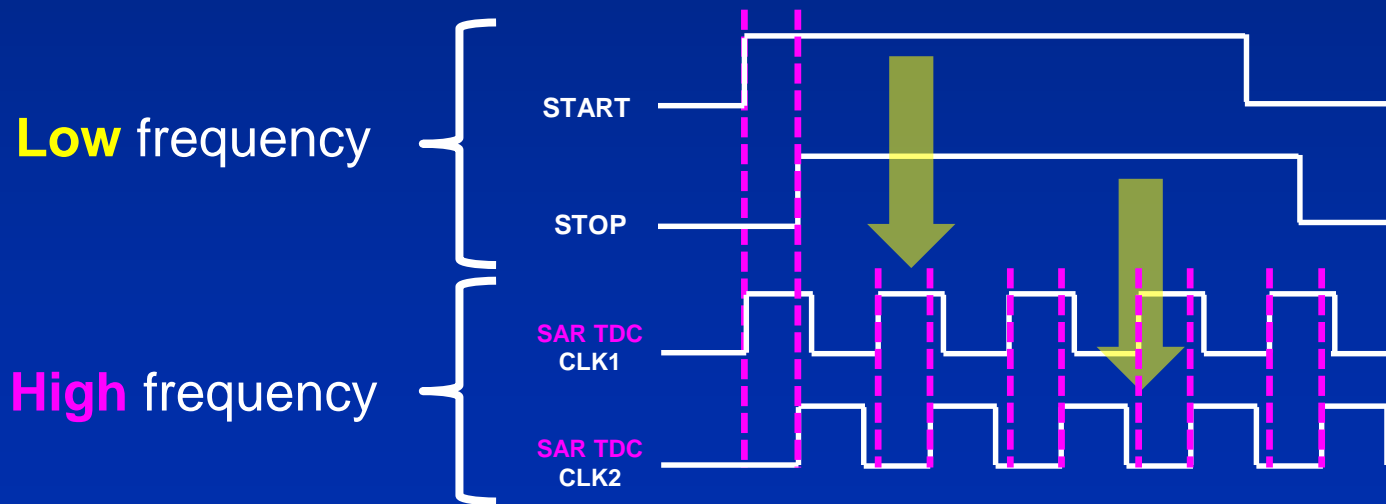 

Short testing time for low frequency repetitive timing

# Verner Oscillation TDC


What about using different frequencies ?

 


$f_1$ : known

$f_2$ : known

 Start oscillation  $f_1$  at START edge  
 $f_2$  at STOP edge



# Verner Oscillation TDC Operation

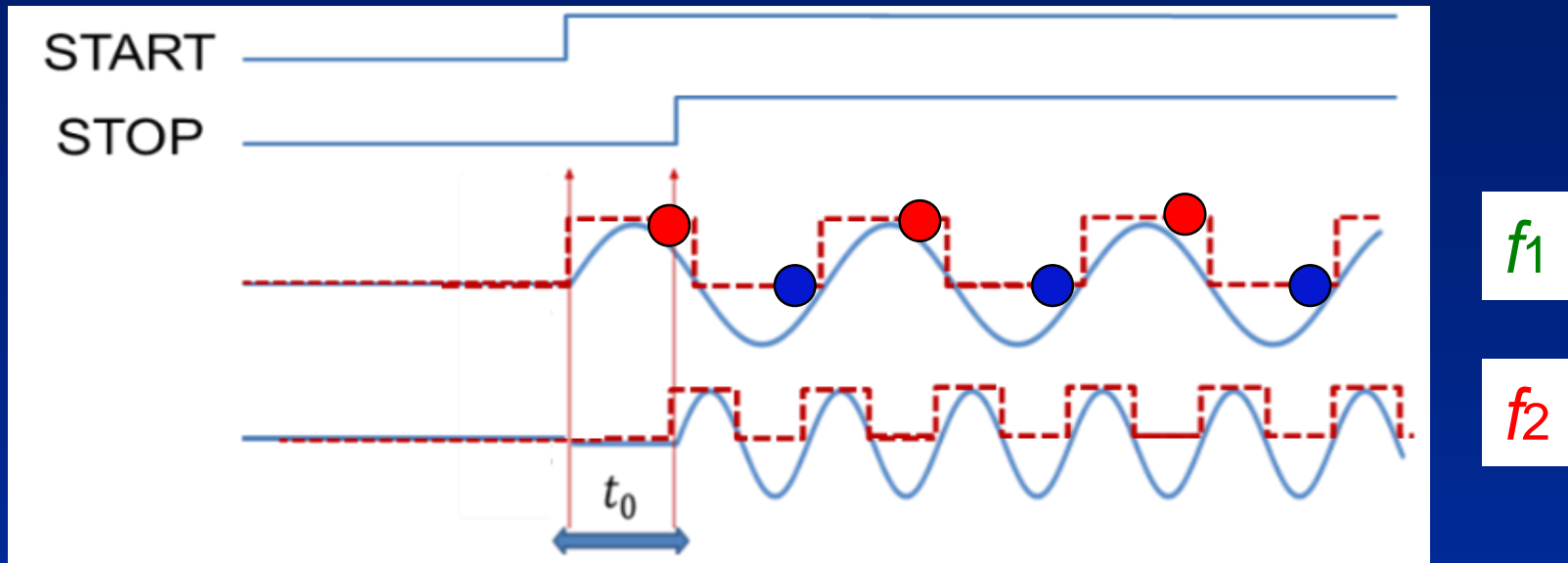


$$t_0 = f(f_1, f_2, \text{number of } \bullet, \bullet \dots, \text{number of } \bullet, \bullet \dots)$$

$$f_1 \doteq f_2$$

Time  
resolution

$$t' = \left| \frac{1}{f_2} - \frac{1}{f_1} \right|$$
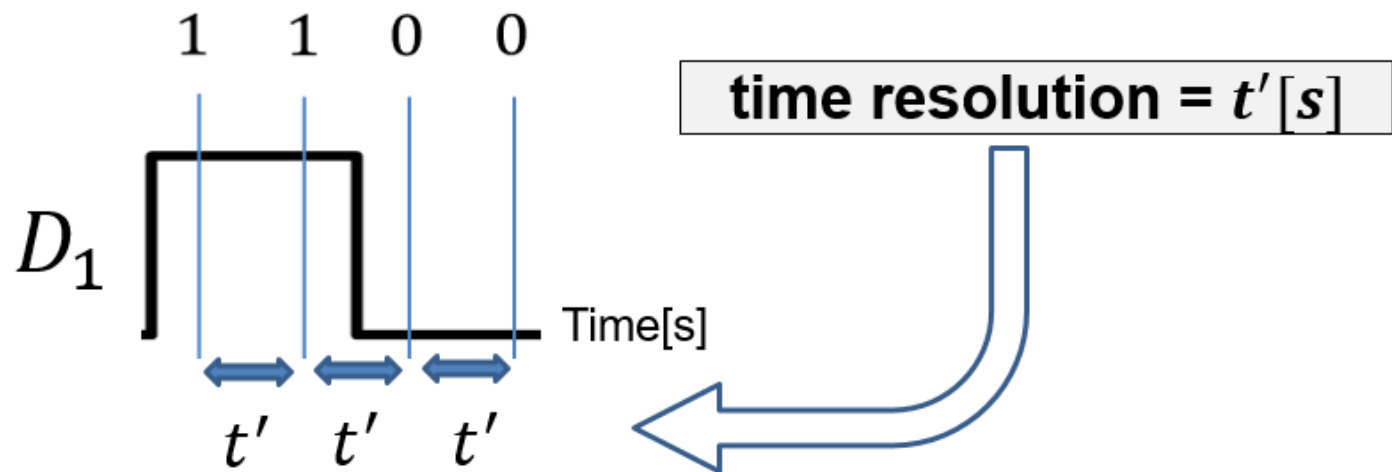
# Usage of Different but Close Frequencies



Different Frequencies

$$t' = \left| \frac{1}{f_2} - \frac{1}{f_1} \right| \quad \begin{array}{l} f_1 = 1[\text{MHz}] \\ f_2 = 0.9999[\text{MHz}] \end{array}$$


$$t' \cong 1 \times 10^{-10} [\text{s}]$$

Equivalent  
Sampling

$$f_1 \doteq f_2$$

Different frequencies → **Fine time resolution** ↔ **Long measurement time**  
Trade off

# Design Tradeoff

 

$f_1$

$f_2$

Fine time resolution

$$t' = \left| \frac{1}{f_2} - \frac{1}{f_1} \right|$$

$$T_{in} = 1/f_1, 1/f_2$$

$$T_{meas} = T_{in} \times T_{in} / t'$$


Wide input time range

Long Measurement time




- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion

# Proposed TDC Architecture


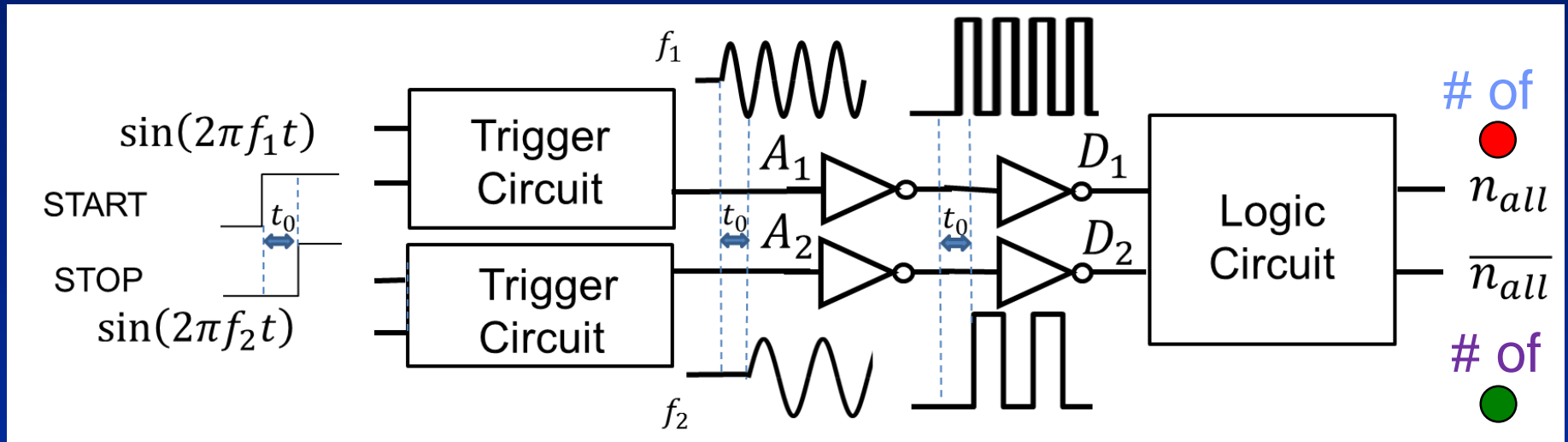


$f_1$ : known


$f_2$ : known

 


# Logic Circuit for Time Measurement

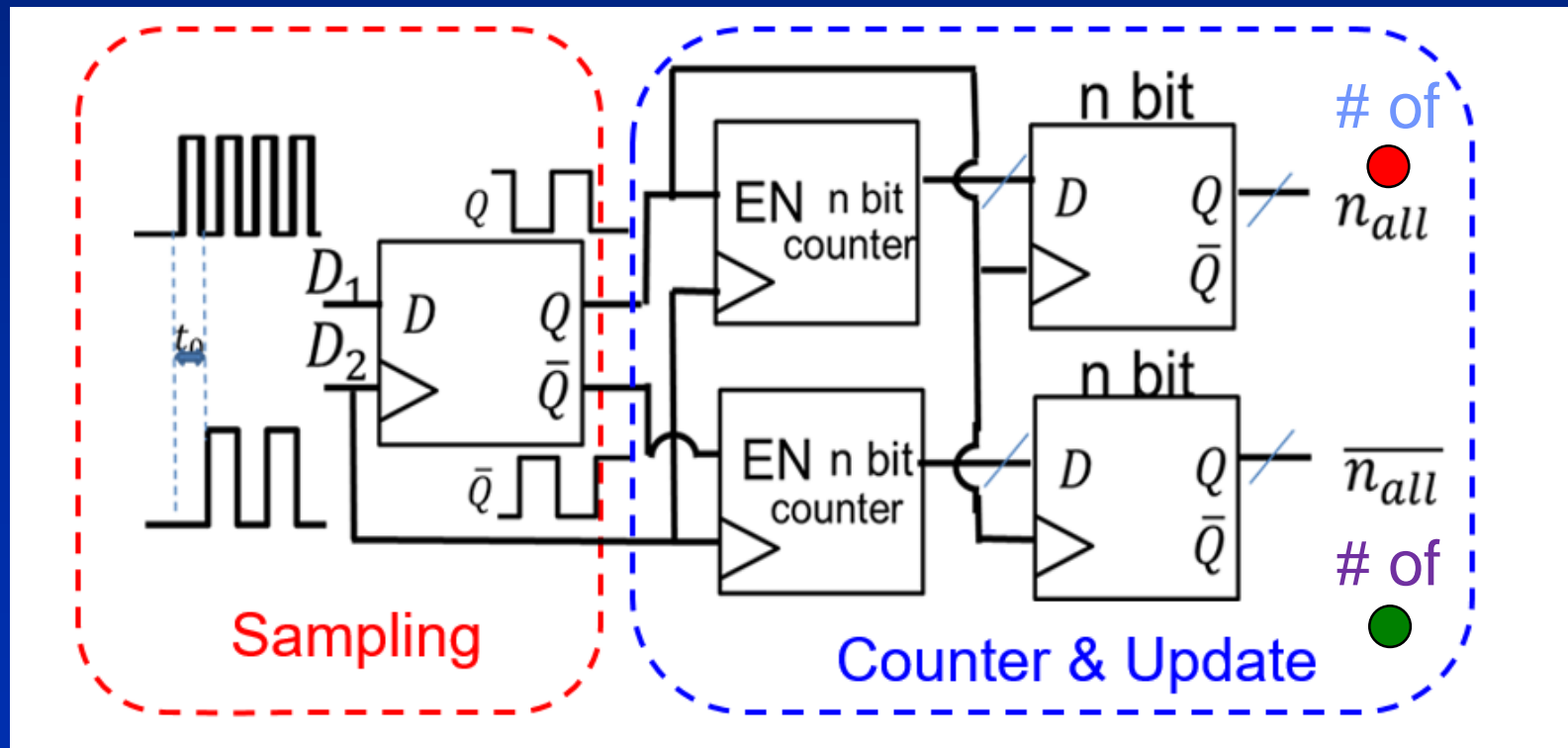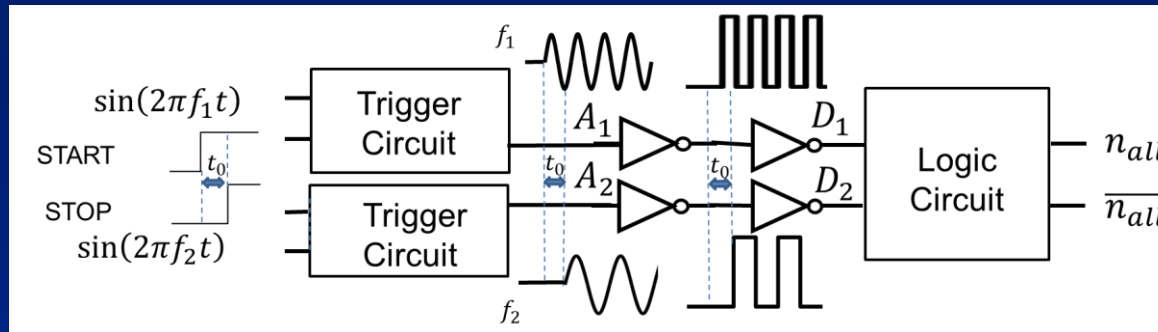


# D1 Sampling by D2

 


input

 

clock

 




output

 

$$n_{all}(= n_1 + n_2 \dots) \quad \overline{n_{all}}(= \overline{n_1} + \overline{n_2} \dots)$$



$$n_{beat} = n_2 + \overline{n_2} = n_3 + \overline{n_3} = \dots = \frac{f_2}{|f_2 - f_1|}$$

# Counter & Update

  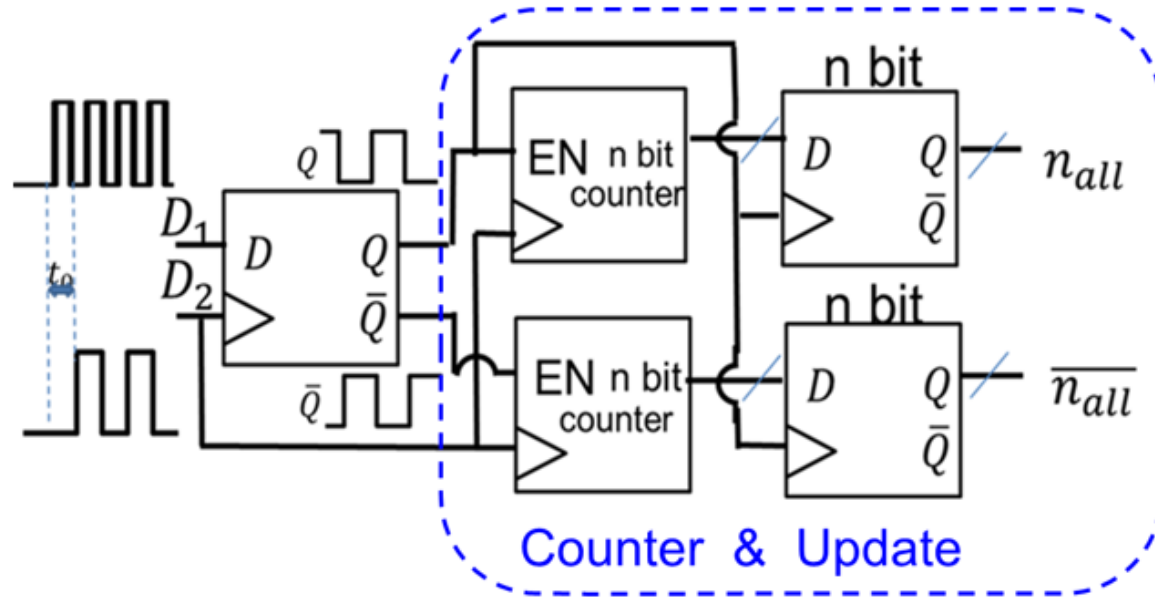

# Deviation Points by Time Difference


- Timing difference  $t_0$  generates **deviation**

  (a)  $f_1 > f_2$ (b)  $f_1 < f_2$ 



$$\text{deviation} = \begin{cases} (\overline{n_{all}} - n_{all}) & \text{(in case } f_1 > f_2) \\ \{n_{beat}/2 - (\overline{n_{all}} - n_{all})\} & \text{(in case } f_1 < f_2) \end{cases}$$
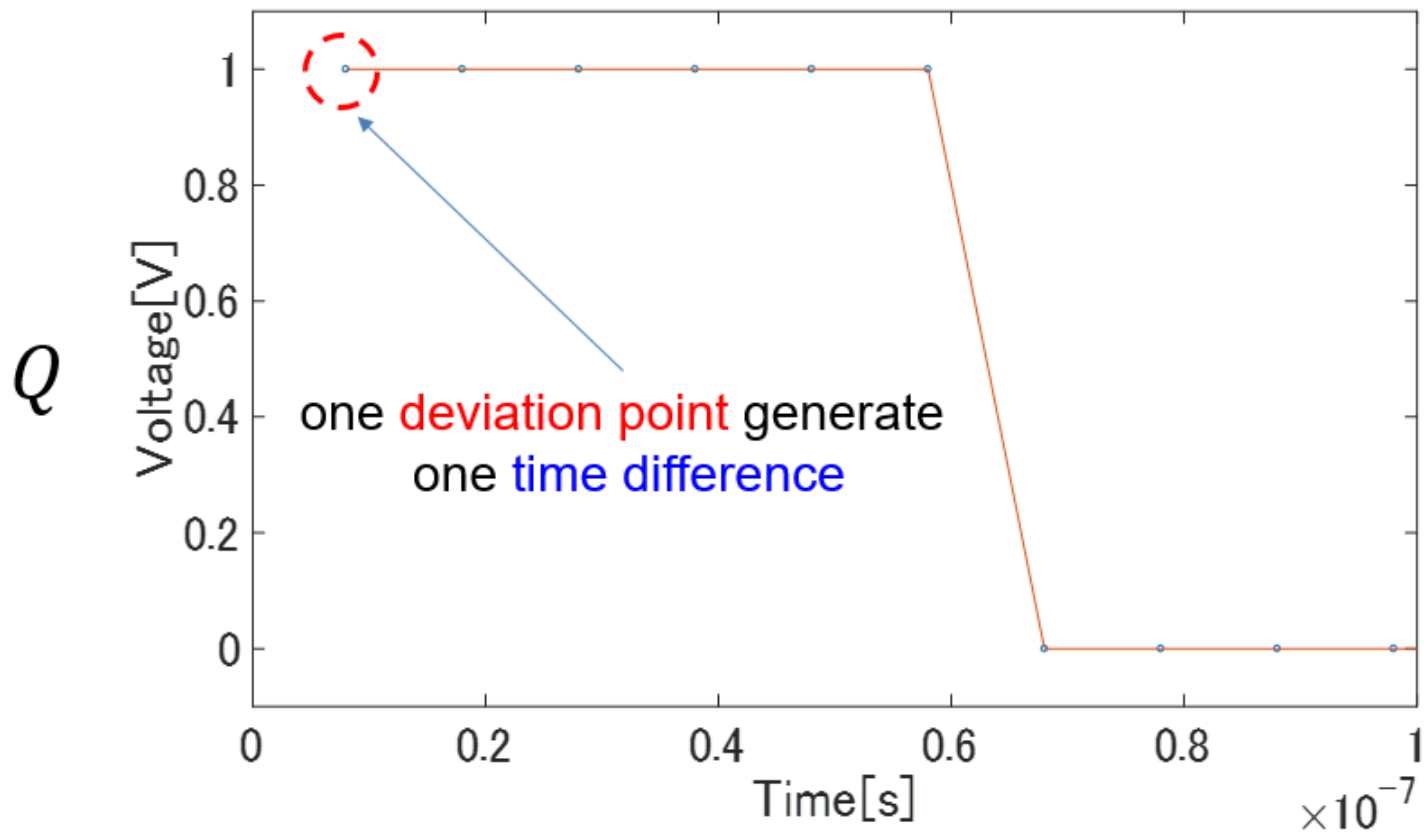
# Deviation and Time Resolution

$$t_0 = \begin{cases} (\overline{n_{all}} - n_{all})t' & \text{(in case } f_1 > f_2) \\ \{n_{beat}/2 - (\overline{n_{all}} - n_{all})\}t' & \text{(in case } f_1 < f_2) \end{cases}$$



# Equivalent Time Sampling

  


Sampling  $D_1$  by clock  $D_2$

$$t' = \left| \frac{1}{f_2} - \frac{1}{f_1} \right|$$


$$t' = 1/f_2$$

(in case  $f_1 \ll f_2$ )

 

**Fine time resolution**

(in case  $f_1 \approx f_2$ )

 


**Coarse time resolution ?**



# Waveform Reconstruction

(in case  $f_1 \approx f_2$ )

 


overlap

Sampled points  
rearrangement

(in case  $f_1 \ll f_2$ )

**Fine  
time resolution**


**High** frequency  
operation

 

(in case  $f_1 \approx f_2$ )


**Fine  
time resolution**

**Low** frequency  
operation

 
 
# Measurement Time Resolution



After overlap (in case  $f_1 \approx f_2$ )





Time resolution =  $t'$

$$t' = \left| \frac{1}{f_2} - \frac{1}{f_1} \right| = \left| \frac{f_1 - f_2}{f_1 f_2} \right| \quad \Rightarrow \quad \lim_{f_1 \rightarrow f_2} t' = \text{Fine time resolution}$$

# Proposed TDC Linearity

  

Low Linearity

  



High Linearity

# Simulation Verification of Proposed TDC

## ◆ Simulation Conditions

$$f_1 = 99[\text{MHz}], f_2 = 100[\text{MHz}], t_0 = 1[\text{ns}]$$

## ◆ SPICE Simulation Results

 
 


At 5[ $\mu\text{s}$ ]  $n_{all} = 210$ ,  $\overline{n_{all}} = 250$


⇒  $t_0 = 1.01[\text{ns}]$  Error is **1**[%]

- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion

# Ring Oscillator with Start

  

# Digital Centric TDC

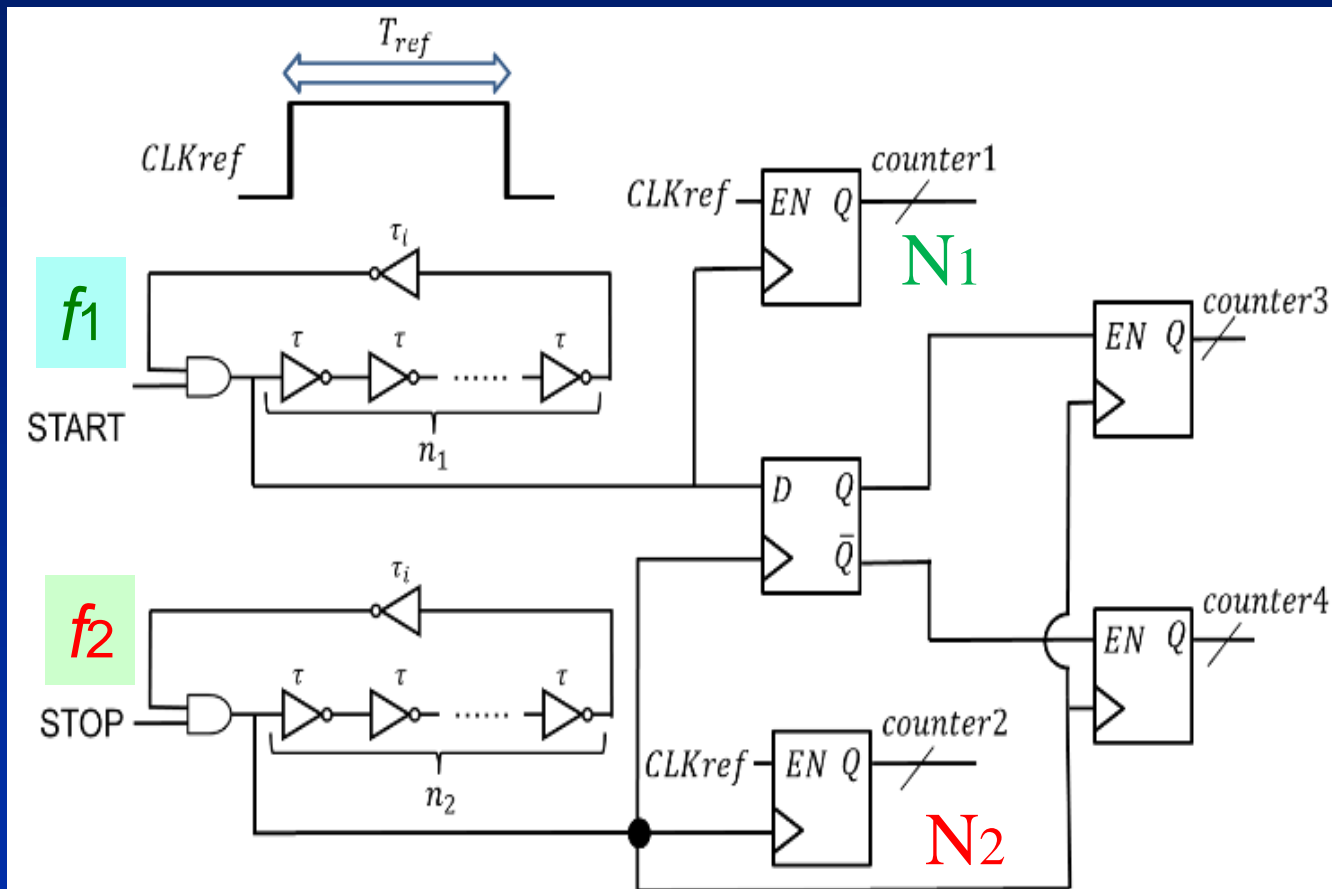

## Ring oscillator frequencies

$f_1 \doteq$  Counter 1 output  $N_1$  / reference time  $T_{ref}$

$f_2 \doteq$  Counter 2 output  $N_2$  / reference time  $T_{ref}$

- Research Background
- Measurement Principle
- Analog Centric TDC
- Digital Centric TDC
- Discussion & Conclusion



# TDC Architecture Comparison

	Clocks Under Test	Measurement Time	Time Resolution	Circuit	FPGA	
Flash-type	Single event ○	Short ○	Coarse ✖	Large ✖	Digital ○	
Gray code based	Single event ○	Short ○	Coarse ✖	Small ○	Digital ○	
SAR-type	Repetitive clock △	Middle △	Middle △	Small ○	Digital ○	
Delta-Sigma type	Repetitive clock △	Long ✖	Fine ○	Small ○	Small Analog △	
Integral type	Single event ○	Long ✖	Fine ○	Small ○	Small Analog △	Oscillators
Verner Oscillator	Single event ○	Long ✖	Fine ○	Small ○	Small Analog △	Oscillators



Excellent



Good



Bad

# Comparison of Time and Voltage

- Dynamic range of time domain signal can be infinite.
- Time flows in one direction.
- Ring oscillator can be often used for time domain signal processing.
- Exact frequency division is possible, whereas exact voltage division is difficult.
- Frequency is a stable signal.
- Jitter is a difficult problem.
- Time as well as voltage can be held.
- Time as well as voltage can be amplified.
- New TDC architectures can be inspired by existing ADC architectures.

# Conclusion

- Verner Oscillator TDC architectures
  - Analog centric and digital centric ones
  - Using two oscillators with different frequencies

➔ Can be shared among multi-channel TDCs

- No delay line
- No self-calibration required
- Design tradeoff

Measurement time

Time resolution

Input time range

# Time is very important !

光阴似箭

Effective executives know that time is the limiting factor of the other resources.






Peter Drucker

# Appendix : N-Stage Trigger Circuit

S. Sakurai, H. Kobayashi, et. al.,  
"Study OF Multi-Stage Oscilloscope Trigger Circuit,"  
IEEE ISPACS, Xiamen, (Nov. 2017)

# Three-stage Trigger Circuit

  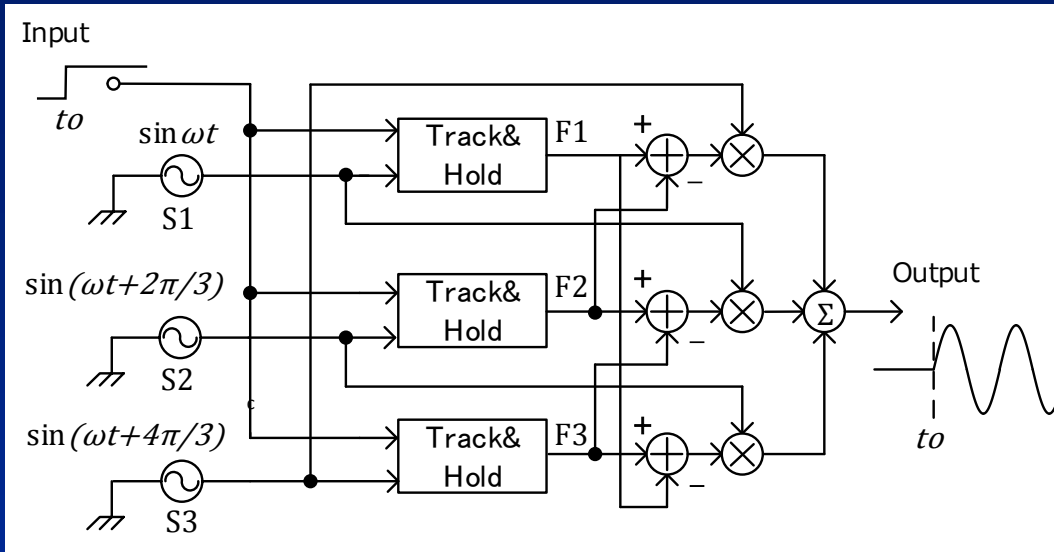

# Analysis of Three-stage Trigger Circuit

Signal source

$$S_1 = \sin \omega t, S_2 = \sin \left( \omega t + \frac{2\pi}{3} \right), S_3 = \sin \left( \omega t + \frac{4\pi}{3} \right)$$

Triggered T/H circuit output

$$F_1 = \sin \omega t_0, F_2 = \sin \left( \omega t_0 + \frac{2\pi}{3} \right), F_3 = \sin \left( \omega t_0 + \frac{4\pi}{3} \right)$$


• Track mode

$$\begin{aligned} V_{o_{track}} &= S_1(S_2 - S_3) + S_2(S_3 - S_1) + S_3(S_1 - S_2) \\ &= 0 \quad \text{(Constant)} \end{aligned}$$

• Hold mode

$$\begin{aligned} V_{o_{hold}} &= S_1(F_2 - F_3) + S_2(F_3 - F_1) + S_3(F_1 - F_2) \\ &= \frac{3\sqrt{3}}{2} \sin(\omega(t - t_0)) \end{aligned}$$

# N-Stage Trigger Circuit

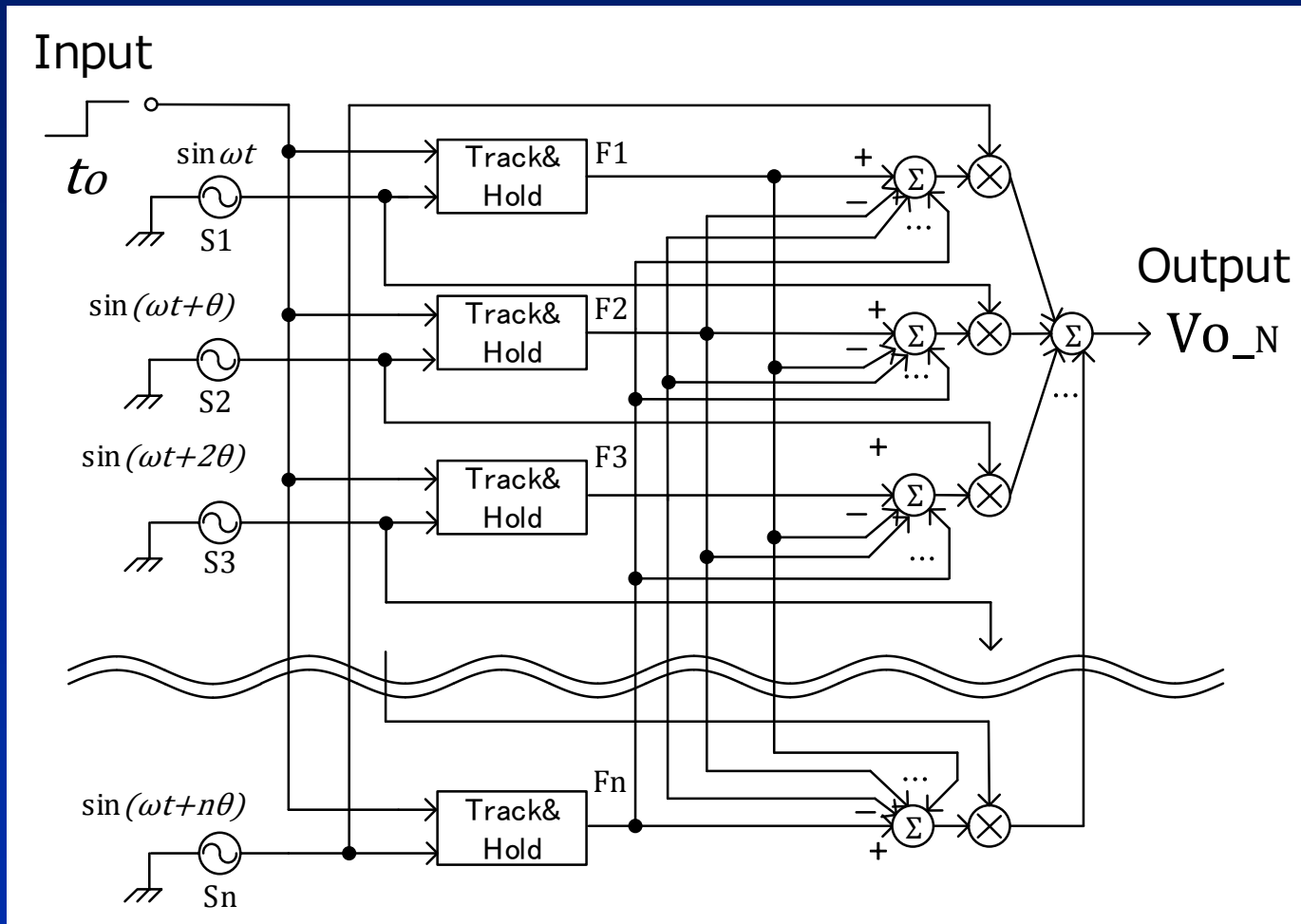

Trigger circuit is a key !  
 Trigger circuit for TDC  $\longleftrightarrow$  T/H circuit for ADC.