

S38-1 Data Converters II

15:45-16:15 PM

Nov. 2, 2018 (Fri)

Performance Improvement of Delta-Sigma ADC/DAC/TDC Using Digital Technique

Haruo Kobayashi

J.-L. Wei, M. Murakami, J. Kojima,

N. Kushita, Y. Du, J. Wang

Gunma University, Japan



Contents

- Objective of This Paper
- What is DWA ?
- LP, HP DWA
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

Contents

- Objective of This Paper
- What is DWA ?
- LP, HP DWA
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

Objective of This Paper

- Review the research results of authors' group

in the area of **DWA: Data Weighted Averaging** .

ADC/ DAC performance improvement
with simple digital techniques

- Consider their application to TDC
- Consider to unify the DWA algorithms and establish their design methodology.

Contents

- Objective of This Paper
- **What is DWA ?**
- LP, HP DWA
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

Calibration Techniques Classification

ADC/DAC/TDC digital calibration techniques
prevail in nano-CMOS era.

● Error Correction

- No measurement of errors
- Redundancy usage

● Self-Calibration

- Error measurement
- Compensation
- Reference

Voltage

Current

Time (frequency)


Linearity

DWA Techniques


- Error Correction
 - No measurement of errors
 - Redundancy usage
 - Time averaging of errors
 - Spectrum shaping of errors

DWA: Data Weighted Averaging

DEM: Dynamic Element Matching

 


W/O DWA

 

LP DWA




BP DWA

 



HP DWA

Segment DAC with Redundancy

Digital
input
= 4

 


Multiple
realization
configurations

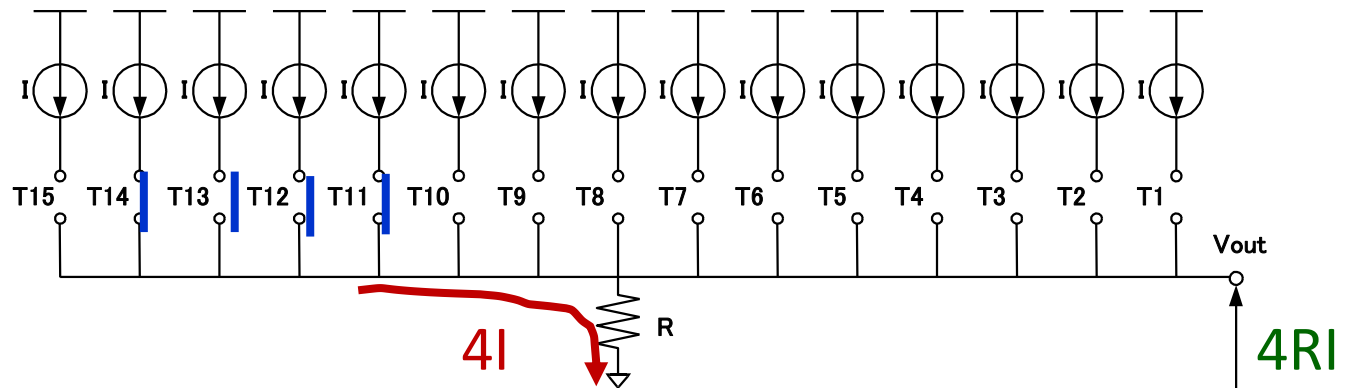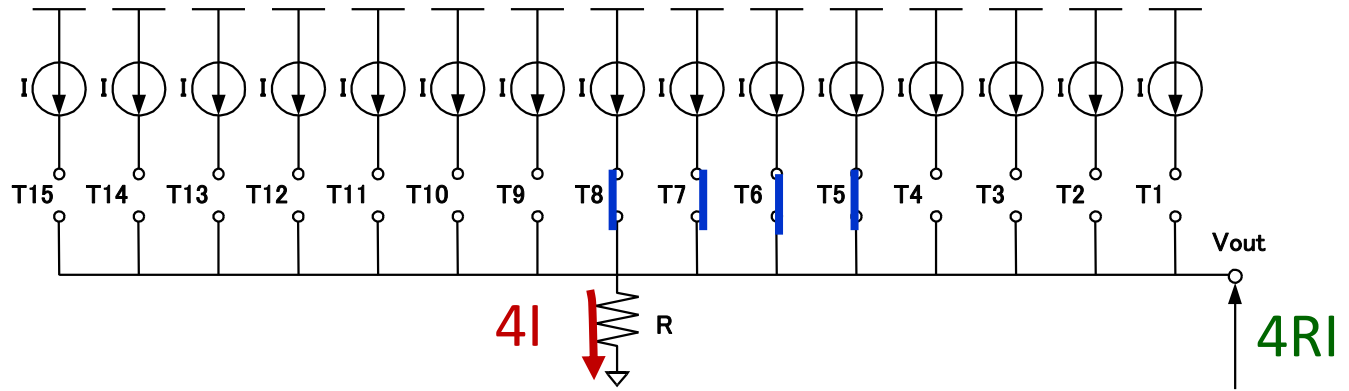



Unit Cell Mismatches

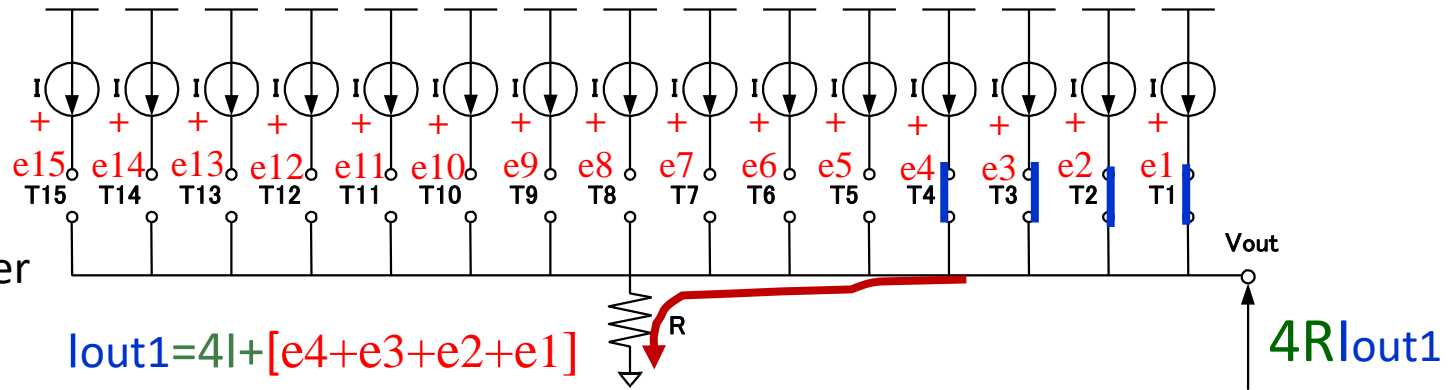Current mismatches $e_{15}, e_{14}, \dots, e_1$ spectrum shaping by cell selection order




DWA algorithm

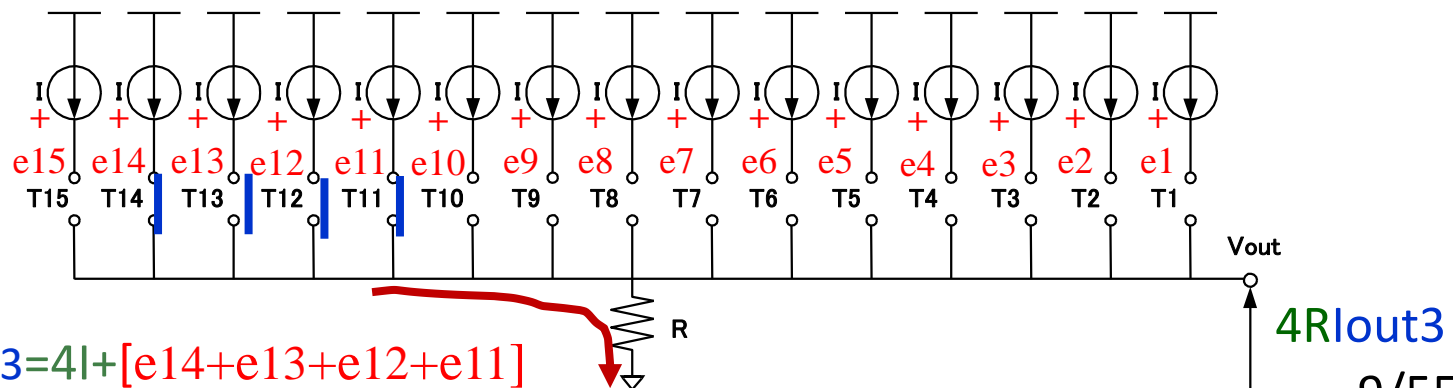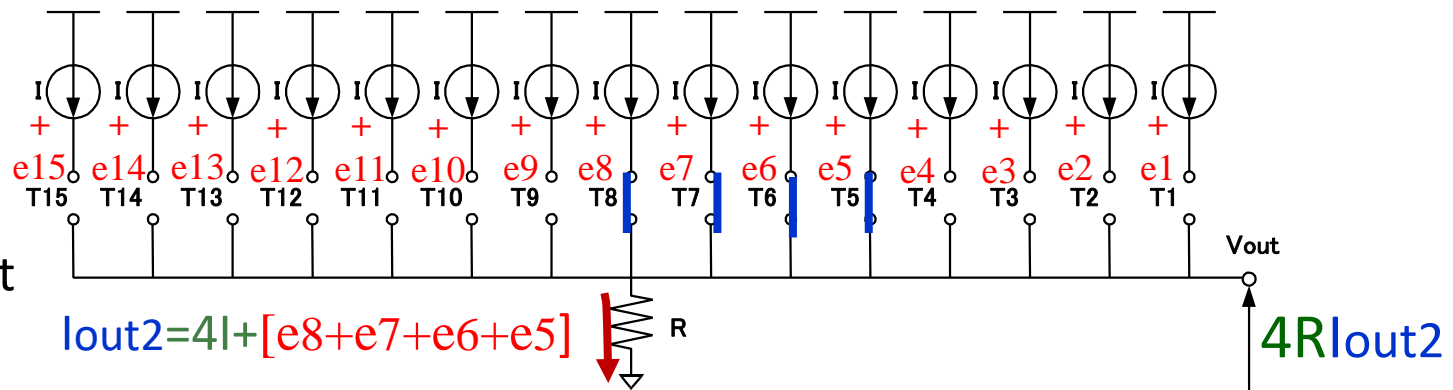No measurement of $e_{15}, e_{14}, \dots, e_1$




$\Delta\Sigma$ Modulation and DWA

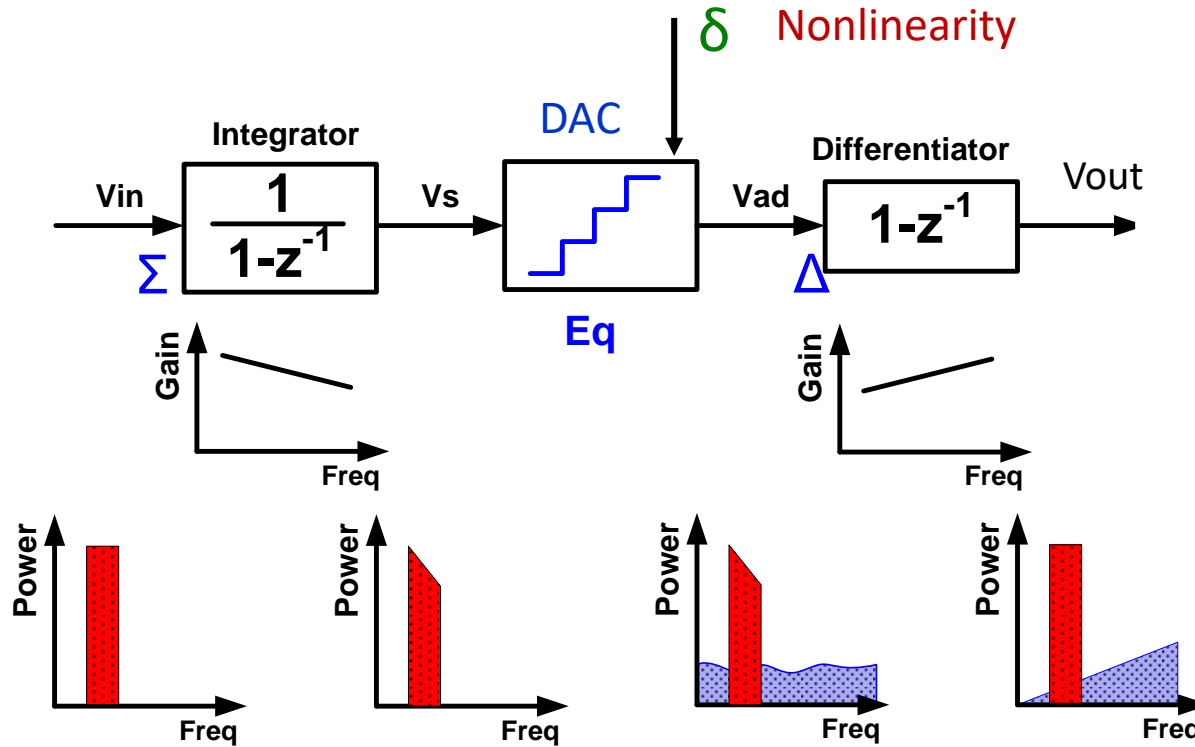

$$V_{out}(z) = V_{in}(z) + (1 - z^{-1}) \cdot \delta(z)$$

DAC nonlinearity $\delta(z)$ is first-order noise-shaped.

$\Delta\Sigma$ Modulation and DWA

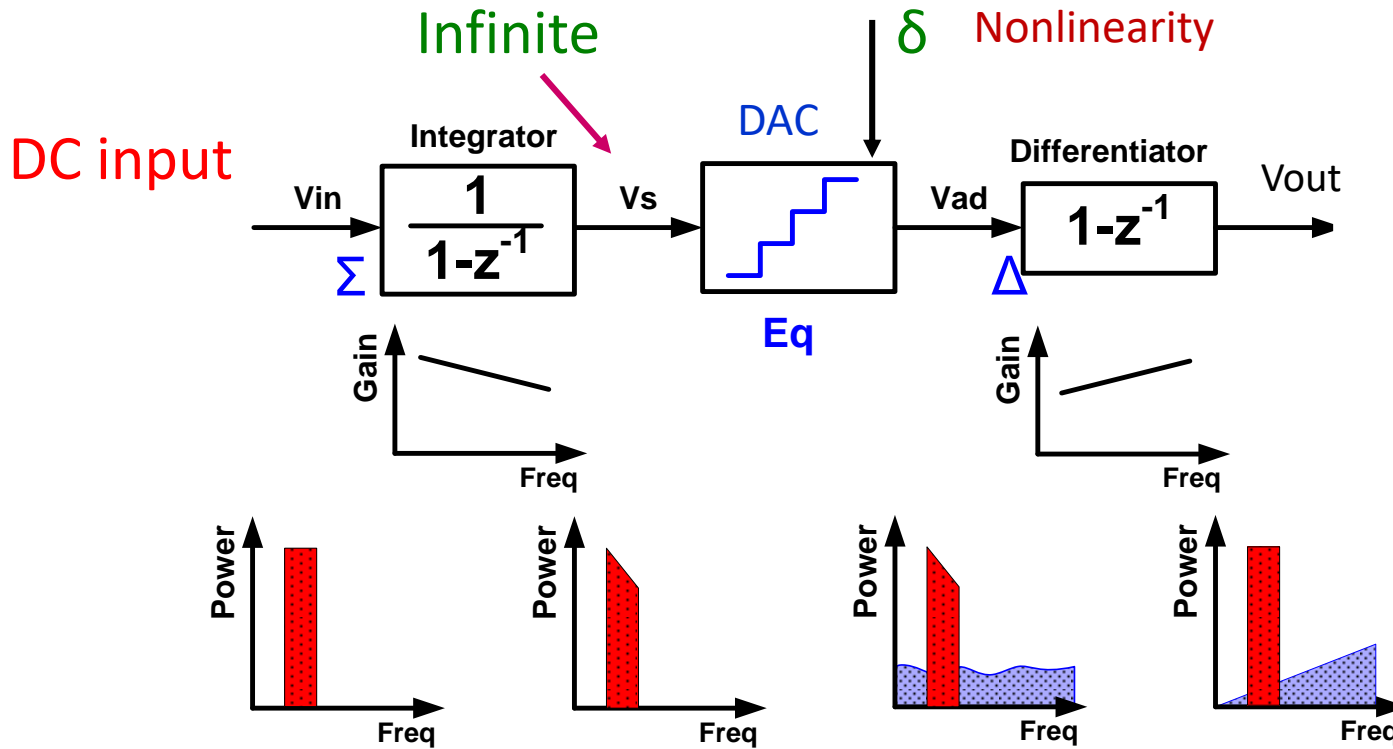


This configuration can NOT be implemented !

Equivalent Operation Using DWA to $\Delta\Sigma$ Modulation



Normal DAC




DWA DAC

 

Current Cell

 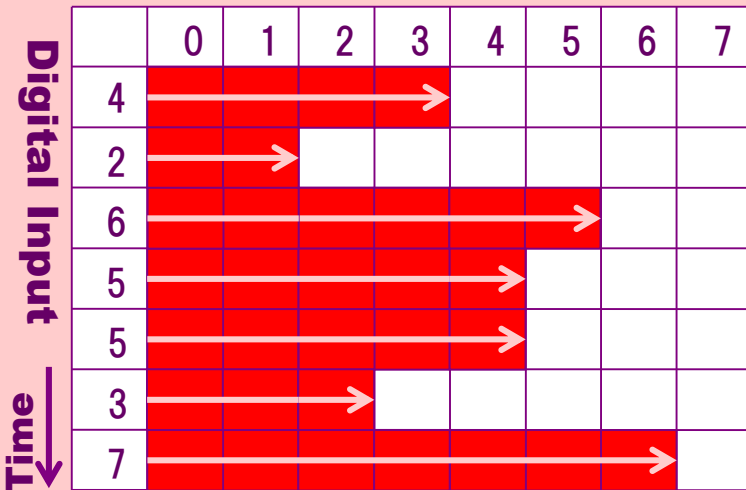


Current Cell

 

“Infinite” is equivalently realized with wrap-around

DWA Operation is a fun !

 

Passing a baton in relay race !




Contents

- Objective of This Presentation
- What is DWA ?
- **LP, HP DWA**
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

LP: Low Pass

HP: High Pass

LP $\Delta\Sigma$ AD Modulator

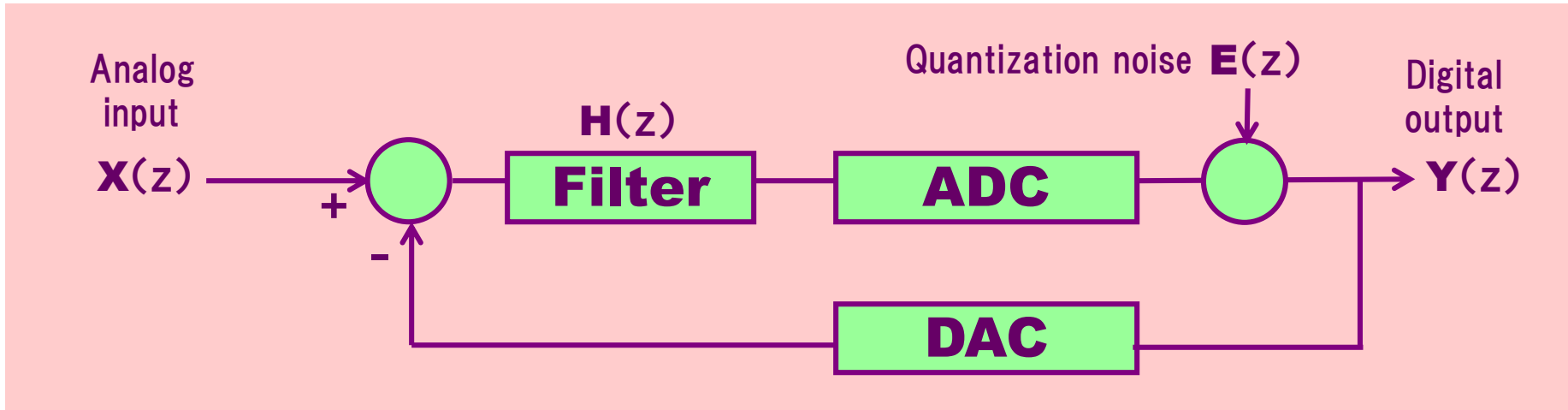


STF


NTF

$$Y(z) = \frac{H(z)}{1+H(z)} X(z) + \frac{1}{1+H(z)} E(z)$$


↓
↓
1
0

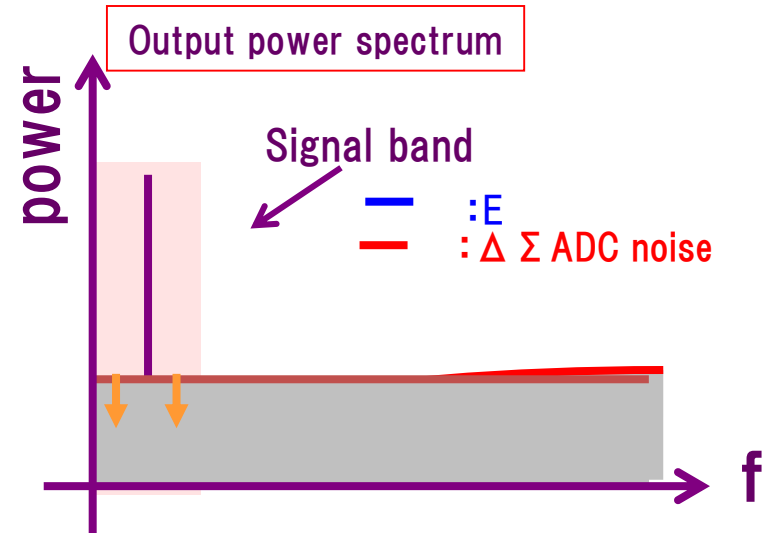

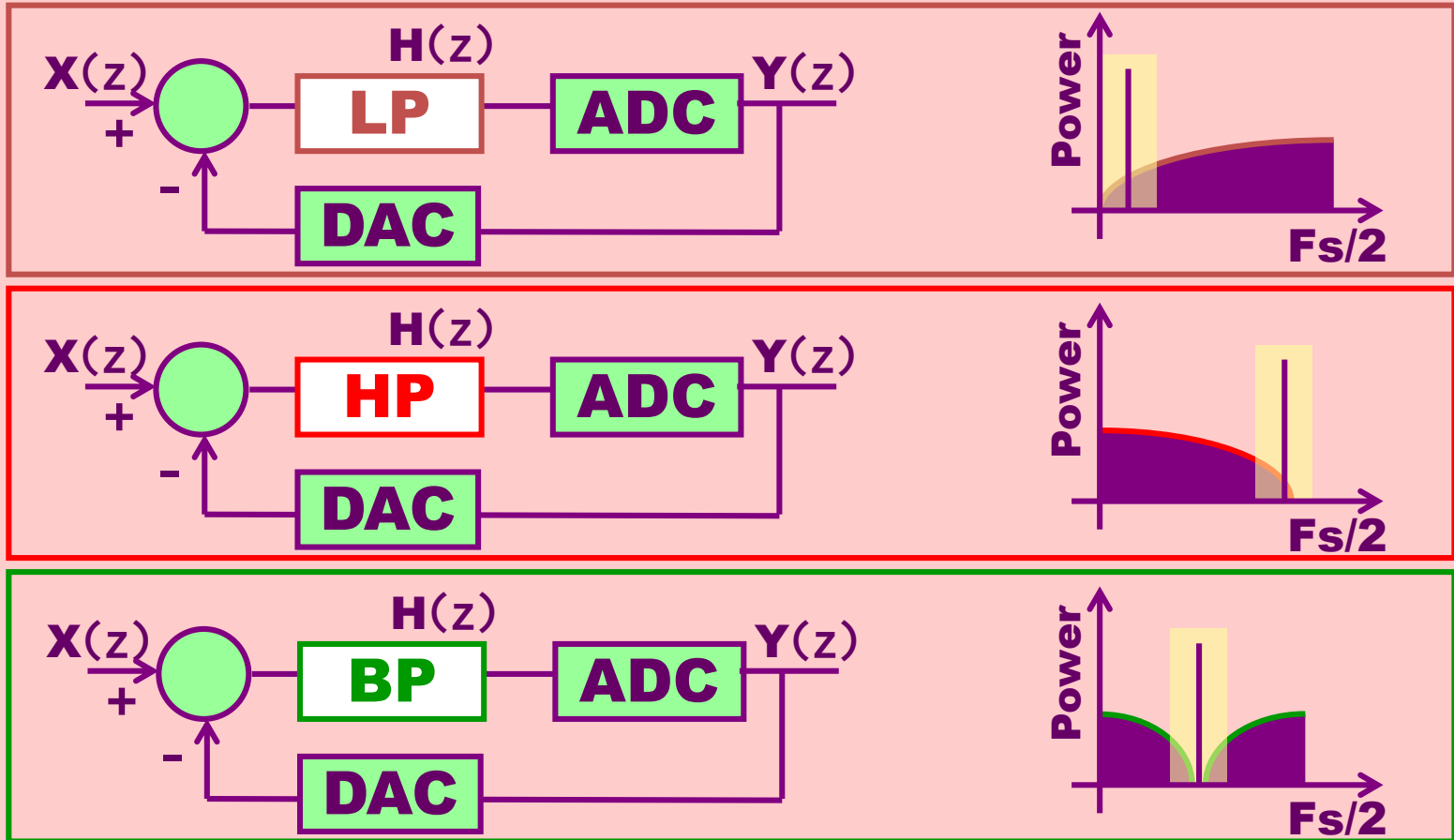Varieties of $\Delta\Sigma$ AD Modulators





Multi-bit DAC Nonlinearity

 

● :Single-bit Output

○ :Multi-bit Output

  


$$Y(z) = \frac{H(z)}{1 + H(z)} \{X(z) - \delta(z)\} + \frac{1}{1 + H(z)} E(z)$$

$\delta(z)$ is NOT noise-shaped

Why Multi-bit ADC/DAC inside $\Delta\Sigma$ AD Modulator ?


Single-Bit

 

- High slew-rate of opamp

⇒ Large power

Multi-Bit

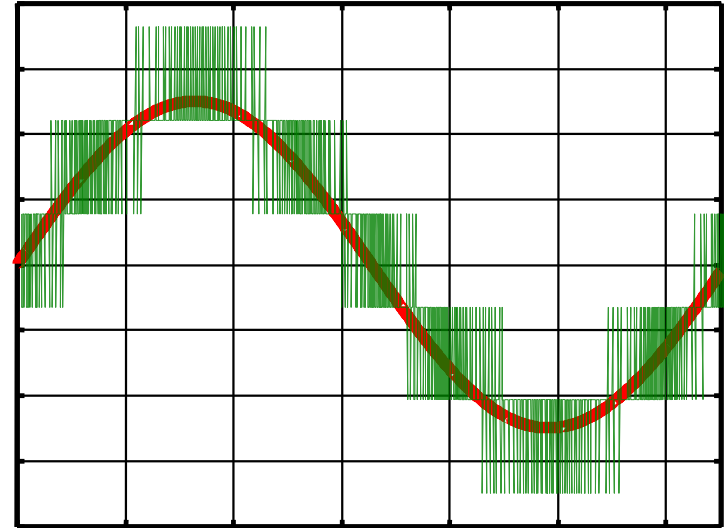

- Low slew-rate of opamp

⇒ Small power

- Problem:

Multi-bit DAC nonlinearity


Unit Cell Mismatches

Segment DAC




Current Cell Mismatch
($e_0, e_2, e_3, \dots, e_7$)

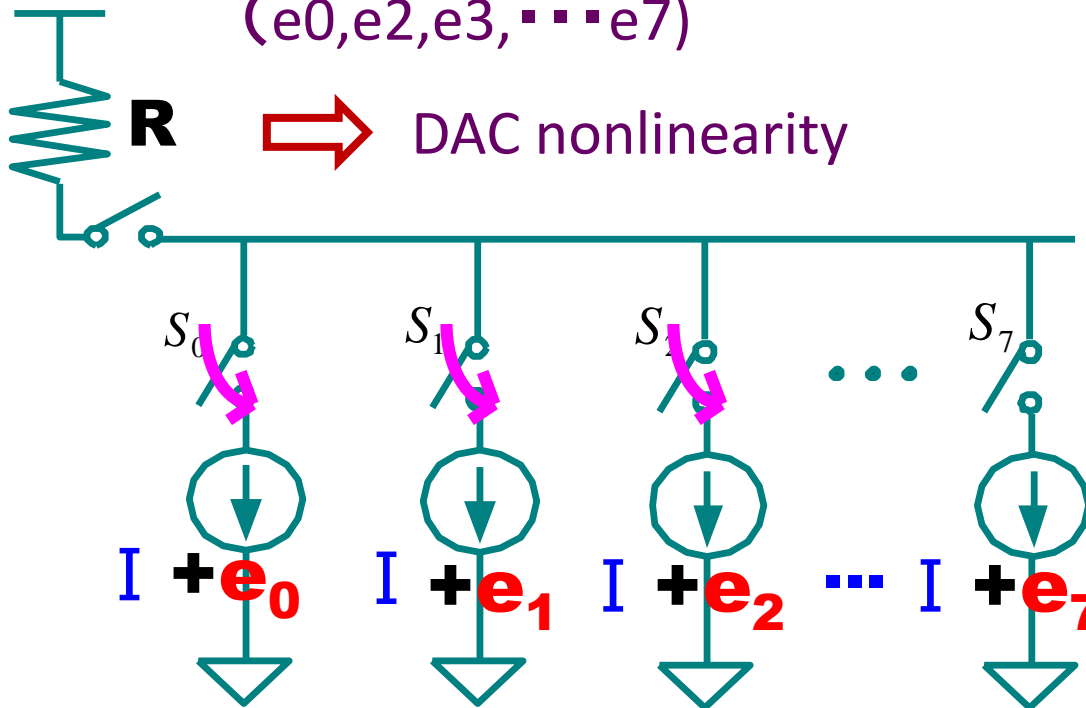
Errors of specific current cells
are accumulated




Current Cell

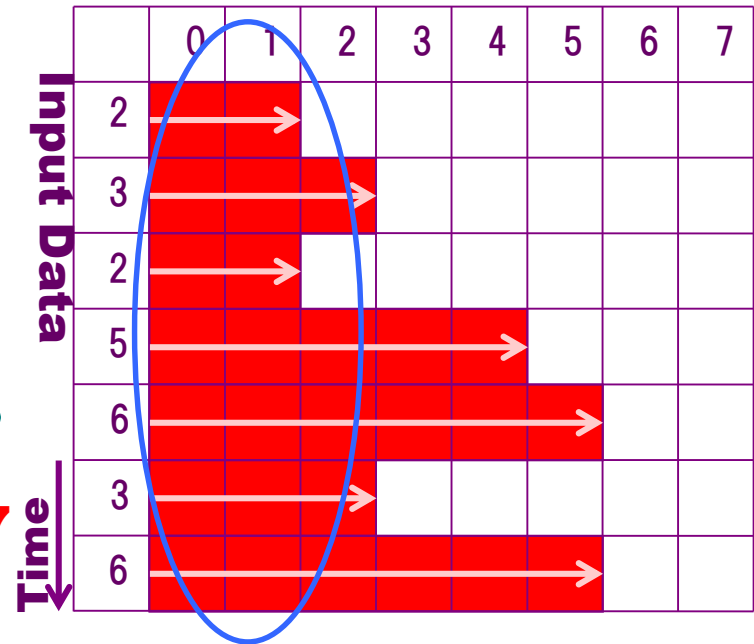




Equivalent LP DWA Algorithm

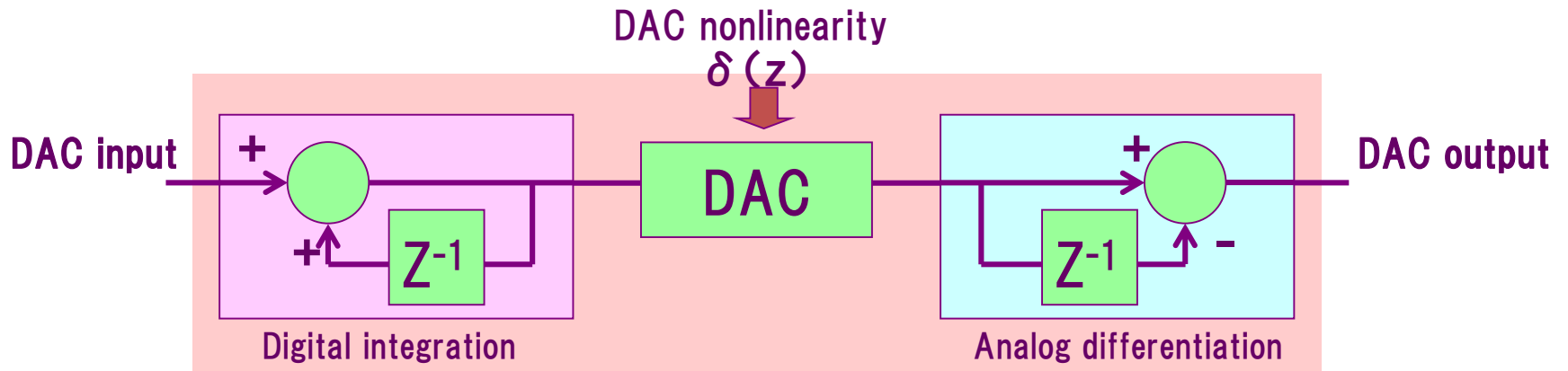

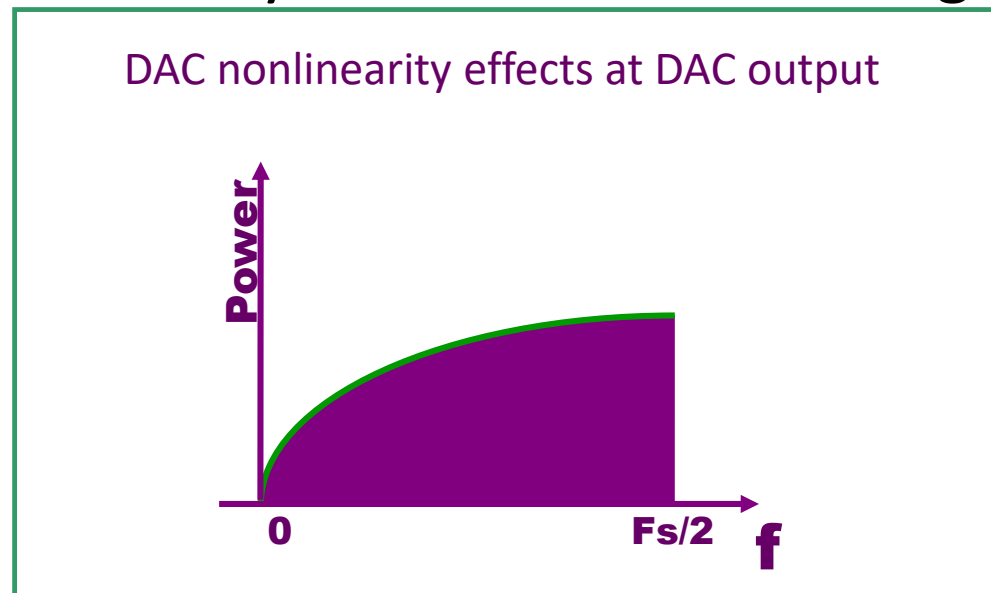
- Signal \rightarrow Integration \times Differentiation = Flat
- DAC Nonlinearity \rightarrow Differentiation (High Pass)




LP DWA Algorithm Realization

   



Let's Consider HP DWA Algorithm

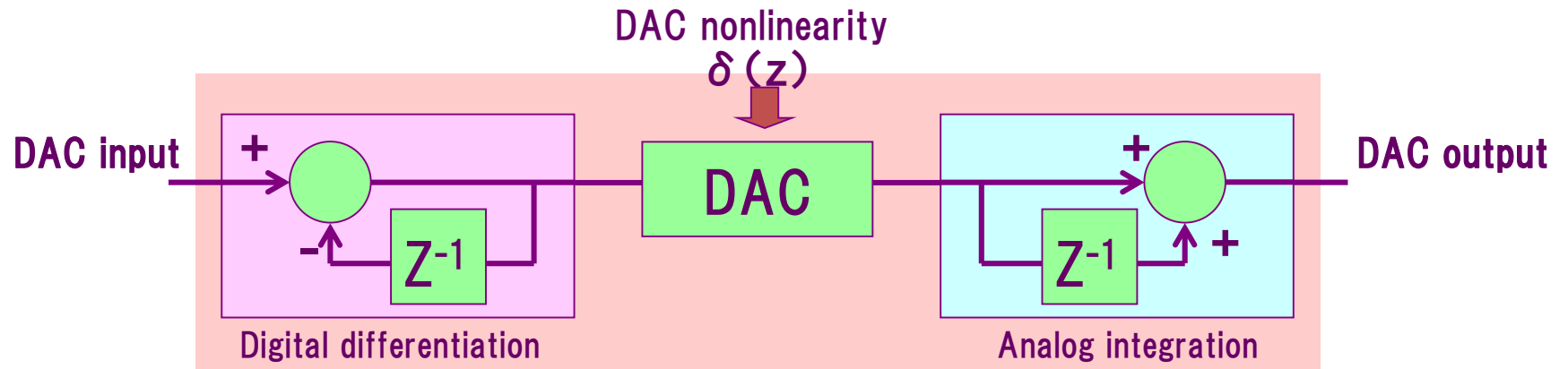

 
- Signal \rightarrow Differentiation \times Integration = Flat
- DAC Nonlinearity \rightarrow Integration (Low Pass)



HP DWA Algorithm Realization

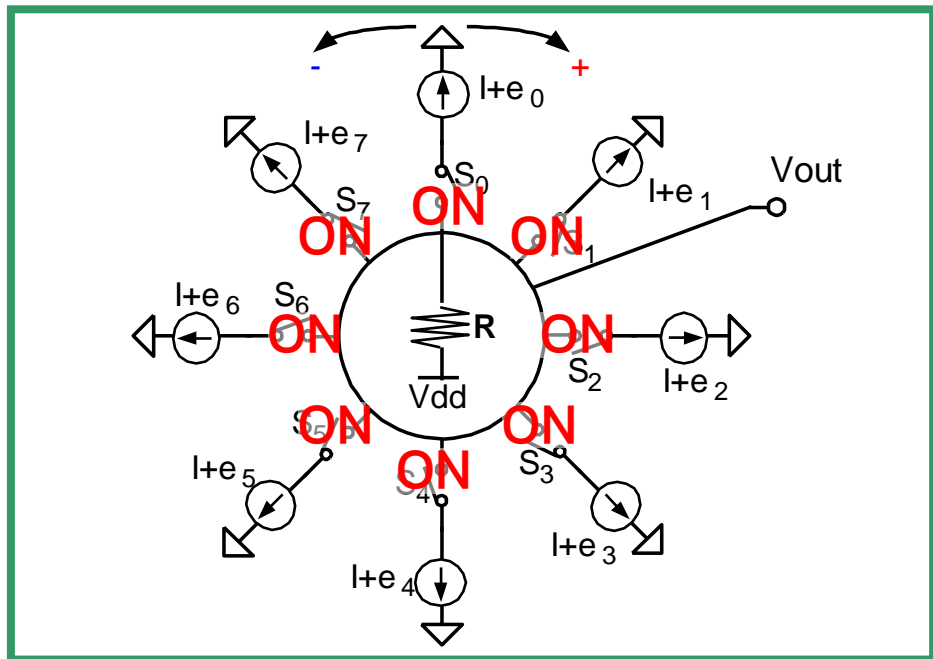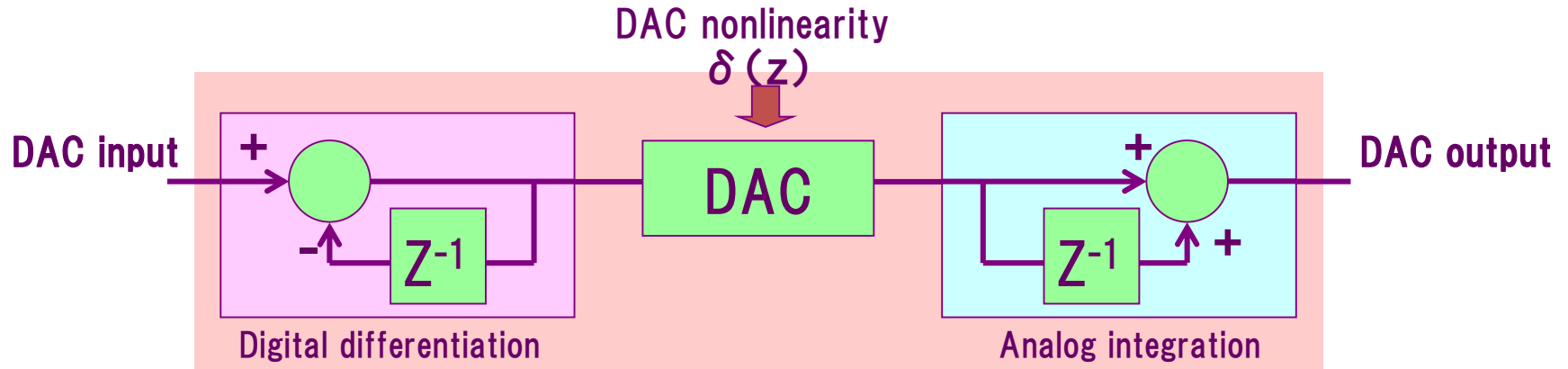

$$H(z) = 1 / (1 + Z^{-1})$$

 

Contents


- Objective of This Presentation
- What is DWA ?
- LP, HP DWA
- **Multi-Bandpass DWA**
- Multi-Bandpass Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

[1] A. Motozawa, H. Kobayashi, et. al.,
"Multi-BP $\Delta\Sigma$ Modulation Techniques and Their Applications",
IEICE Tran, J90-C(Feb. 2007).

Multi-Bandpass DWA


Type I DWA

 - **N** pointers
- **N**-channel interleave of **LP** DWA algorithm



Type II DWA

 - **N** pointers
- **N**-channel interleave of **HP** DWA algorithm




LP ^{Type I} ⇒ Multi-BP

LP Algorithm




$$H(z) = 1/(1 - z^{-1})$$

Current Cell

 


Multi-BP Algorithm (LPF)

N=4

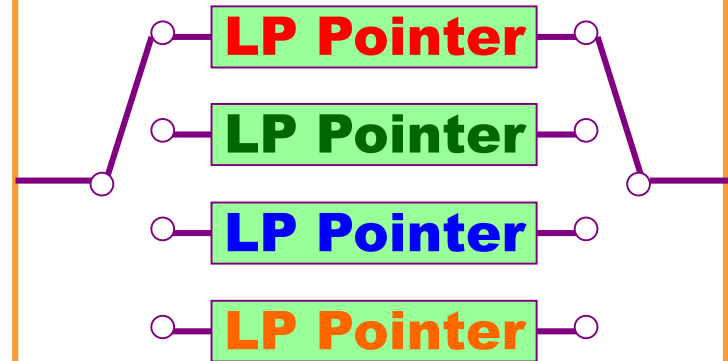


$$H(z) = 1/(1 - z^{-4})$$

Current Cell

 


Type II

HP

 

BP

 

Multi-BP


HP Algorithm



$$H(z) = 1/(1+Z^{-1})$$


Back and forth

Current cell

 


BP Algorithm

N=2

 


$$H(z) = 1/(1+Z^{-2})$$

 


Multi-BP Algorithm


N=4

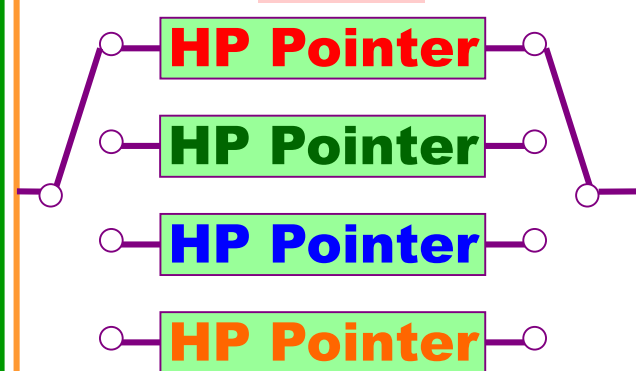

$$H(z) = 1/(1+Z^{-4})$$

 

Multi-BP Type II N=4

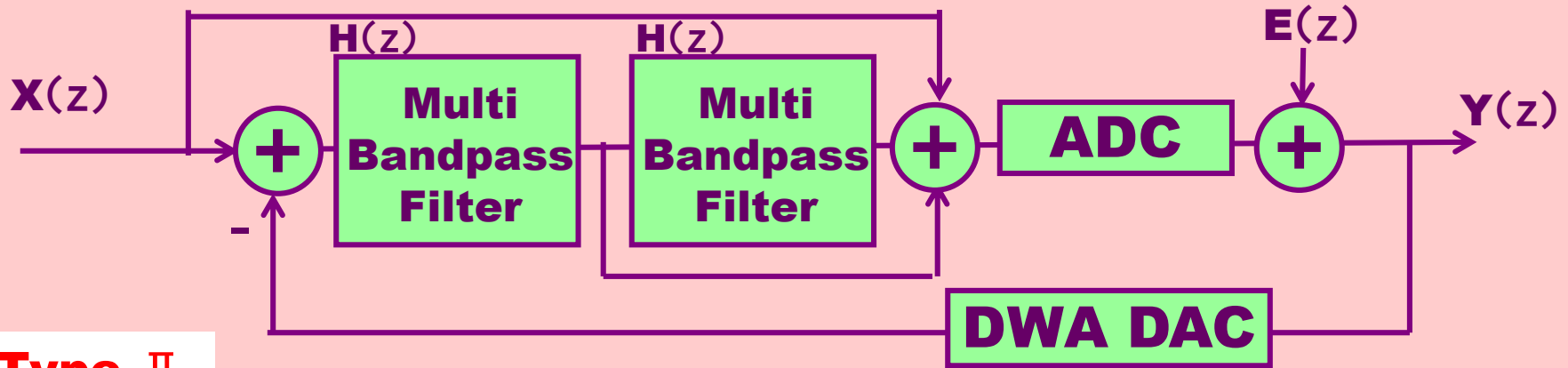

Type II



$$H(z) = \frac{-z^{-4}}{1+z^{-4}}$$

$$\text{STF} = -z^{-4}$$

$$\text{NTF} = (1+z^{-4})^2$$

Signal Bands
1/8, 3/8
X Fs

Multi-BP Type II N=4 Simulation Results

  

Multi-BP DWA algorithm is effective

Contents


- Research Objective
- What is DWA ?
- LP, HP DWA
- Multi-Bandpass DWA
- **Multi-Bandpass Complex DWA**
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

[1] M. Murakami, H. Kobayashi, et.al.,
"I-Q Signal Generation Techniques for Communication IC Testing and
ATE Systems", IEEE International Test Conference (Nov. 2016).

[2] H. San, H. Kobayashi, et. al., "A Second-Order Multi-bit Complex
Bandpass $\Delta\Sigma$ AD Modulator With I, Q Dynamic Matching and DWA
Algorithm", IEICE Trans. Electron, (June 2007).

Necessity of I,Q signal

RF analog front-end of Receiver IC

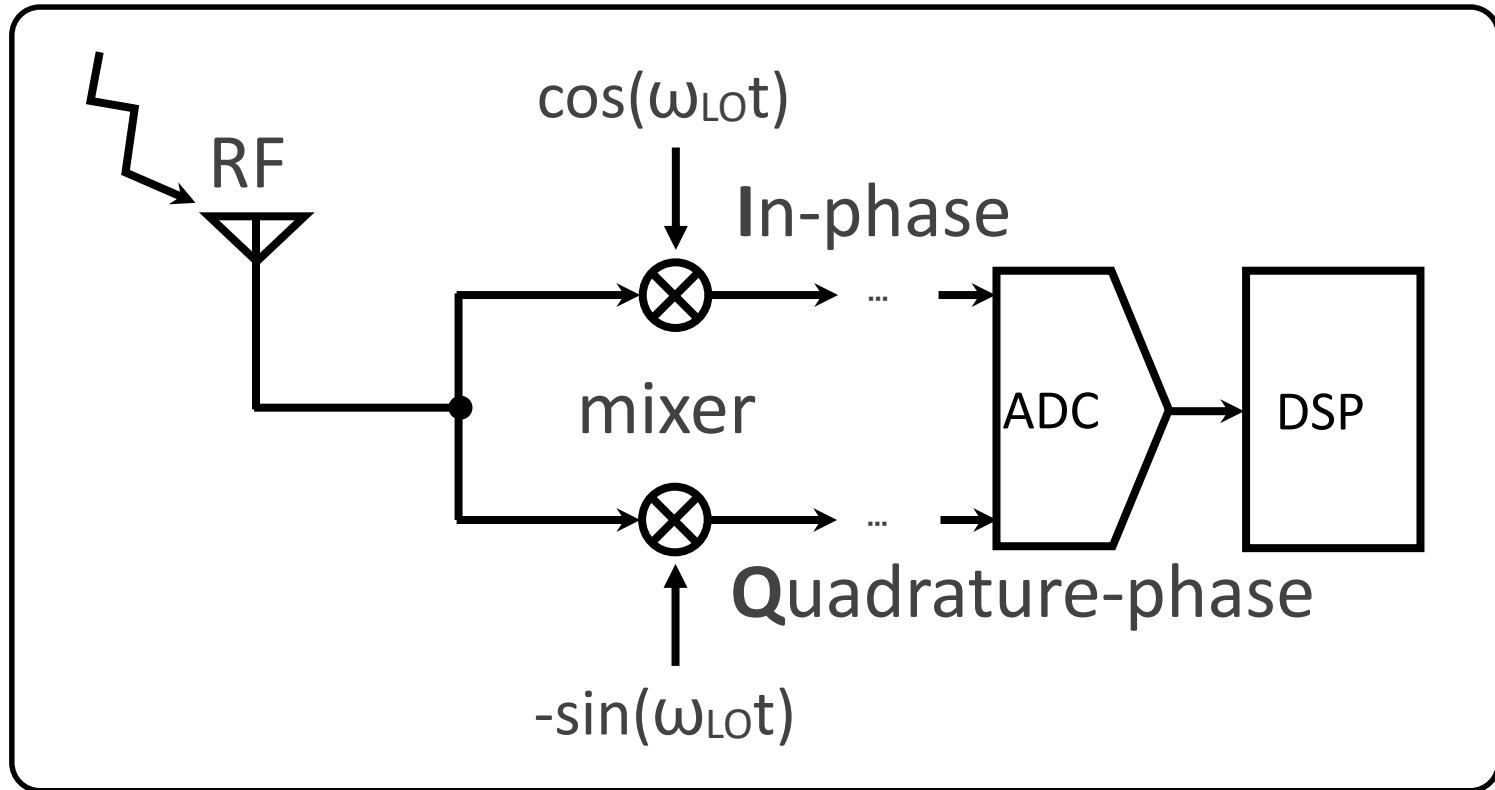


Need testing!

Necessity of Multi-Tone Signal




Linearity testing of

 - ✓ Mixer
- ✓ Up/Down converter
- ✓ Radio communication system , etc.




Noise Power Ratio (NPR)



Need!

   


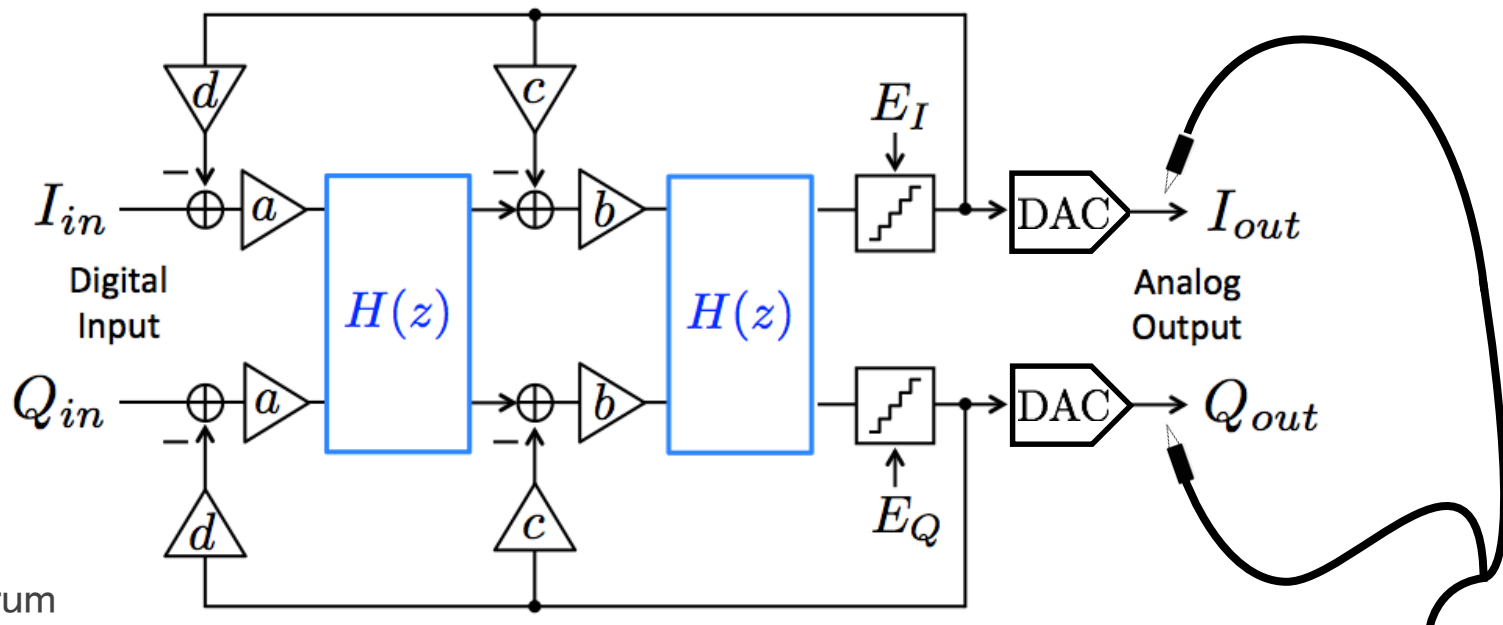
2nd-order Complex Multi-BP $\Delta\Sigma$ DAC



Output spectrum

  

Principle of Complex BP Noise Shape

 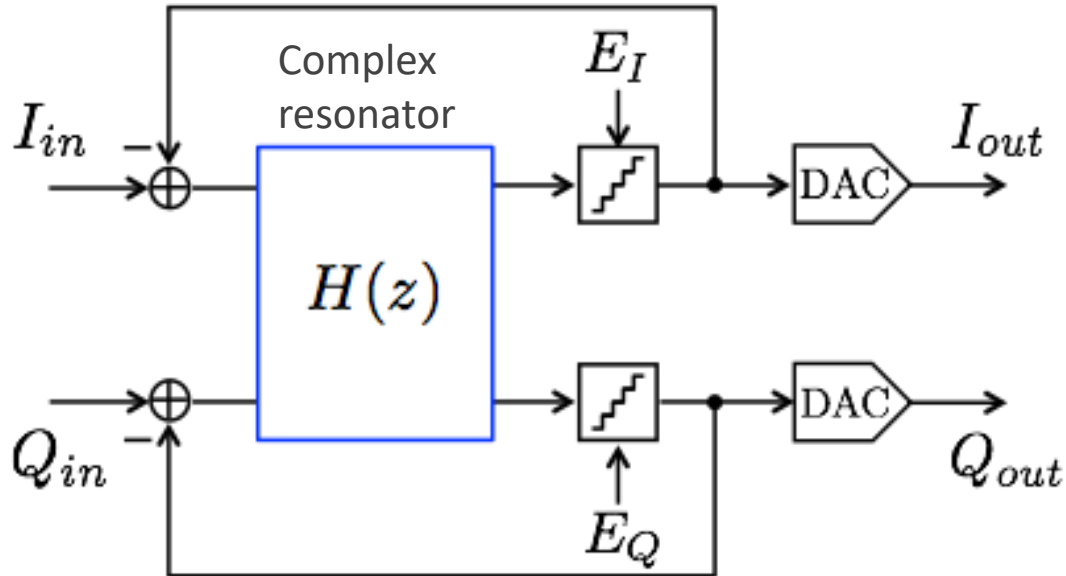


Signal Transfer Function = 1


$$I_{out} + jQ_{out} = \boxed{1} (I_{in} + jQ_{in}) + \boxed{0} (E_I + jE_Q)$$

Noise Transfer Function = 0

Complex Resonator

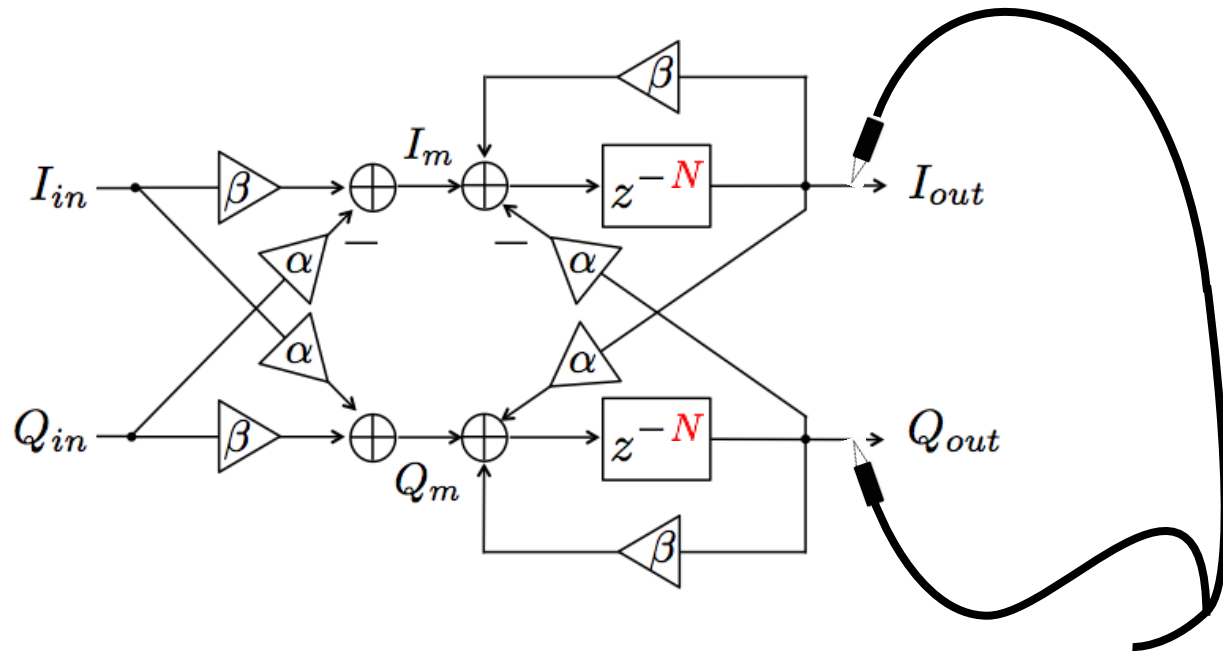


Output spectrum

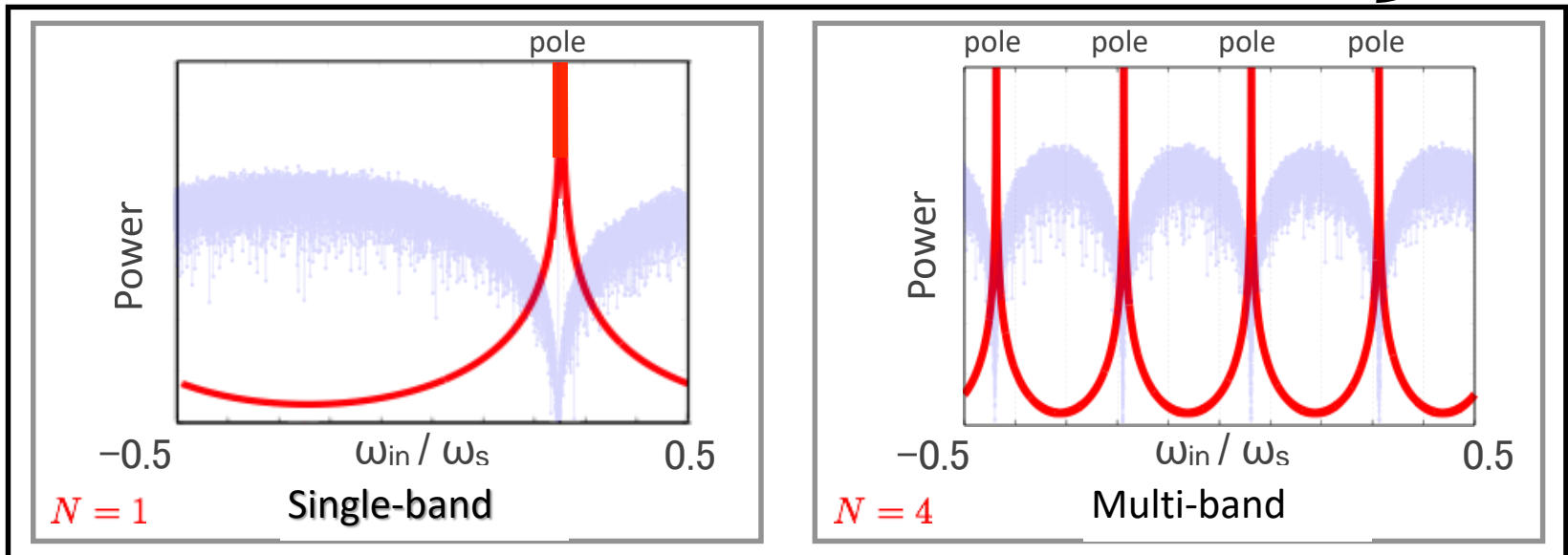


Complex Resonator



Asymmetric

 


Output spectrum

 

Asymmetric

  


Equivalent Circuit of Complex DWA

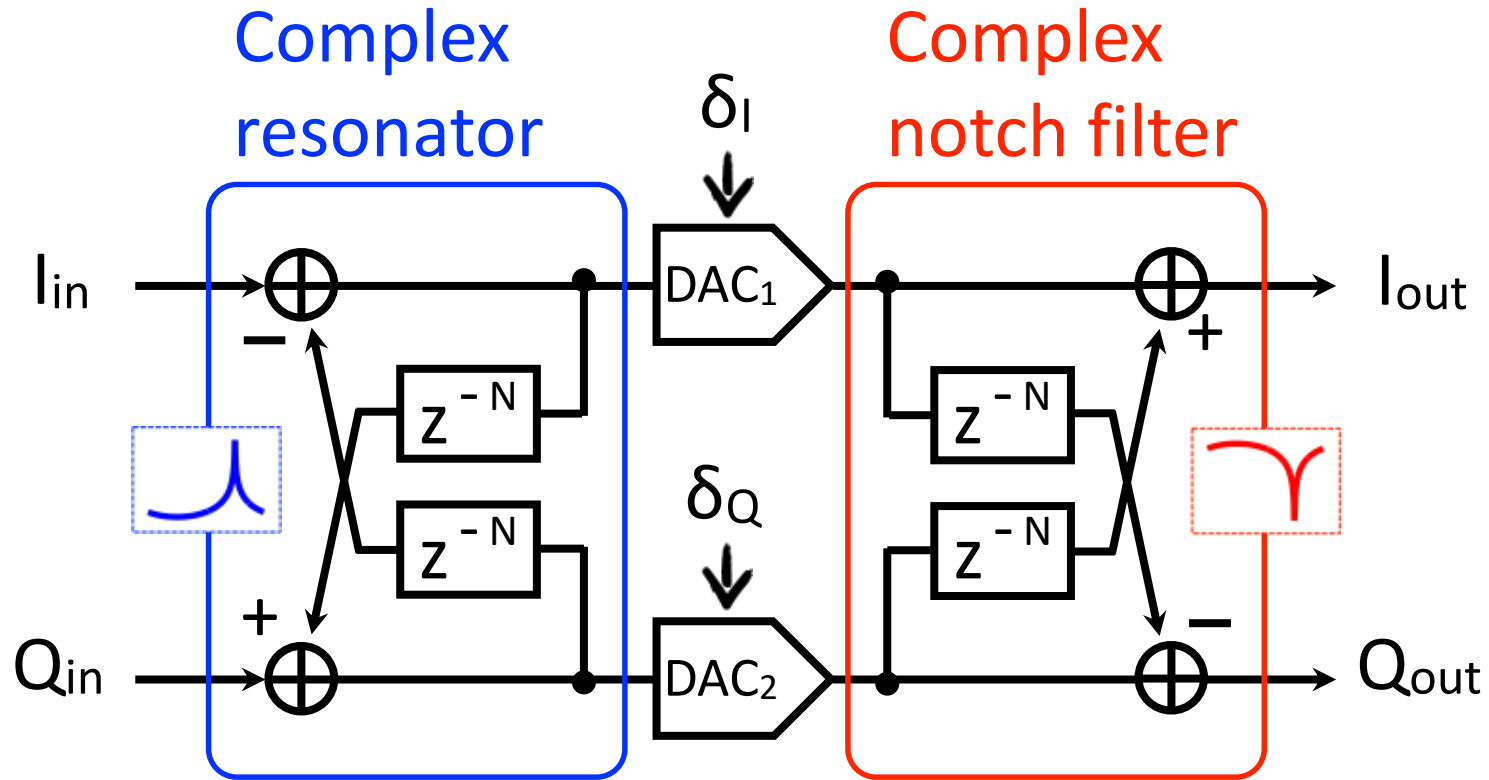



δ_I, δ_Q affected by only **complex notch**

DAC input can be

 

Can't be realized directly

Equivalent Circuit Implementation

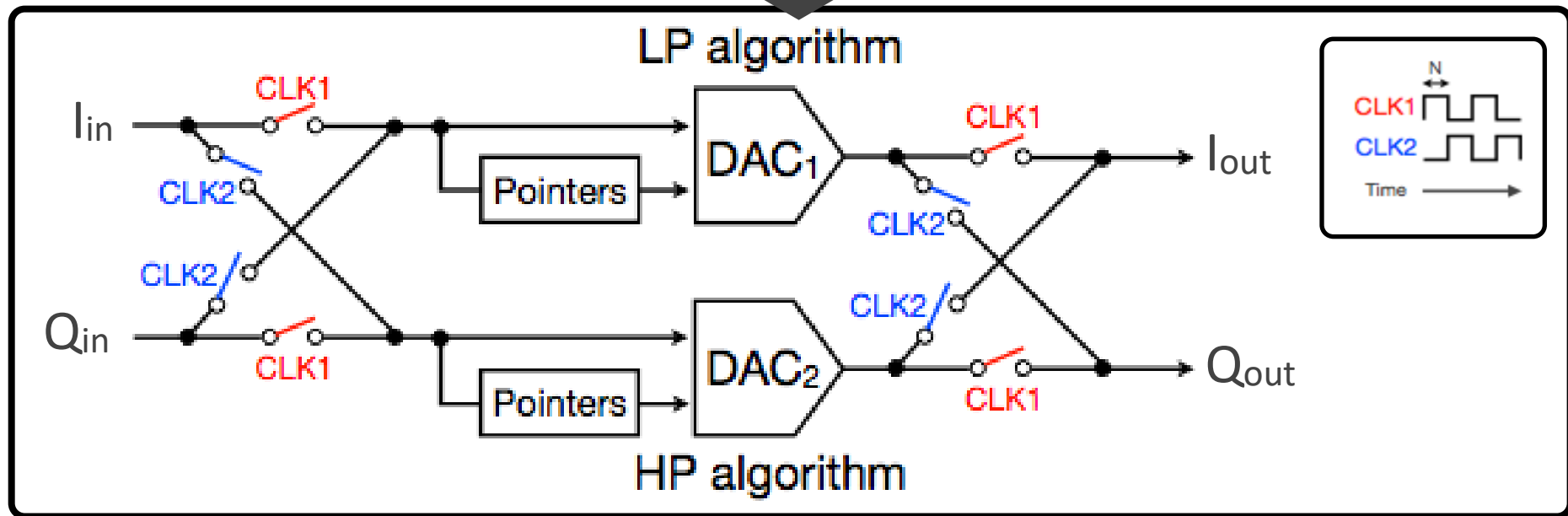 


- ◆ Attach pointers
- ◆ Exchange upper-path and lower-path every N clock

➔ Complex DWA is realized.

Complex Multi-Bandpass DWA Algorithm

$N = 4$ (four zero points)

 

DAC₁ (**LP** operation)



DAC₂ (**HP** operation)

TIME ↓ |DAC Input:



I_{in}	Q_{in}	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
4	2	←							
3	2	←							
2	6	←							
2	1	←							
6	7	←			←				
1	5		←						
7	4		←						
5	3		←						

I_{in}	Q_{in}	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
4	2	←							
3	2	←							
2	6	←							
2	1	←							
6	7	←				←			
1	5		←						
7	4	←							
5	3	←				←			

Simulation Result ~Ideal Linear DAC~

 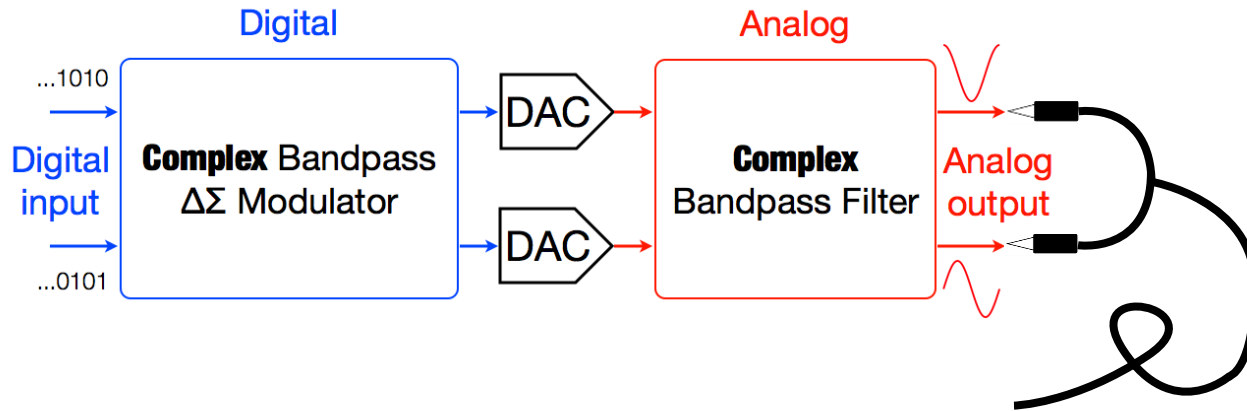

 
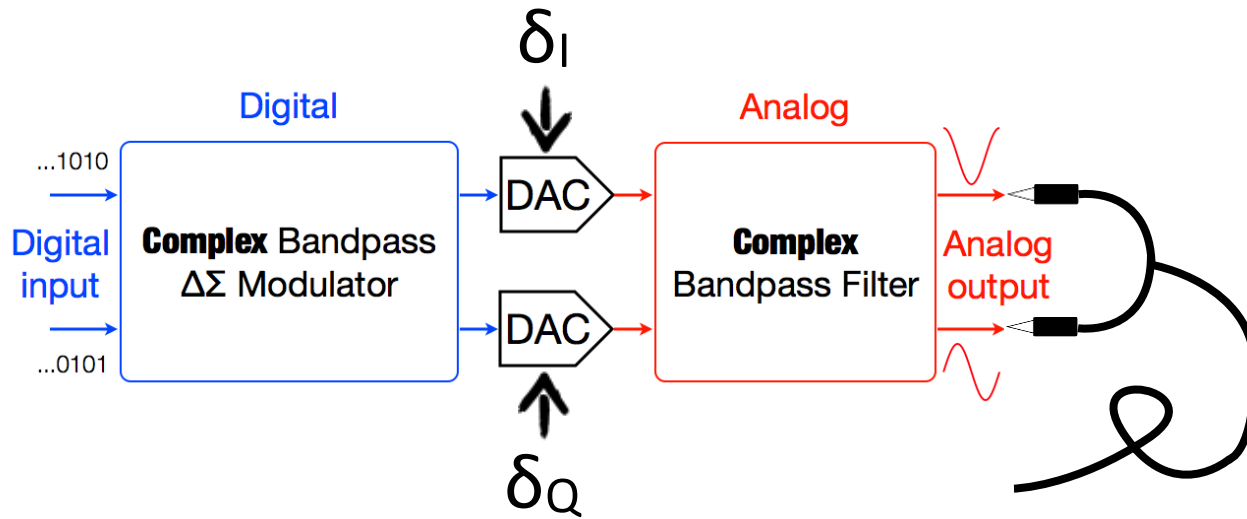
Simulation Result ~Actual Non-Linear DAC~



Notches filled with noise

Simulation Result




~Actual Non-Linear DAC + DWA~

 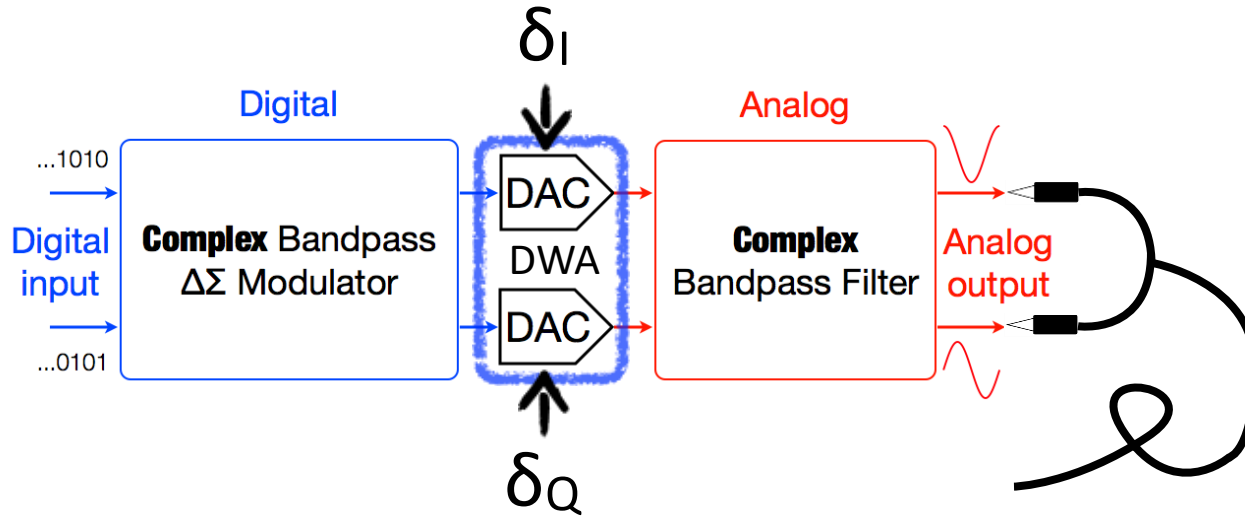


Notches filled with noise

Simulation Result


~Actual Non-Linear DAC + DWA~

 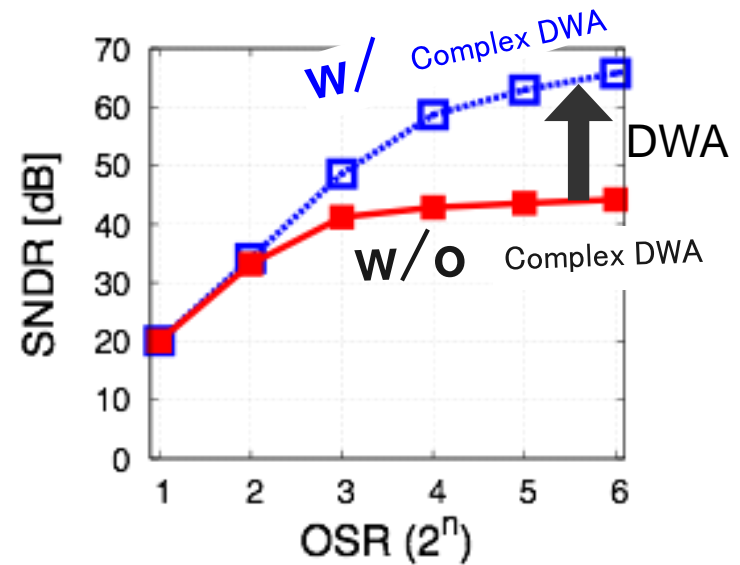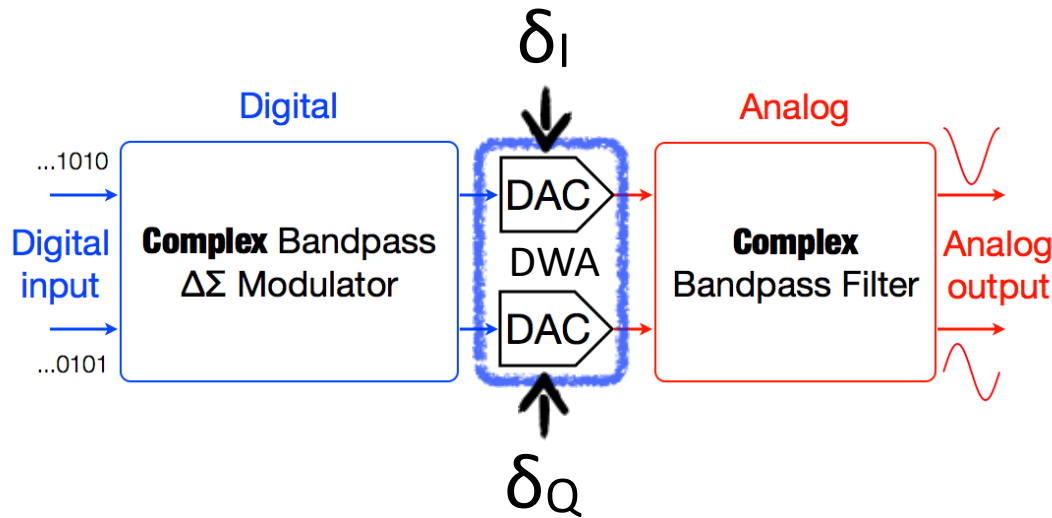

DWA

 

Notches filled with noise

 

Steep Notches




Contents

- Research Objective
- What is DWA ?
- LP, HP DWA
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- **Second-Order DWA**
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

[1] H. Hagiwara, H. Kobayashi, et. al.,
“DA Converter Circuit Provided with DA Converter of
Segmented Switched Capacitor Type”,
US Patent Application, Pub. No.: US 2005/0285768 A1 (Dec. 29, 2005).

2nd-order DWA
  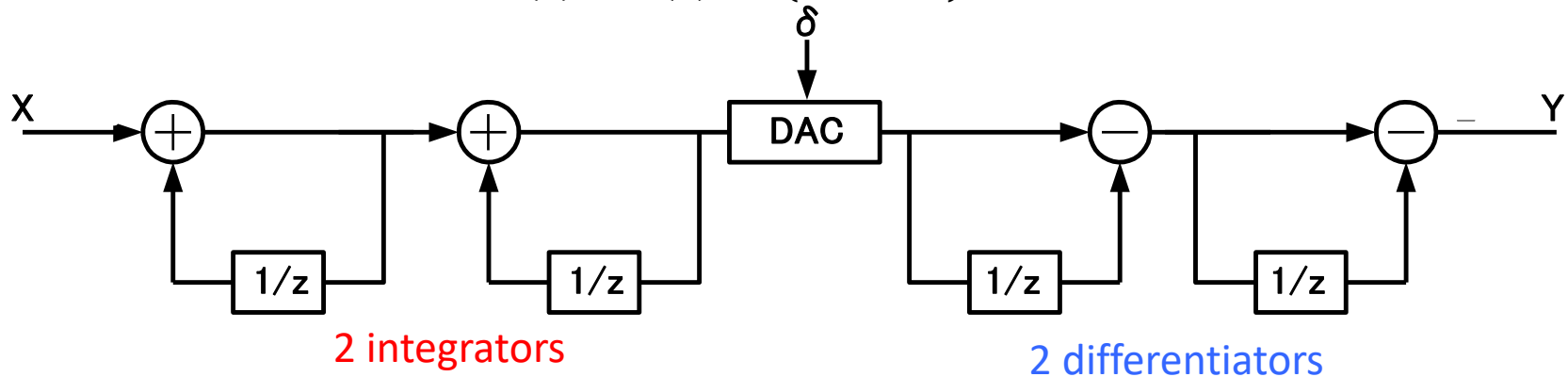
$$Y(z) = X(z) + (1 - z^{-1})^2 \delta(z)$$



- 2nd-order DWA is more effective
- But its circuit/operation become complicated

Contents

- Research Objective
- What is DWA ?
- LP, HP DWA
- Multi-Bandpass DWA
- Multi-Bandpass Complex DWA
- Second-Order DWA
- **Application to Multi-bit $\Delta\Sigma$ TDC**
- Conclusion




[1] T. Chujo, H. Kobayashi, et. al.,
“Timing Measurement BOST With Multi-bit Delta-Sigma TDC”,
20th IEEE International Mixed-Signal Testing Workshop (June 2015).

$\Delta\Sigma$ TDC Features

Timing T measurement between CLK1 and CLK2



   
$\Delta\Sigma$ Time-to-Digital Converter (TDC)



$$T \propto \# \text{ of } 1' \text{ at } Dout$$

- Simple circuit
- High linearity
- Measurement time \rightarrow longer \Rightarrow time resolution \rightarrow finer

Principle of $\Delta\Sigma$ TDC

 

Dout # of 1's is proportional to ΔT


ΔT

of 1's

Dout

short

few

 


long



many


$\Delta\Sigma$ TDC Configuration

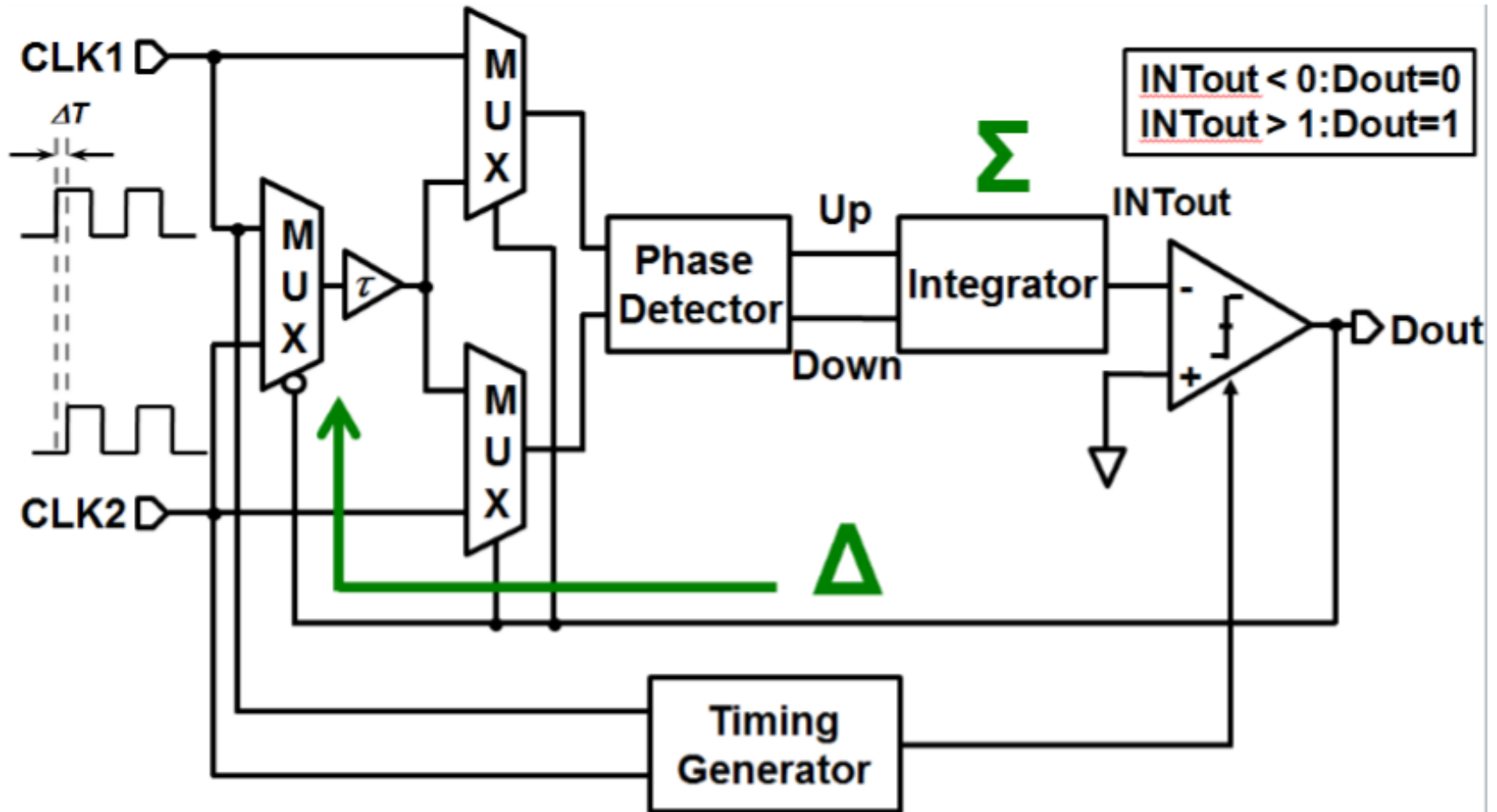

[1] T. Chujo, H. Kobayashi, "Timing Measurement BOST With Multi-bit Delta-Sigma TDC", IEEE IMSTW (June 2015).

[2] Y. Osawa, H. Kobayashi, "Phase Noise Measurement Techniques Using Delta-Sigma TDC", IEEE IMS3TW (Sept. 2014).


Multi-Bit $\Delta\Sigma$ TDC

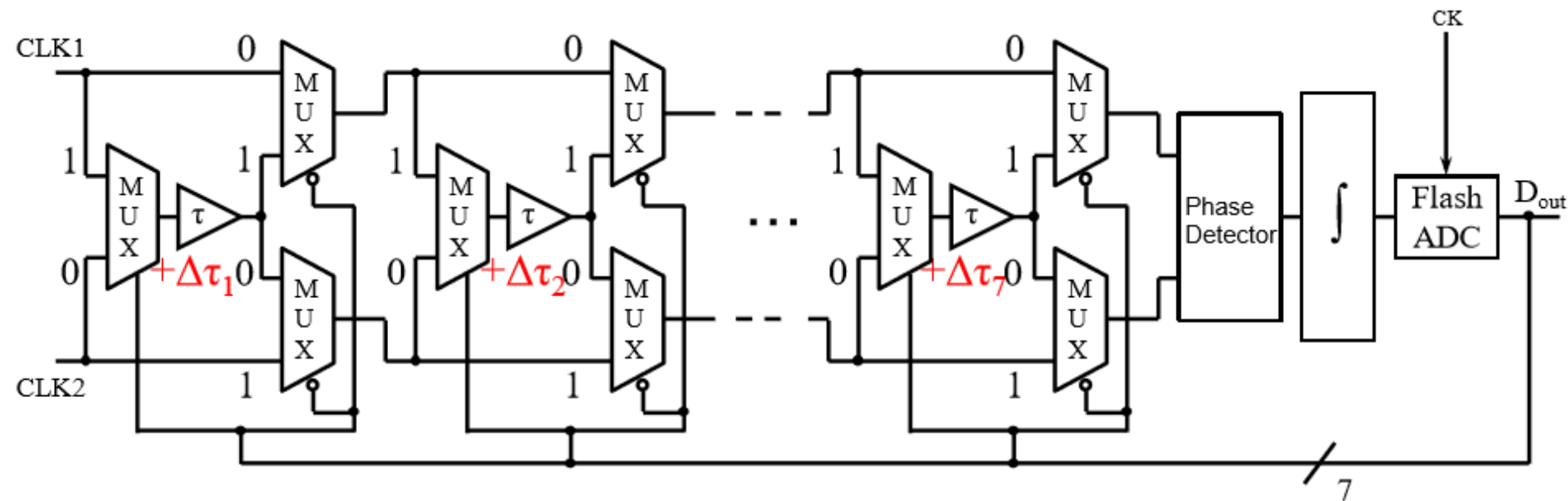

- 3-bit : 7 comparators and delays
 - Fine time resolution with a given measurement time
- ↕
- Shorter measurement time with a given time resolution
- TDC non-linearity due to mismatches among delay cells.

Multi-bit $\Delta\Sigma$ TDC with DWA



For short measurement time:

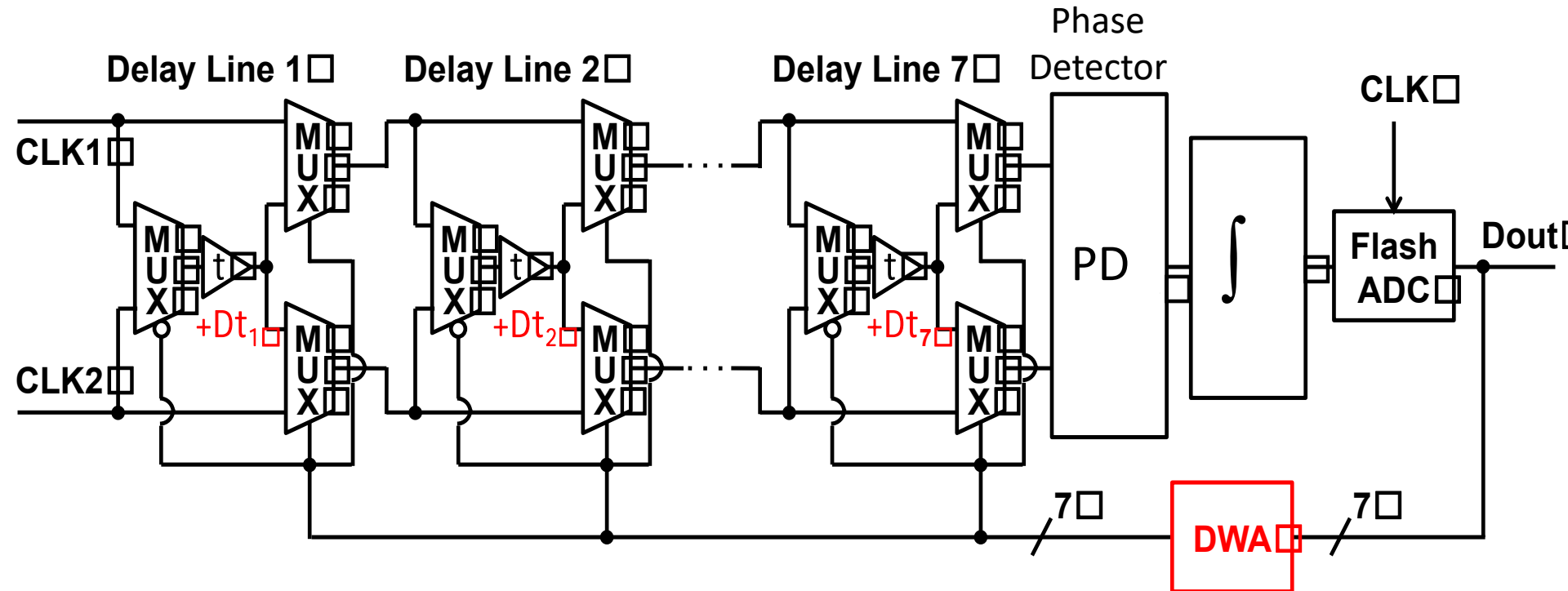


DWA: Data Weighted Averaging

DSP algorithm of compensation for mismatches among delays.

Measured Result

  

Integral Non-linearity

 

10,000 TDC
output data
are measured.



Analog FPGA
Implementation

Contents


- Research Objective
- What is DWA ?
- LP, HP DWA
- Multi-Band DWA
- Multi-Band Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- Conclusion

Conclusion

- Spectrum shaping of errors is possible with DWA algorithms.
Their hardware implementation is simple.
- So far, DWA algorithm derivation is based on mathematical intuition of the researcher as well as simulation.
There are no systematic or theoretical methods.
- There are still possibilities of new DWA algorithms.

Final Statement

 Mathematics is the alphabet
with which God has written the Universe.



Galileo Galilei


Mathematics is the alphabet
with which the circuit designer writes his/her new idea.

Contents

- Research Objective
- What is DWA ?
- LP, HP DWA
- Multi-Band DWA
- Multi-Band Complex DWA
- Second-Order DWA
- Application to Multi-bit $\Delta\Sigma$ TDC
- **Digital Dither for $\Delta\Sigma$ DAC**
- Conclusion


- [1] J. Kojima, H. Kobayashi, et. al., “Limit Cycle Suppression Technique Using Digital Dither in Delta Sigma DA Modulator”, IEEE ICSICT (Nov. 2016).
- [2] J. Wei, H. Kobayashi, et. al., “Limit Cycle Suppression Technique Using Random Signal in Delta-Sigma DA Modulator”, IEEE ICSICT (Nov. 2018).

$\Delta\Sigma$ DA Converter

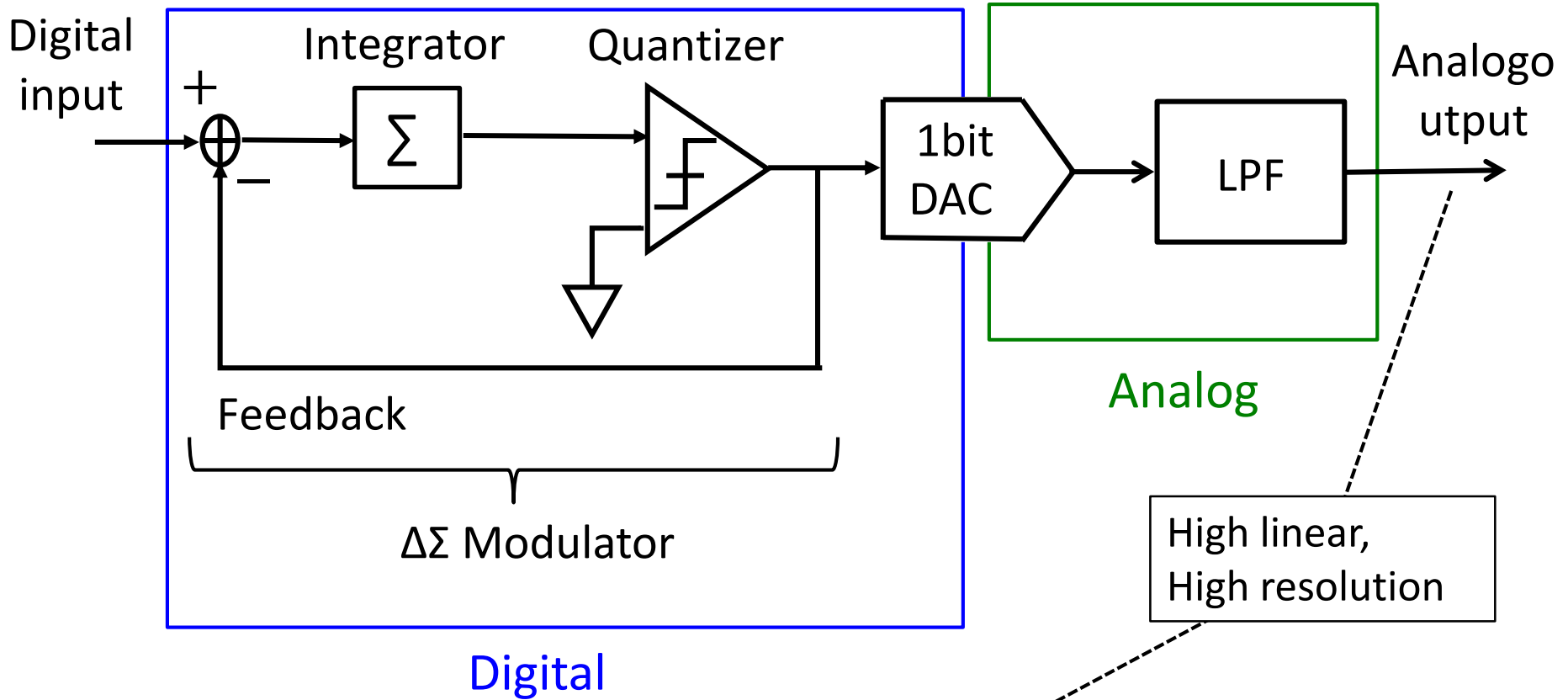


< Usage >

- Measurement
- Audio

 

Merits & Demerits of $\Delta\Sigma$ DAC

 


Merit

- Mostly digital circuit
- High linear & high resolution for low frequency signal generation

Demerit


- Limit cycle problem for small input

 

✘ Due to modulator nonlinearity by quantizer

Adding Dither at Input

Adding random signal to digital input

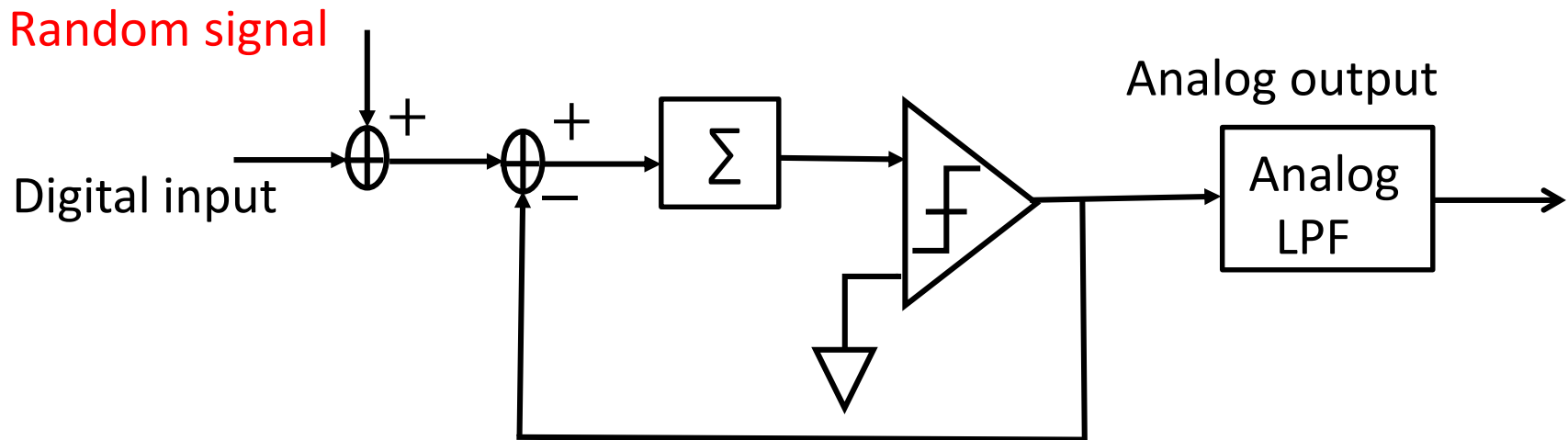

Drawbacks


- Input range sacrifice
- Random signal has to be out of signal band
➔ difficult to generate

Our Approach


Digital input

Digital dither signal

Analog output

 

 
Limit cycle reduction
with **digital dither signal**



Limit cycle




Stair

 

Smooth !

Proposed Circuit

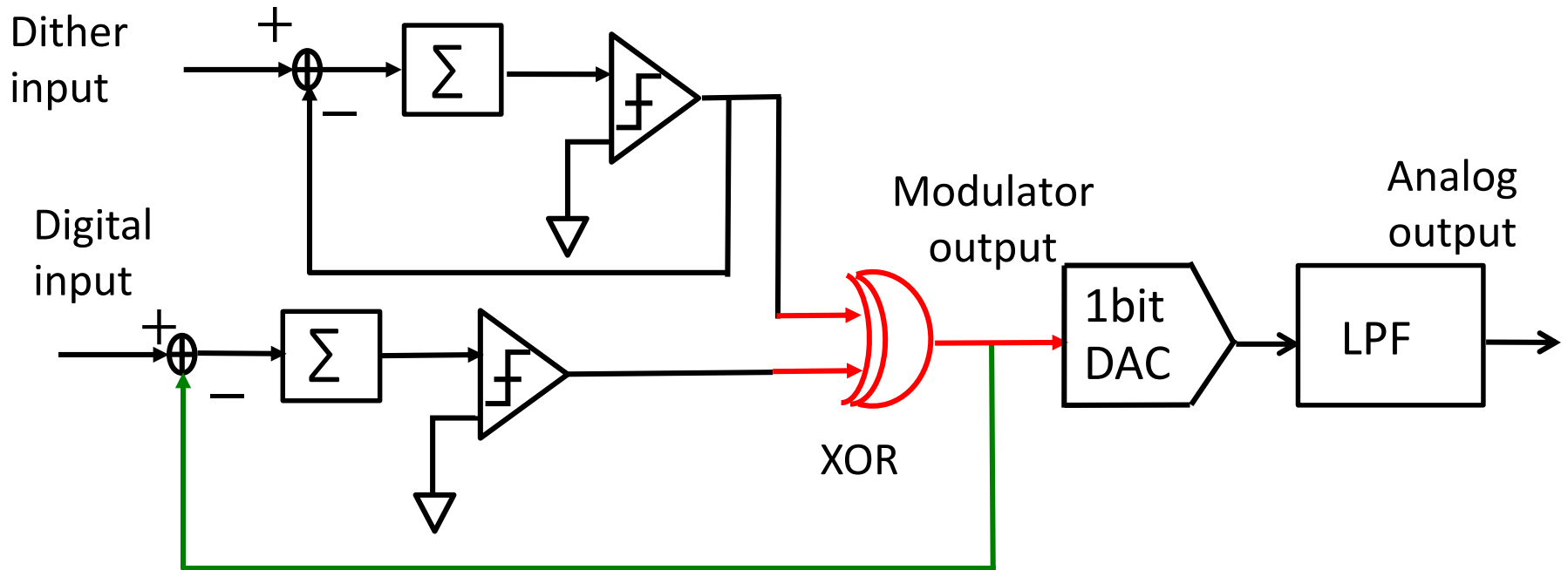

< Features >

① 1-bit output



A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

② Digital dither





NOT affect output signal,
thanks to feedback

Digital signal "1" reverses
comparator output with XOR

10-bit case



Simulation Results

Sine wave

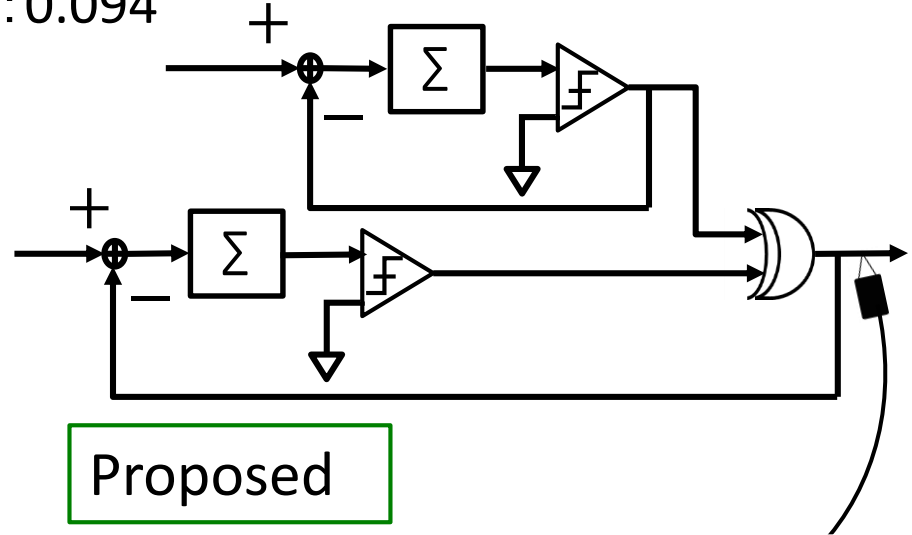 



Conventional

Proposed

  


Another Configuration

LP modulator

 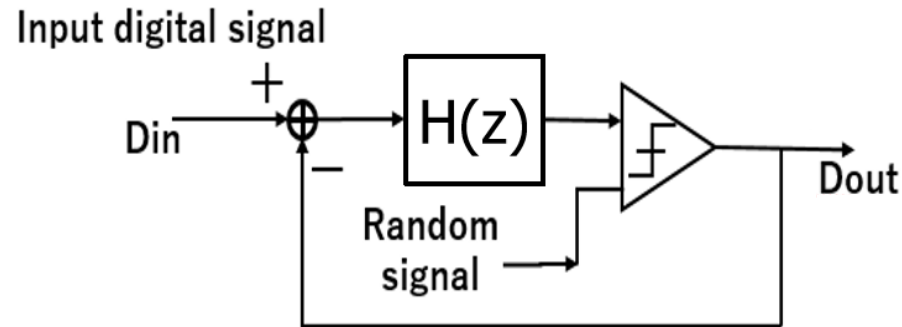


w/o dither

 


w/ dither

BP modulator

 


Modulator Operation



Without dither

 

Time domain

 


With dither

 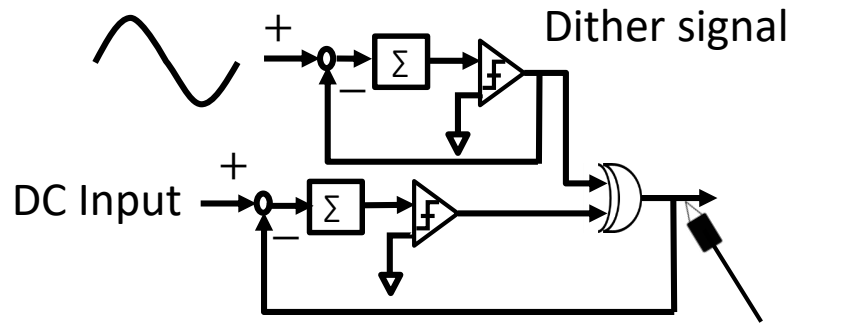

✓ Orders of '0' and '1' -> different


✓ Total numbers of 1's -> the same

Frequency domain

 

Linear




Noise

 

DC signal power -> the same


10-bit case

SFDR Comparison

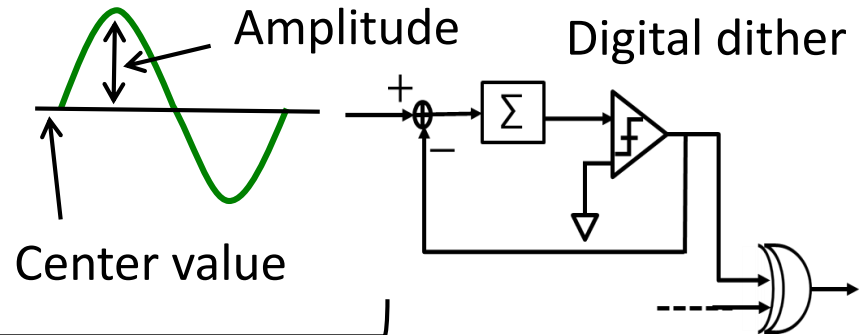  

Varying DC input

SFDR [dB]

 

With dither
Without dither



SFDR improvement
by more than 10dB


10-bit case
DC = 0.1

SFDR (Spurious Free Dynamic Range)


$$\text{SFDR} = \frac{\text{Signal Power}}{\text{Maximum Harmonics Power}}$$

$$\text{SFDR} = 5.4 \text{ dB} < 22.9 \text{ dB}$$

Conventional

 


Proposed

 

Research Objective

 
- Testing the timing between two repetitive digital signals
Ex. Data and clock
in Double Data Rate memory




- Short testing time
- Good accuracy



Implement BOST with small circuitry

 


Type I N=8 Multi-BP $\Delta\Sigma$ AD Modulator

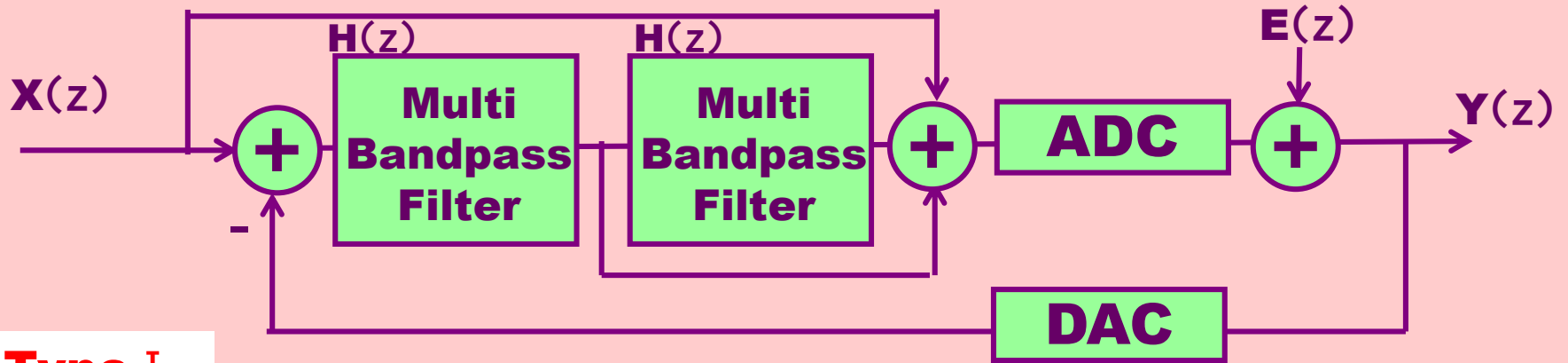

Type I

$H(z)$

$$\frac{Z^{-8}}{1-Z^{-8}}$$

 

$$STF = Z^{-8}$$



$$NTF = (1-Z^{-8})^2$$

Signal Bands :

0, 1/8, 1/4, 3/8, 1/2

$\times F_s$

  Type I N=8 Multi-BP $\Delta\Sigma$ AD Modulator Simulation Results



Modulator operation is confirmed.

Our Work

Focus on Multi-bit $\Delta\Sigma$ Time-to-Digital Converter (TDC)

- Repetitive digital signals
  $\Sigma\Delta$ TDC can be used

- Simple circuit

- Fine time resolution

- Testing time

Single-bit $\Sigma\Delta$ TDC	Long
-------------------------------	------

Multi-bit $\Sigma\Delta$ TDC	Short
------------------------------	-------

- Linearity

Single-bit $\Sigma\Delta$ TDC	Good
-------------------------------	------

Multi-bit $\Sigma\Delta$ TDC	Bad	due to delay elements mismatches
------------------------------	-----	----------------------------------



For their compensation

DWA algorithm, BOST (FPGA) verification

Conclusion

- Spectrum shaping of errors is possible with DWA algorithms.
Their hardware implementation is simple.
- The algorithm derivation is based on mathematical intuition of the researcher as well as simulation.
There are no systematic or theoretical methods.
- There are still possibilities of new algorithm.
- Dither adding at the comparator is effective.