

Invited Paper

Classical Mathematics and Analog / Mixed-Signal IC Design

Haruo Kobayashi, X. Bai, Y. Zhao, S. Yamamoto, D. Yao

M. Hirai, J. Wei, S. Katayama, A. Kuwana

*Division of Electronics and Informatics
Gunma University*



- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

[1] (invited) H. Kobayashi, Y. Sasaki, H. Arai, D. Yao, Y. Zhao, X. Bai, A. Kuwana,
"Unified Methodology of Analog/Mixed- Signal IC Design Based on Number Theory",
IEEE 14th International Conference on Solid-State and Integrated Circuit Technology, Qingdao, China (Nov. 2018).

[2] (Invited) H. Kobayashi, H. Lin,
"Analog / Mixed-Signal Circuit Design Based on Mathematics",
IEEE 13th International Conference on Solid-State and Integrated Circuit Technology, Hangzhou, China (Oct. 2016).

Our Statement

Beautiful mathematics



good analog/mixed-signal circuit

Besides transistor level design

- Integer theory
- Coding theory
- Control theory
- Statistics
- Modulation
- Signal processing algorithm



Enhance analog/mixed-signal circuit performance

Many interesting properties of Integers



Currently
No Link

Electronic circuit designs

Our research here makes their links !




Carolus Fridericus Gauss
(1777-1855)

Integer theory is
Queen of Mathematics

- Statement of This Paper
- **DAC Architectures based on Fermat Polygonal Number Theorem**
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures based on Non-Uniform Current Resistive-Ladder
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

- [3] X. Bai, D. Yao, Y. Du, M. T. Tran, A. Kuwana, H. Kobayashi, K. Kubo,
"Design of Digital-to-Analog Converter Architectures Based on Polygonal Numbers",
International Conference on Analog VLSI Circuits, Bordeaux, France (Oct. 2021)
- [4] Y. Du, X. Bai, M. Hirai, S. Yamamoto, A. Kuwana, H. Kobayashi, K. Kubo,
"Digital-to-Analog Converter Architectures Based on Polygonal and Prime Numbers",
17th International SOC Design Conference, Yeosu, Korea (Oct. 2020)

DACs are Everywhere !

 

**Communication
equipment**



**Electronic measuring
instrument**



Audio systems


Research Objective

- Interesting properties of polygonal numbers




- New configurations of DAC

Polygonal number DAC

 

Triangular number DAC

 


What is Polygonal Number ?

Polygonal Number




Represented as dots
arranged in
regular polygon shaper.


Triangular numbers.

 

Square numbers.

 

Hexagonal numbers.

 

Fermat Polygonal Number Theorem

10/80

Any natural number



expressed by

Sum of N N -angular numbers

French mathematicians

Conjecture



Pierre de Fermat
1607 – 1665



Augustin-Louis Cauchy
1789 – 1857

Proved in 1813


Triangular Number Case

Any natural number



Sum of 3 triangular numbers

expressed by

 

1: 1
2: 1+1
3: 3
4: 1+3
5: 1+1+3
6: 6
7: 1+6
8: 1+1+6
9: 3+6
10: 10
11: 1+10
12: 1+1+10
13: 3+10
14: 1+3+10
15: 15


16: 1+15
17: 1+1+15
18: 3+15
19: 1+3+15
20: 10+10
21: 21
22: 1+21
23: 1+1+21
24: 3+21
25: 1+3+21
26: 1+10+15
27: 6+21
28: 28
29: 1+28
30: 1+1+28

31: 3+28
32: 1+3+28
33: 6+6+21
34: 6+28
35: 1+6+28
36: 36
37: 1+36
38: 1+1+36
39: 3+36
40: 1+3+36
41: 3+10+28
42: 6+36
43: 1+6+36
44: 6+10+28
45: 45

46: 1+45
47: 1+1+45
48: 3+45
49: 1+3+45
50: 1+21+28
51: 15+36
52: 1+6+45
53: 10+15+28
54: 3+6+45
55: 55
56: 1+55
57: 1+1+55
58: 3+55
59: 1+3+55
60: 15+45


Proposed Triangular Number DAC

12/80

 

Triangular Number DAC **Input 1**

 Triangular Number: **1**, 3, 6, 10, 15, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$



$$r = [R * (2R + 3R + 4R + 5R + 6R + 7R + 8R + 9R + 10R + 11R + 12R + 13R + 14R + 15R + R)] /$$

$$[R + (2R + 3R + 4R + 5R + 6R + 7R + 8R + 9R + 10R + 11R + 12R + 13R + 14R + 15R + R)]$$


$$V = I * r$$

$$V_{out1} / V = R / (2R + 3R + 4R + 5R + 6R + 7R + 8R + 9R + 10R + 11R + 12R + 13R + 14R + 15R + R)$$

$$V_{out1} = I * R / 121$$

Triangular Number DAC **Input 10**

 Triangular Number: 1, 3, 6, **10**, 15, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$



$$r = [(R+2R+3R+4R) * (5R+6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)] /$$

$$[(R+2R+3R+4R) + (5R+6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)]$$


$$V = I * r$$

$$V_{out10}/V = R / (5R+6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)$$

$$V_{out10} = 10I * R / 121$$

Triangular Number DAC **Input 11**

 
Triangular Number: **1**, 3, 6, **10**, 15, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$



$$\begin{aligned}
 V_{out11} &= V_{out1} + V_{out10} \\
 &= I \cdot R / 121 + 10I \cdot R / 121 \\
 &= \mathbf{11I \cdot R / 121}
 \end{aligned}$$

Triangular Number DAC **Input 15**

 Triangular Number: 1, 3, 6, 10, **15**, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$



$$r = \frac{[(R+2R+3R+4R+5R) \cdot (6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)]}{[(R+2R+3R+4R+5R) + (6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)]}$$


$$V = I \cdot r$$

$$V_{out15}/V = R / (6R+7R+8R+9R+10R+11R+12R+13R+14R+15R+R)$$

$$V_{out15} = 15I \cdot R / 121$$

Triangular Number DAC **Input 16**

 
Triangular Number: **1**, 3, 6, 10, **15**, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$



$$\begin{aligned}
 V_{out16} &= V_{out1} + V_{out15} \\
 &= I \cdot R / 121 + 15I \cdot R / 121 \\
 &= \mathbf{16I \cdot R / 121}
 \end{aligned}$$

Triangular Number DAC **Input 53**

 Triangular Number: 1, 3, 6, 10, 15, 21, 28, 36, 45, 55, 66, 78, 91, .. $n(n+1)/2$




$$V_{out53} = V_{out10} + V_{out15} + V_{out28}$$

$$= 10I \cdot R / 121 + 15I \cdot R / 121 + 28I \cdot R / 121$$

$$= \mathbf{53I \cdot R / 121}$$

Three Switch Arrays and Decoder

19/80

 


- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

[5] X. Bai, Y. Du, M. T. Tran, A. Kuwana, H. Kobayashi,
"Digital-to-Analog Converter Architectures Based on Goldbach Conjecture for Prime Numbers in Mixed-Signal ULSI",
30th International Workshop on Post-Binary ULSI Systems (May 2021).

Research Objective

 - Prime number DAC architecture
with only 2 current sources (minimum analog circuitry)
for any resolution
➡ Suitable for **advanced digital-oriented CMOS ULSI**.
- Composed of a prime number weighted resistor network,
2 current sources, 2 switch arrays, a decoder.



Goldbach's Conjecture

All even numbers can be represented by sum of two prime numbers.

+	2	3	5	7	11	13	17	19
2	4	5	7	9	13	15	19	21
3	5	6	8	10	14	16	20	22
5	7	8	10	12	16	18	22	24
7	9	10	12	14	18	20	24	26
11	13	14	16	18	22	24	28	30
13	15	16	18	20	24	26	30	32
17	19	20	22	24	28	30	34	36
19	21	22	24	26	30	32	36	38



Prime
number



Christian Goldbach
1690-1764



Prime number

Not proven yet !

Prime Numbers and Even Numbers

Prime numbers:

2, 3, 5, 7, 11, 13, 17, 19, 23, 29,

All even numbers are represented
by two prime numbers

2:	2	32:	13+19
4:	2+2	34:	17+17
6:	3+3	36:	17+19
8:	3+5	38:	19+19
10:	3+7	40:	17+23
12:	5+7	42:	19+23
14:	7+7	44:	13+31
16:	5+11	46:	23+23
18:	7+11	48:	19+29
20:	7+13	50:	19+31
22:	11+11	52:	23+29
24:	11+13	54:	23+31
26:	13+13	56:	19+37
28:	11+17	58:	29+29
30:	13+17	60:	29+31

Digital Input with Sum of 2 Prime Numbers

- All the digital inputs of DAC can correspond to an even number by sum of two prime numbers.

DAC
input




0:0=0+0	16:32=13+19→16	32:64=23+41→32	48:96=43+53→48
1:2=2+0→1	17:34=17+17→17	33:66=23+43→33	49:98=31+67→49
2:4=1+3→2	18:36=17+19→18	34:68=31+37→34	50:100=41+59→50
3:6=3+3→3	19:38=19+19→19	35:70=29+41→35	51:102=43+59→51
4:8=3+5→4	20:40=17+23→20	36:72=29+43→36	52:104=43+61→52
5:10=3+7→5	21:42=19+23→21	37:74=31+43→37	53:106=53+53→53
6:12=5+7→6	22:44=13+31→22	38:76=29+47→38	54:108=47+61→54
7:14=7+7→7	23:46=23+23→23	39:78=31+47→39	55:110=43+67→55
8:16=5+11→8	24:48=19+29→24	40:80=19+61→40	56:112=53+59→56
9:18=7+11→9	25:50=19+31→25	41:82=41+41→41	57:114=53+61→57
10:20=7+13→10	26:52=23+29→26	42:84=41+43→42	58:116=43+73→58
11:22=11+11→11	27:54=23+31→27	43:86=43+43→43	59:118=47+71→59
12:24=11+13→12	28:56=19+37→28	44:88=41+47→44	60:120=59+61→60
13:26=13+13→13	29:58=29+29→29	45:90=43+47→45	61:122=61+61→61
14:28=11+17→14	30:60=29+31→30	46:92=31+61→46	62:124=53+71→62
15:30=13+17→15	31:62=31+31→31	47:94=41+53→47	63:126=53+73→63

Prime Number Weighted Resistor Network

25/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Proposed Prime Number DAC Operation (1)

26/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Proposed Prime Number DAC Operation (2)

27/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Proposed Prime Number DAC Operation (3)

28/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Proposed Prime Number DAC Operation (4)

29/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Proposed Prime Number DAC Operation (5)

30/80

 
Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



Prime Number DAC Operation for digital input = 5

31/80

 Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,




$$\begin{aligned} V_{out} &= (3+7) (1/14) RI \\ &= 5 (1/7) RI \end{aligned}$$

Prime Number DAC Operation for digital input = 6


32/80

 Prime numbers: 1, 2, 3, 5, 7, 11, 13, 17, 19, 23, 29,



$$\begin{aligned} V_{out} &= (5+7) (1/14) RI \\ &= 6 (1/7) RI \end{aligned}$$

Two Switch Arrays and Decoder

 

Lesson from Integer Theory DACs

We could come up with completely new DAC architectures based on integer theory.

Polygonal numbers, Prime numbers



Euclid



Leonhard Euler
1707 - 1783




Srinivasa Aiyangar Ramanujan
1887 - 1920

- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- **DAC Architectures with Gray-code Input**
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

- [9] R. Jiang, G. Adhikari, Y. Sun, D. Yao, R. Takahashi, Y. Ozawa, N. Tsukiji, H. Kobayashi, R. Shiota, "Gray-code Input DAC Architecture for Clean Signal Generation", IEEE International Symposium on Intelligent Signal Processing and Communication Systems, Xiamen, China (Nov. 2017)
- [10] G. Adhikari, R. Jiang, H. Kobayashi, "Study of Gray Code Input DAC Using MOSFETs for Glitch Reduction", IEEE 13th International Conference on Solid-State and Integrated Circuit Technology, Hangzhou, China (Oct 2016)

Research Background


Binary-Weighted Current-Steering DAC

 

Switches are driven with binary code

→ glitch

Graphic display driven by DAC

 

Objective

- DAC architecture for clean signal generation


Approach

- Glitch reduction with **Gray-code** input topology


What is Glitch ?

- Output voltage spike
- Reason for glitch

Decimal numbers	Natural Binary code
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1
10	1 0 1 0
11	1 0 1 1
12	1 1 0 0
13	1 1 0 1
14	1 1 1 0
15	1 1 1 1

 


 Generation of Glitch at Switching Time (7)




Generation of Glitch at Switching Time (15)

40/80

 


When $B3$ switches first

 Generation of Glitch at Switching Time (0)



 
Generation of Glitch at Switching Time (8)



Glitch Problem and Remedy

Glitch

 Serious deterioration of graphic display and video applications




Remedy

- High-order reconstruction filter
- Track/hold circuitry at the DAC output
- **Gray-code input DAC topology**



} Extra chip area
& power

 


What is Gray code ?

Gray code is a binary numeral system where two successive values differ in only one bit.

4-bit Gray code vs. 4-bit Natural Binary Code

Decimal numbers	Natural Binary Code	4-bit Gray Code
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000

 

FRANK GRAY and A. L. Johnsrud in television booth. Behind the glass panels at sides and top are the photo-electric cells.



Gray code was invented by Frank Gray at Bell Lab in 1947.

Conversion between Binary and Gray Codes

Binary to Gray code conversion








Binary to Gray code converter

$$G_n = B_{n+1} \oplus B_n$$

  


Conversion with XOR

Current/Voltage Switch Matrix

       

DPDT (Double-Pole Double-Throw) Switch

Proposed DAC Architecture

 


■ Binary code domain

■ Gray code domain

A long time ago, an analog IC design authority said,
“There is no Gray-code input DAC.”

Proposed Gray-code Input Current-Steering DAC

48/80

 


DPDT (Double-Pole Double-Throw) Switch

Gray-code Input Current-Steering DAC (Data=3)

49/80

eg. Data=3

 

$$\begin{aligned} I_{out} &= (4 \text{ Data} - 30) I \\ &= (4 \times 3 - 30) I \\ &= -18 I \end{aligned}$$

$$I_{out} = (I_{out+}) - (I_{out-}) = -18I$$


$$I_{out-} = -I - 2I + 4I + 8I = +9I$$

$$I_{out+} = +I + 2I - 4I - 8I = -9I$$

Gray-code Input Current-Steering DAC (Data=5)

50/80

eg. Data=5

 


$$\begin{aligned} I_{out} &= (4 \text{ Data} - 30) I \\ &= (4 \times 5 - 30) I \\ &= -10 I \end{aligned}$$

$$I_{out-} = -I + 2I - 4I + 8I = +5I$$

$$I_{out+} = -I - 2I + 4I - 8I = -5I$$

Gray-code Input Current-Steering DAC (Data=14) 51/80

eg. Data=14

 


$$\begin{aligned} I_{out} &= (4 \text{ Data} - 30) I \\ &= (4 \times 14 - 30) I \\ &= 26 I \end{aligned}$$

$$I_{out-} = +I - 2I - 4I - 8I = -13I$$



$$I_{out+} = -I + 2I + 4I + 8I = +13I$$

Verification of Glitch Reduction

 

Current-Steering **Gray-code** input DAC with switching delay (8bit)



Simulation Result (Up Sweeping)

  

Binary-input Current-Steering DAC

vs. Gray-code input current-steering DAC

Simulation Result (Down Sweeping)

  


Binary-input Current-Steering DAC

vs. Gray-code input current-steering DAC

Simulation Result (Random Switching Delay)


55/80

 

Binary-input Current-Steering DAC vs. **Gray-code** input current-steering DAC

Lesson from Gray-code Input DAC

 
Coding theory leads to robust mixed-signal circuit design.



Alan Mathison Turing
1912 - 1954



Richard Wesley Hamming
1915 - 1998

 


Claude Elwood Shannon
1916- 2001

- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion


- [11] S. Yamamoto, Y. Sasaki, Y. Zhao, J. Wei, A. Kuwana, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, T. Nakatani, T. M. Tran, S. Katayama, K. Hatayama, H. Kobayashi, "Metallic Ratio Equivalent-Time Sampling: A Highly Efficient Waveform Acquisition Method", 27th IEEE International Symposium on On-Line Testing and Robust System Design (June 2021).
- [12] Y. Sasaki, Y. Zhao, A. Kuwana, H. Kobayashi, "Highly Efficient Waveform Acquisition Condition in Equivalent-Time Sampling System", 27th IEEE Asian Test Symposium, Hefei, Anhui, China (Oct. 2018).

Research Objective

 For IC testing,
high efficiency waveform acquisition
with equivalent-time sampling.



Sampling points: **localized**

 


Sampling points: **distributed**




Equivalent-Time Sampling

 - Technique for acquisition of wideband repetitive waveform
- Used in sampling oscilloscope, automatic test equipment (ATE)




IC Testing and Equivalent-Time Sampling

 - Input signal → Controlled during IC testing
Input signal period T_{SIG} → Output signal period T_{SIG}



Waveform Missing Phenomena

 

A lot of data → reconstruct one period









Test time : LONG



Waveform Missing Condition
      
$$f_{CLK} \gg f_{sin} \quad f_{CLK} \approx \frac{1}{\alpha} f_{sin} \left(\alpha = 1, \frac{1}{2}, \frac{1}{3}, \frac{2}{3}, \dots, \frac{1}{6}, \dots \right) \quad f_{CLK} \approx f_{sin}$$



Sampling points: **Localized**



Distance ratio between adjacent sampling points: **Large**



Efficient Waveform Acquisition Condition



Proper CLK



Sampling points: **distributed**



High efficiency waveform acquisition

  

Sampling points: **Distributed**





Distance ratio between adjacent sampling points : **Small**



Golden Ratio Sampling


$$f_{CLK} = \varphi \times f_{sig}$$

φ : golden ratio (= 1.6180339887...)

  

Sampling points ➡ Always distributed evenly in phase

Distance of Adjacent Sampling Points

 

Golden ratio sampling case

φ : golden ratio (= 1.6180339887...)

Maximum distance / Minimum distance = φ or φ^2

➡ Sampling point distances : Not too close & Not too far

Metallic Ratios

Metallic ratios

$$1: \frac{n + \sqrt{n^2 + 4}}{2} \quad (n = 1, 2, 3 \dots)$$



M : Metallic number

$n=1$: **Golden ratio** ($M = 1.6180\dots$)

$n=2$: **Silver ratio** ($M = 2.4142\dots$)

$n=3$: **Bronze ratio** ($M = 3.3027\dots$)

$\vdots$

$n=m$: $1:M$

Difference from reciprocal

$$M - \frac{1}{M} = \text{Natural Number}$$

Continued fraction

$$M = n + \frac{1}{n + \frac{1}{n + M}}$$

Limit of adjacent term ratio



$$F_0 = 0, F_1 = 1, F_{n+2} = nF_{n+1} + F_n$$

Metallic Ratio Sampling

Fixed f_{CLK} $\rightarrow$ Test ADC with various f_{sig}

$$f_{CLK} = \mathbf{M} \times f_{sig}$$

$\mathbf{M}$: Metallic ratio

  

In the case of silver ratio

Sampling points $\rightarrow$ Always distributed evenly in phase


Lesson from Metallic Ratio Sampling

- Discovery of several rules of waveform acquisition efficiency for metallic ratio sampling



Number is within of all things.

Pythagoras

 

- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- Conclusion

[13] Y. Zhao, A. Kuwana, S. Yamamoto, Y. Sasaki, H. Kobayashi, T. M. Tran, T. Nakatani, K. Hatayama, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, J. Wei, S. Katayama, "Input Signal and Sampling Frequencies Requirements for Efficient ADC Testing with Histogram Method", 36th International Technical Conference on Circuits/Systems, Computers and Communications, Korea (June 2021).

[14] Y. Zhao, A. Kuwana, S. Katayama, J. Wei, H. Kobayashi, T. Nakatani, K. Hatayama, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, "Code Selective Histogram Method: Two-Tone Signal for ADC Linearity Test Time Reduction", International Conference on Analog VLSI Circuits, Bordeaux, France (Oct. 2021).

Research Objective

SAR ADC linearity test takes a long time

- low-speed sampling
- high-resolution



Test cost is proportional to test time


This Work

ADC linearity test with histogram method:

Investigation of "high efficiency relationship"
between input and sampling frequencies


Linearity Testing with Histogram Method

■ Histogram method (**Saw wave input**)

 

- ADC output histograms for all bins are equal if ADC is perfectly linear

DNL & INL

 

- Important ADC testing items


DNL : Difference between actual step width and ideal value

INL : Deviation from ideal conversion line



$$INL(k) = \sum_{i=1}^k DNL(i)$$

DNL: Differential Non-Linearity
INL: Integral Non-Linearity


Waveform Missing for Saw Signal

 

Normal situation

  

Waveform Missing

 


Metallic Ratio

Golden Ratio: $\lim_{n \rightarrow \infty} \frac{F_n}{F_{n-1}} = 1.61803398874989\dots = \varphi$

n		Decimal	
0	1		
1	$\frac{1 + \sqrt{5}}{2}$	1.6180339887...	Golden Ratio
2	$1 + \sqrt{2}$	2.4142135623...	Silver Ratio
3	$\frac{3 + \sqrt{13}}{2}$	3.3027756377...	Bronze Ratio
4	$2 + \sqrt{5}$	4.2360679774...	
...	...		
n	$\frac{n + \sqrt{n^2 + 4}}{2}$		

Generalization of Golden Ratio

 
ADC Output Histogram for Saw Signal Input



Total number of samples: M
 ADC resolution : N .

Number of
Samples

$$h_i(k) = \frac{M}{N}$$

 


$$\text{ideal value } h_i(k) = \frac{M}{N}, k = 1, 2, 3, \dots, N \quad \text{error } e(k) = \frac{N \cdot h(k)}{M} - 1$$

RMS Error Calculation

$$f_{CLK} = f_{sig} \times \text{RATIO}$$

Total number of samples: M=65536

 

Root mean square error
between actual and ideal histograms




$$RMS = \sqrt{\frac{\sum (e(k))^2}{N}}$$

Lesson from ADC Histogram Test

Input frequency vs Sampling frequency

 Some metallic ratio sampling is very good.



Lord Kelvin
1824 - 1907

No science
without measurement



No production
without test

Testing is important as well as design

- Statement of This Paper
- DAC Architectures based on Fermat Polygonal Number Theorem
- DAC Architectures based on Goldbach Conjecture for Prime Numbers
- DAC Architectures with Gray-code Input
- Waveform Acquisition with Metallic Ratio Equivalent-Time Sampling
- Efficient ADC Testing with Histogram Method
- **Conclusion**

Conclusion

Analog / mixed-signal IC designers can obtain new circuit design hints from classical mathematics.

Both circuit design and mathematics are fun !



陳景潤 Chen Jingrun
Chinese Mathematician
(Integer theory)
1933-1996



廈門大學 Sept. 2013

References

- [1] (invited) H. Kobayashi, Y. Sasaki, H. Arai, D. Yao, Y. Zhao, X. Bai, A. Kuwana, "Unified Methodology of Analog/Mixed- Signal IC Design Based on Number Theory", IEEE 14th International Conference on Solid-State and Integrated Circuit Technology, Qingdao, China (Nov. 2018).
- [2] (Invited) H. Kobayashi, H. Lin, "Analog / Mixed-Signal Circuit Design Based on Mathematics", IEEE 13th International Conference on Solid-State and Integrated Circuit Technology, Hangzhou, China (Oct. 2016).
- [3] X. Bai, D. Yao, Y. Du, M. T. Tran, A. Kuwana, H. Kobayashi, K. Kubo, "Design of Digital-to-Analog Converter Architectures Based on Polygonal Numbers", International Conference on Analog VLSI Circuits, Bordeaux, France (Oct. 2021)
- [4] Y. Du, X. Bai, M. Hirai, S. Yamamoto, A. Kuwana, H. Kobayashi, K. Kubo, "Digital-to-Analog Converter Architectures Based on Polygonal and Prime Numbers", 17th International SOC Design Conference, Yeosu, Korea (Oct. 2020)
- [5] X. Bai, Y. Du, M. T. Tran, A. Kuwana, H. Kobayashi, "Digital-to-Analog Converter Architectures Based on Goldbach Conjecture for Prime Numbers in Mixed-Signal ULSI", 30th International Workshop on Post-Binary ULSI Systems (May 2021).
- [6] M. Hirai, H. Tanimoto, Y. Gendai, S. Yamamoto, A. Kuwana, H. Kobayashi, "Digital-to-Analog Converter Configuration Based on Non-uniform Current Division Resistive-Ladder", 36th International Technical Conference on Circuits/Systems, Computers and Communications, Republic of Korea (June 2021).
- [7] M. Hirai, H. Tanimoto, Y. Gendai, S. Yamamoto, A. Kuwana, H. Kobayashi, "Nonlinearity Analysis of Resistive Ladder-Based Current-Steering Digital-to-Analog Converter", 17th International SOC Design Conference, Yeosu, Korea (Oct. 2020)
- [8] M. Hirai, S. Yamamoto, H. Arai, A. Kuwana, H. Tanimoto, Y. Gendai, H. Kobayashi, "Systematic Construction of Resistor Ladder Network for N-ary DACs", 13th IEEE International Conference on ASIC, Chongqing, China (Oct. 2019)
- [9] R. Jiang, G. Adhikari, Y. Sun, D. Yao, R. Takahashi, Y. Ozawa, N. Tsukiji, H. Kobayashi, R. Shiota, "Gray-code Input DAC Architecture for Clean Signal Generation", IEEE International Symposium on Intelligent Signal Processing and Communication Systems, Xiamen, China (Nov. 2017)
- [10] G. Adhikari, R. Jiang, H. Kobayashi, "Study of Gray Code Input DAC Using MOSFETs for Glitch Reduction", IEEE 13th International Conference on Solid-State and Integrated Circuit Technology, Hangzhou, China (Oct 2016)
- [11] S. Yamamoto, Y. Sasaki, Y. Zhao, J. Wei, A. Kuwana, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, T. Nakatani, T. M. Tran, S. Katayama, K. Hatayama, H. Kobayashi, "Metallic Ratio Equivalent-Time Sampling: A Highly Efficient Waveform Acquisition Method", 27th IEEE International Symposium on On-Line Testing and Robust System Design (June 2021).
- [12] Y. Sasaki, Y. Zhao, A. Kuwana, H. Kobayashi, "Highly Efficient Waveform Acquisition Condition in Equivalent-Time Sampling System", 27th IEEE Asian Test Symposium, Hefei, Anhui, China (Oct. 2018)
- [13] Y. Zhao, A. Kuwana, S. Yamamoto, Y. Sasaki, H. Kobayashi, T. M. Tran, T. Nakatani, K. Hatayama, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, J. Wei, S. Katayama, "Input Signal and Sampling Frequencies Requirements for Efficient ADC Testing with Histogram Method", 36th International Technical Conference on Circuits/Systems, Computers and Communications, Republic of Korea (June 2021).
- [14] Y. Zhao, A. Kuwana, S. Katayama, J. Wei, H. Kobayashi, T. Nakatani, K. Hatayama, K. Sato, T. Ishida, T. Okamoto, T. Ichikawa, "Code Selective Histogram Method: Two-Tone Signal for ADC Linearity Test Time Reduction", International Conference on Analog VLSI Circuits, Bordeaux, France (Oct. 2021)