

Bridge-less Power Factor Correction Converter with Adaptive Switching Pulse Enabling Control

Ahmad Bustoni, Noriyuki Oiwa, Shotaro Sakurai,
Yifei Sun, Yasunori Kobori, Haruo Kobayashi

Division of Electronics and Informatics
Gunma University



Outline


- Background and Purpose
- Basic PFC Circuit
- Conventional PFC (Half-bridgeless) Circuit
- Proposed PFC (Full-bridgeless) Circuit
- Conclusion

Outline

- **Background and Purpose**
- Basic PFC Circuit
- Conventional PFC (Half-bridgeless) Circuit
- Proposed PFC (Full-bridgeless) Circuit
- Conclusion



What is Power Supply Circuit ?

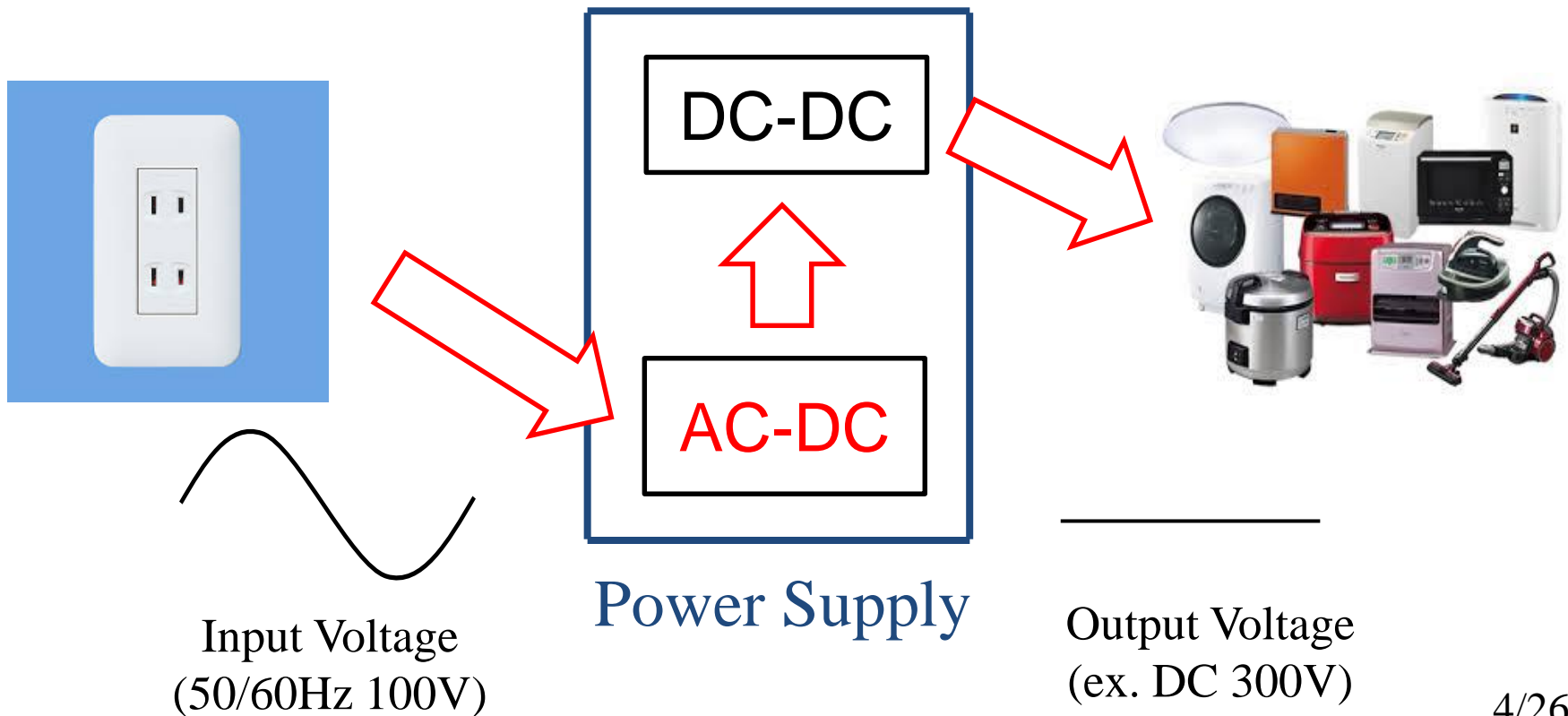- Commercial power supply circuits
→ Convert AC into DC voltages





PFC Circuit

PFC shapes input current waveform


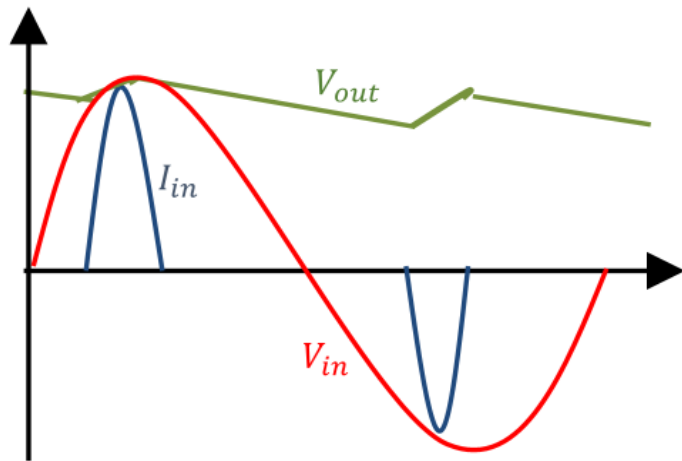
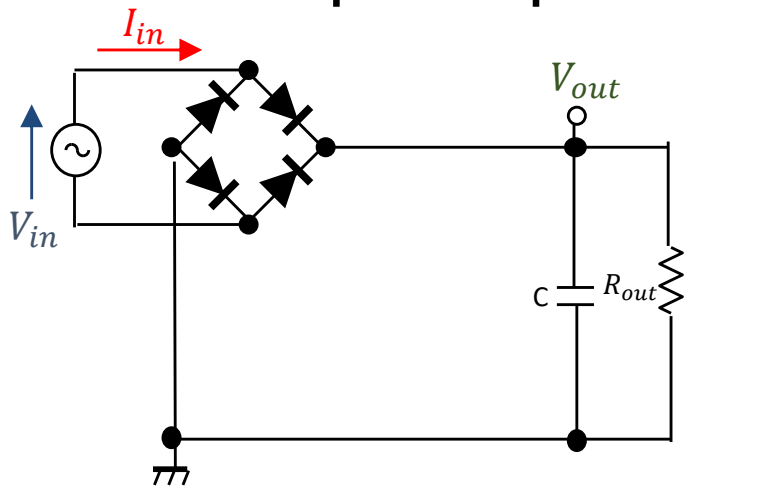


Without PFC

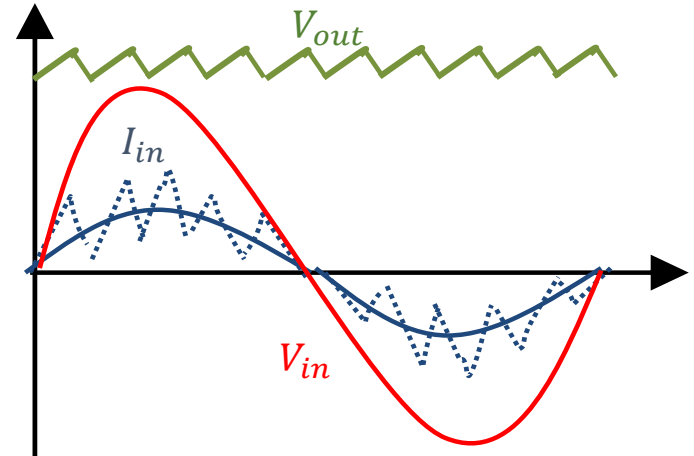
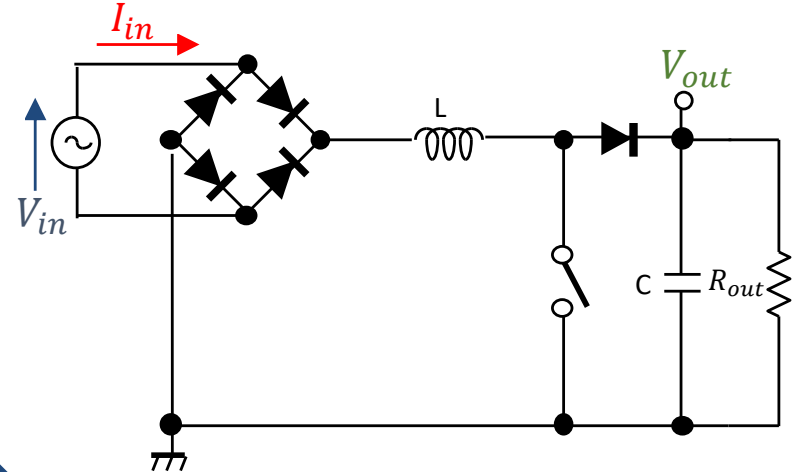


With PFC

Research Purpose

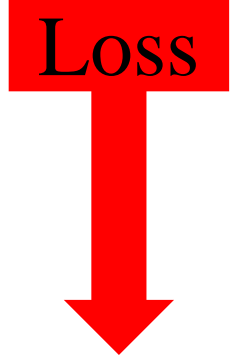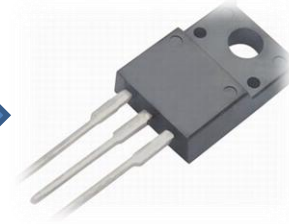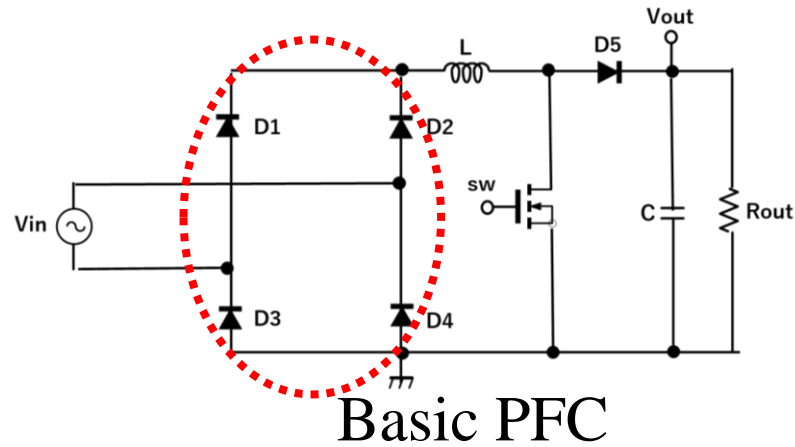

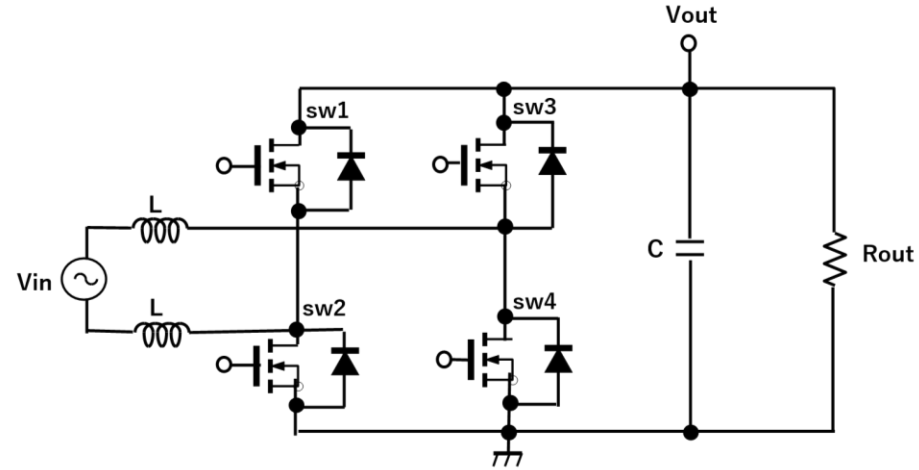
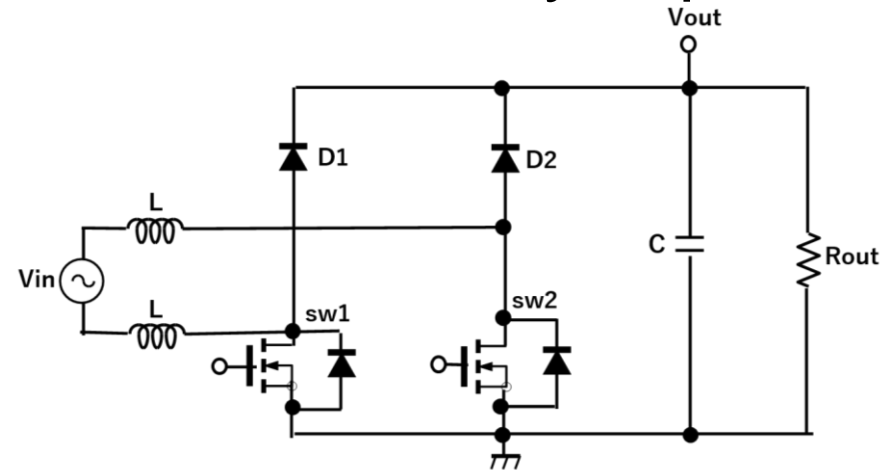
● Efficiency improvement in PFC converter




Outline

- Background and Purpose
- **Basic PFC Circuit**
- Conventional PFC (Half-bridgeless) Circuit
- Proposed PFC (Full-bridgeless) Circuit
- Conclusion

Basic PFC Circuit

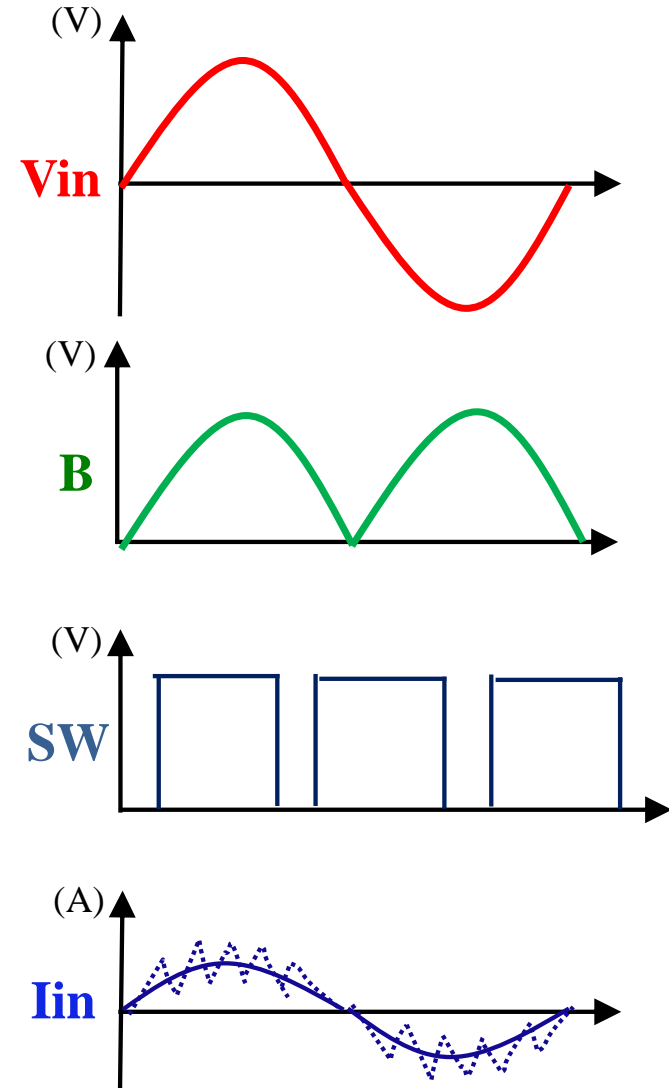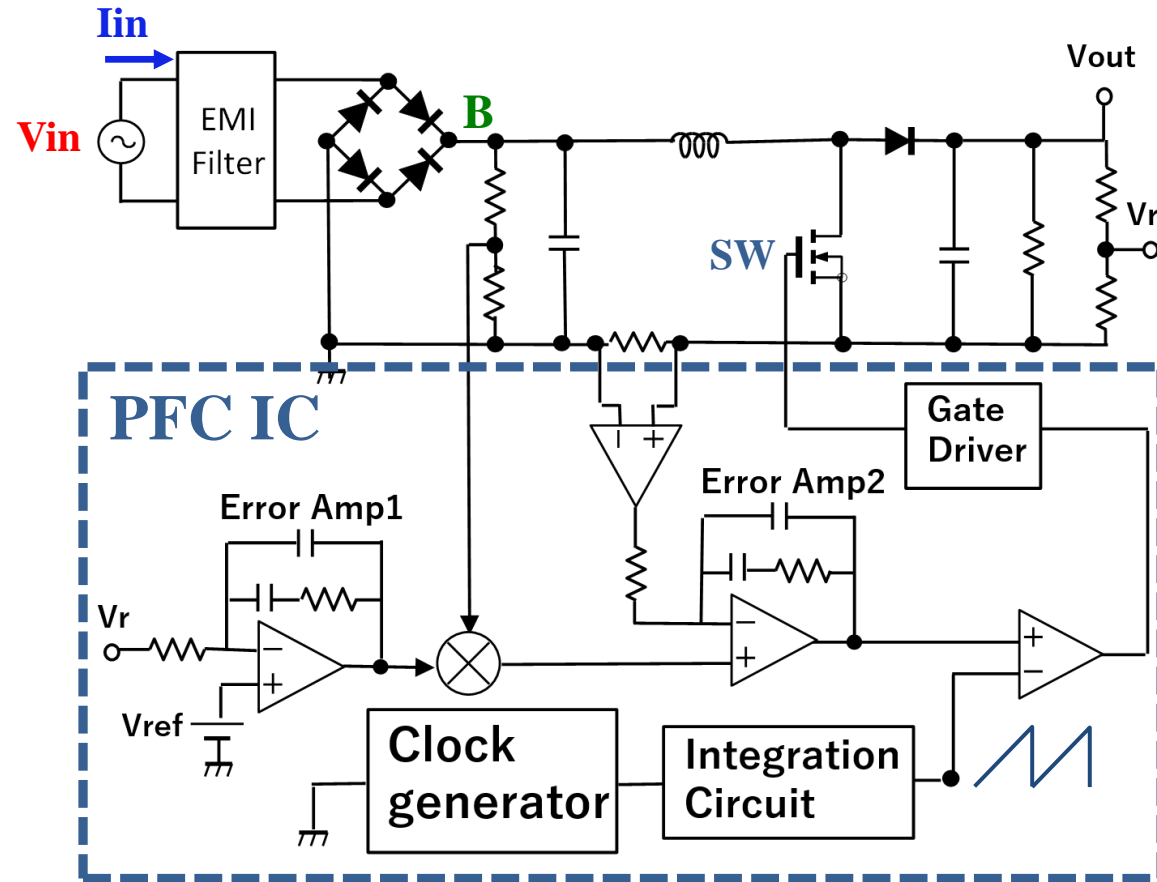

Efficiency of Basic PFC

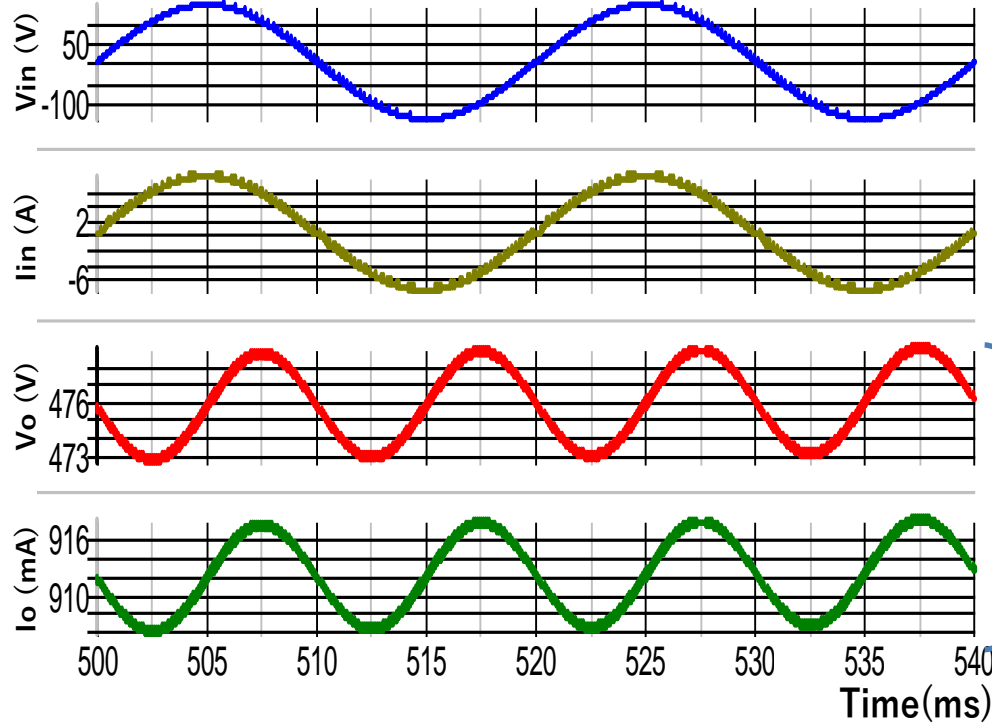

AC $V_{in}=100[V]$ @50Hz

Parameters	Simulation Value
I_{in}	5.26[A]
Input power	526[W]
Output power	434[W]

Expand

$$V_o = 476V \pm 3V$$
$$I_o = 912mA \pm 6mA$$


$$\text{efficiency} = \frac{\text{Output power}}{\text{Input power}} \times 100 = \frac{434}{526} \times 100$$
$$= 82.5\%$$

Outline

- Background and Purpose
- Basic PFC Circuit
- **Conventional PFC (Half-bridgeless) Circuit**
- Proposed PFC (Full-bridgeless) Circuit
- Conclusion

Half-Bridgeless Circuit


MOSFET → efficiency **increase**

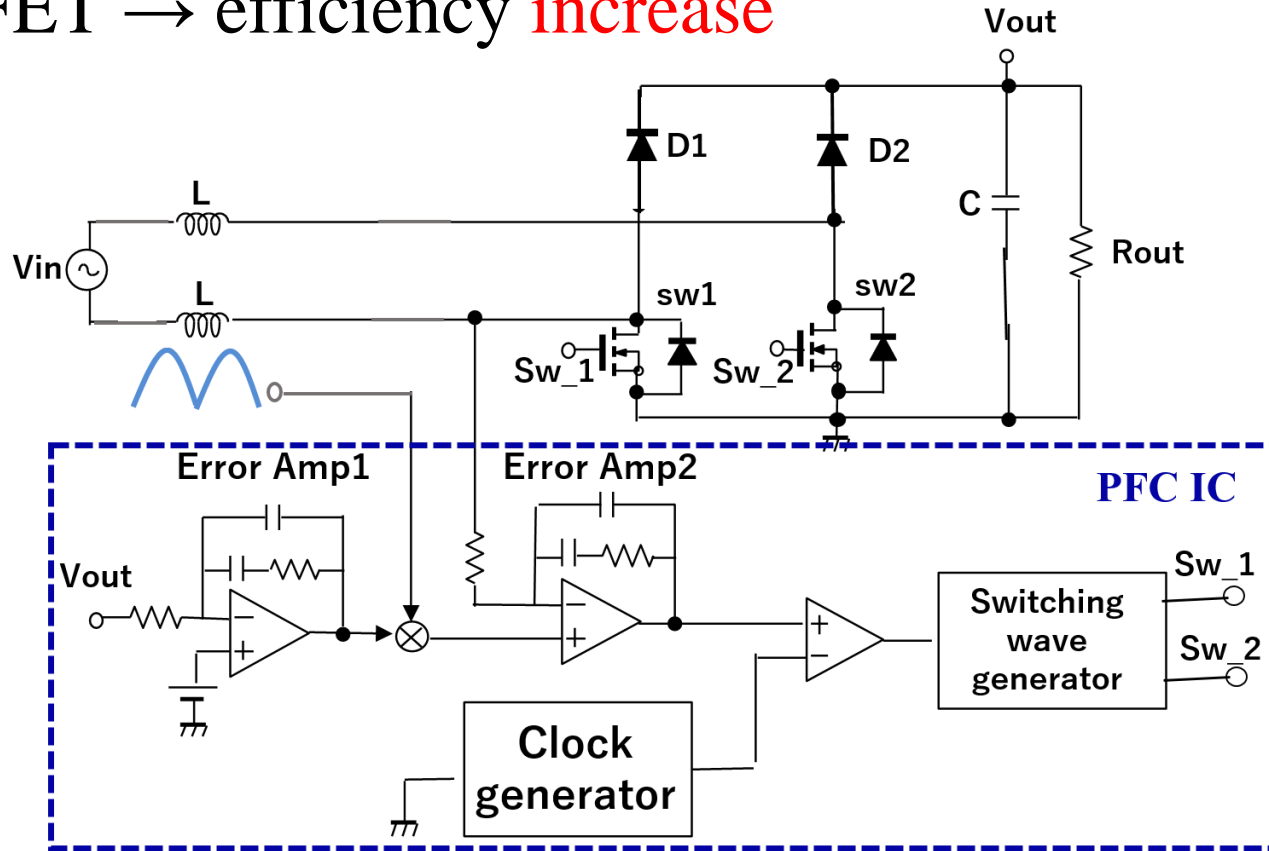

Conditions

- $V_{in} = 100[V_{rms}] @ 50Hz$
- Clock frequency = 200[kHz]
- $L = 1[mH]$
- $C = 500[uF]$
- $R_{DS(on)} = 1[m\Omega]$

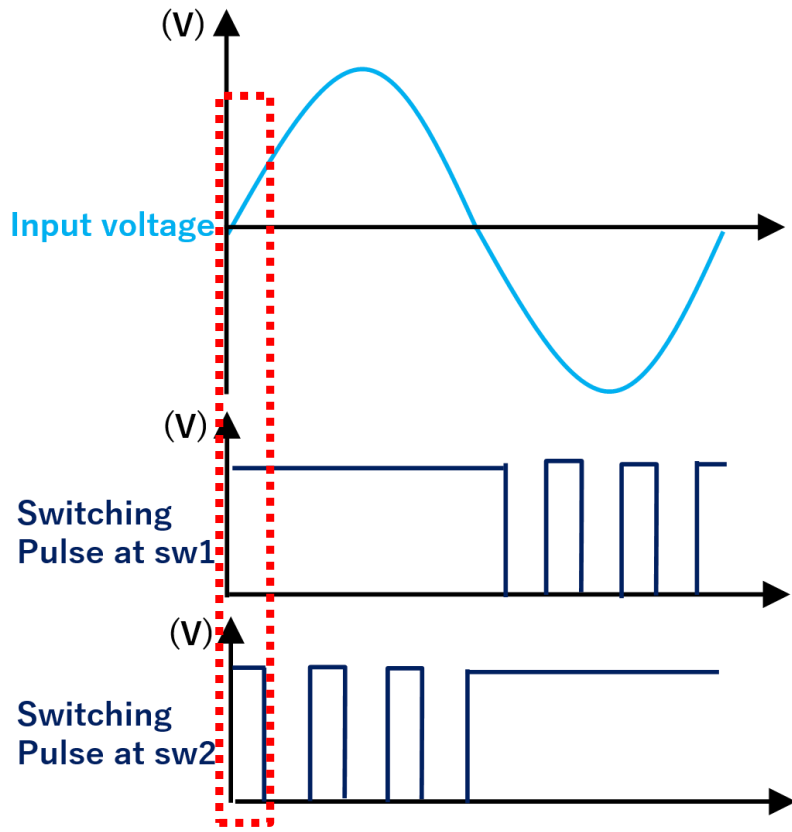
Operation of Half-Bridgeless Circuit (1/2)




$V_{in} > 0$

sw1 \rightarrow ON

sw2 \rightarrow ON

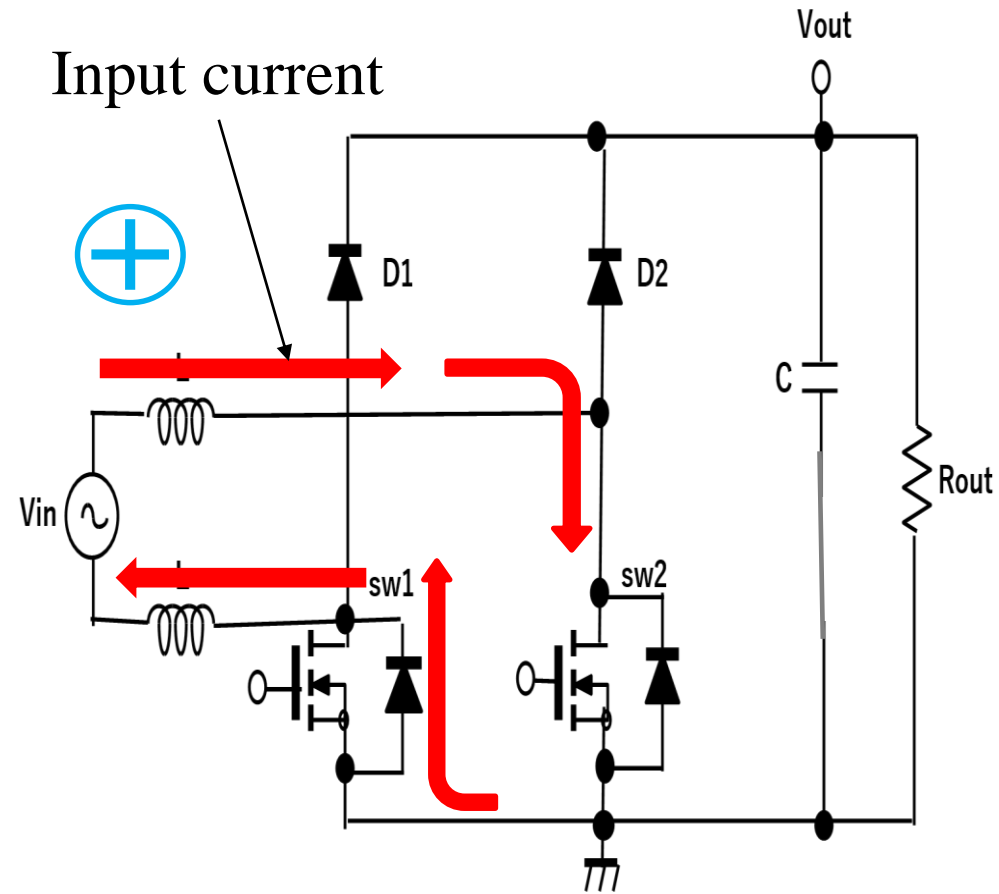

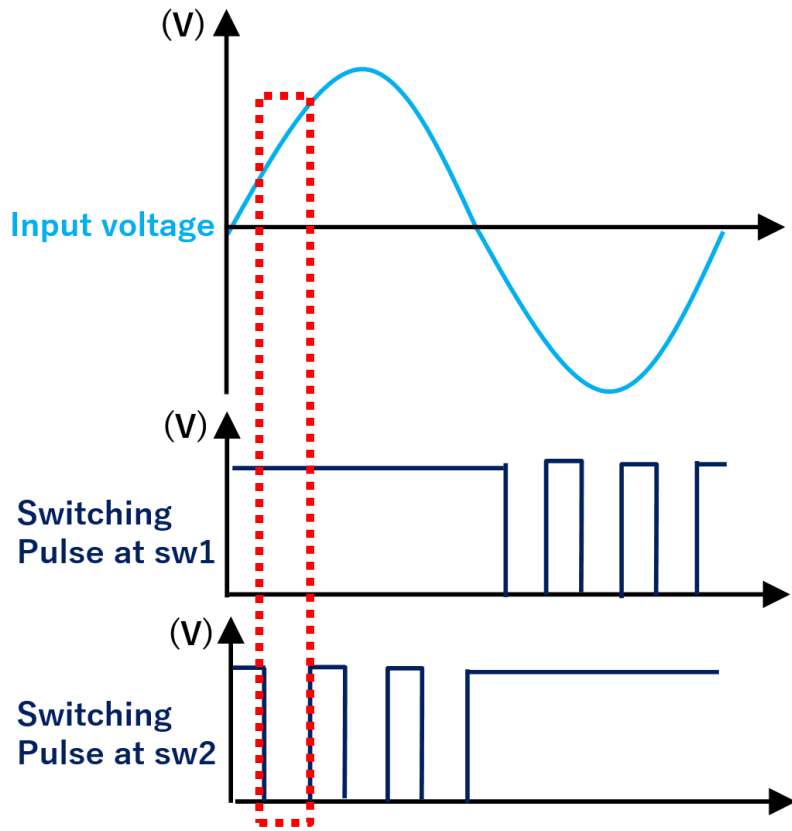Operation of Half-Bridgeless Circuit (2/2)




$V_{in} > 0$

sw1 \rightarrow ON


sw2 \rightarrow OFF

Boost Converter

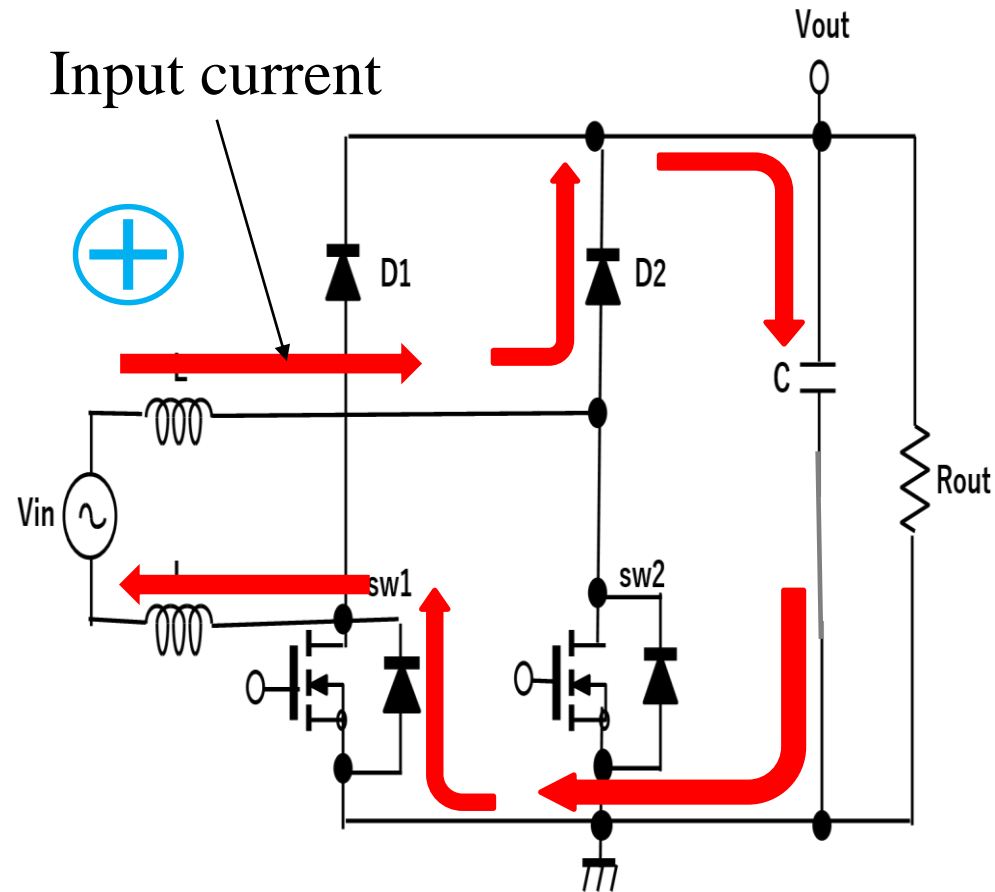

Efficiency of Half-Bridgeless PFC

AC $V_{in}=100[V]$ @50Hz

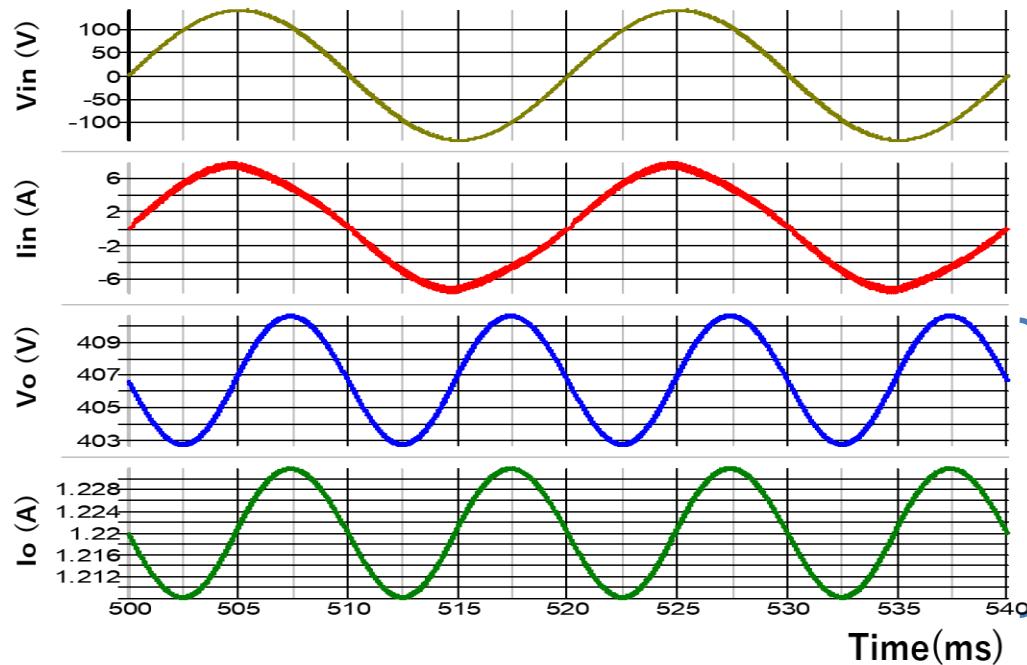

Parameters	Simulation Value
I_{in}	5.26[A]
Input power	526[W]
Output power	496[W]

Expand

$$V_o = 406.5V \pm 4V$$

$$I_o = 1.22A \pm 0.012A$$


$$\begin{aligned}
 \text{efficiency} &= \frac{\text{Output power}}{\text{Input power}} \times 100 = \frac{496}{526} \times 100 \\
 &= 94.3\% \quad (> 82.5\% \text{ Basic})
 \end{aligned}$$

Outline

- Background and Purpose
- Basic PFC Circuit
- Conventional PFC (Half-bridgeless) Circuit
- **Proposed PFC (Full-bridgeless) Circuit**
- Conclusion

Proposed Full-Bridgeless Circuit

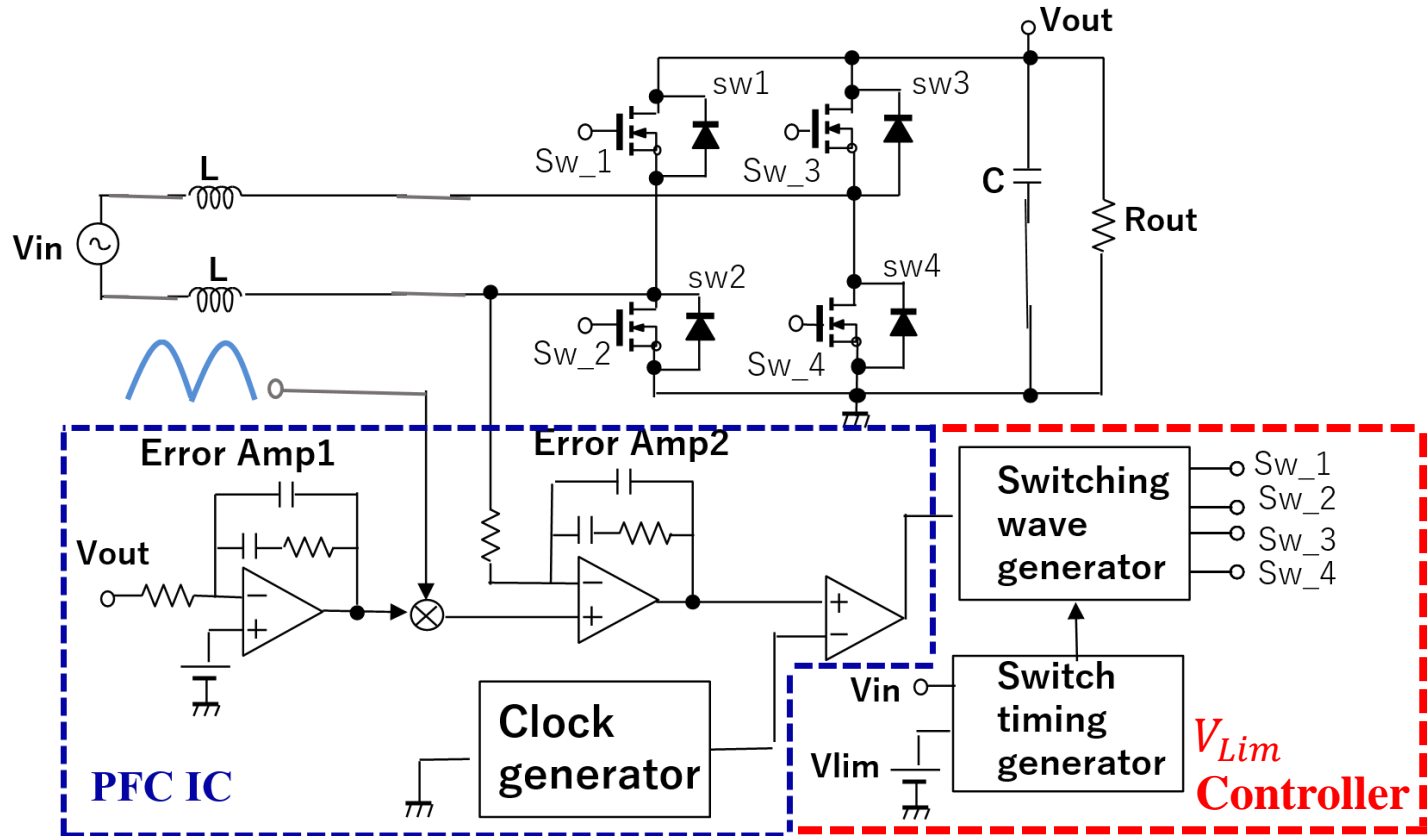V_{Lim} Controller → Prevention of reverse current of sw1 or sw3





Conditions

- $V_{in} = 100[V_{rms}]@50Hz$
- $C = 500[\mu F]$
- Clock frequency = 200[kHz]
- $R_{DS(on)} = 1[m\Omega]$
- $L = 1[mH]$



Reverse Current

- Without V_{Lim} controller circuit

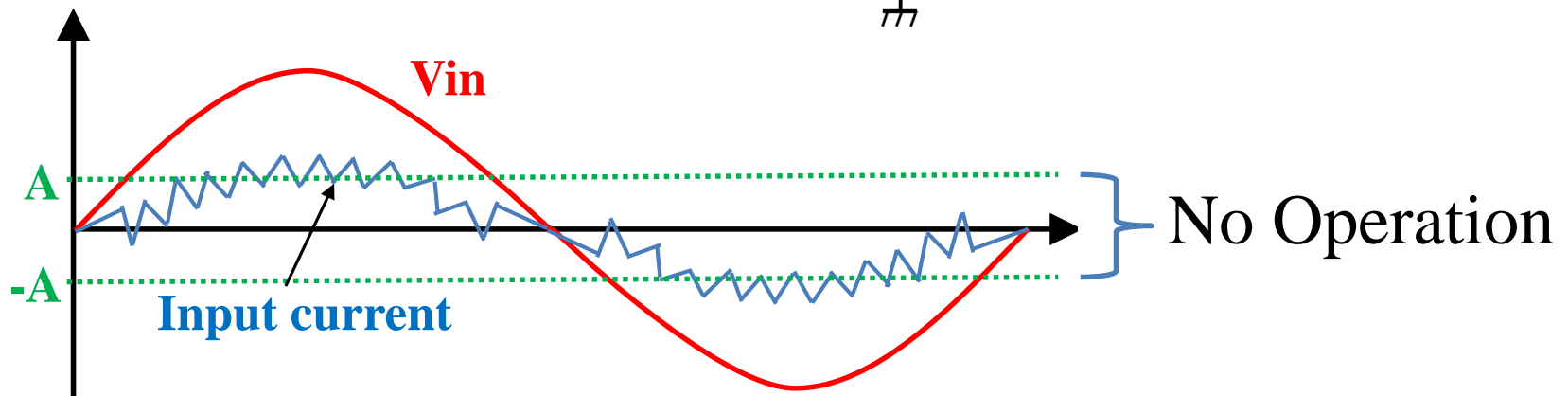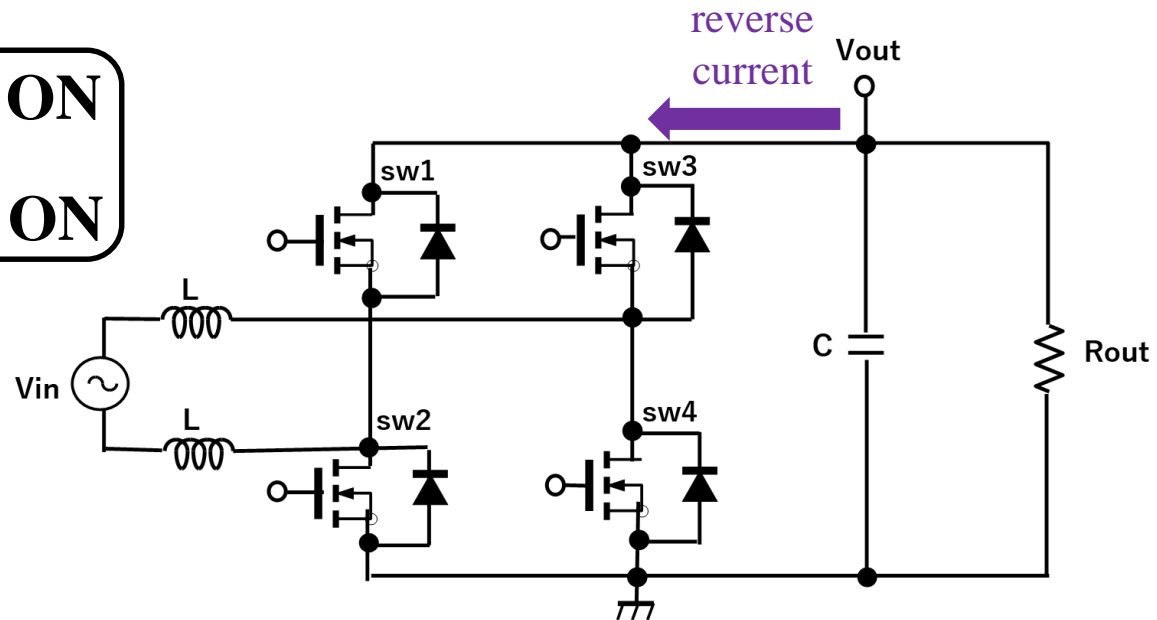$V_{in} < A$ & sw3 ON
 $V_{in} > -A$ & sw1 ON



V_{Lim} controller circuit

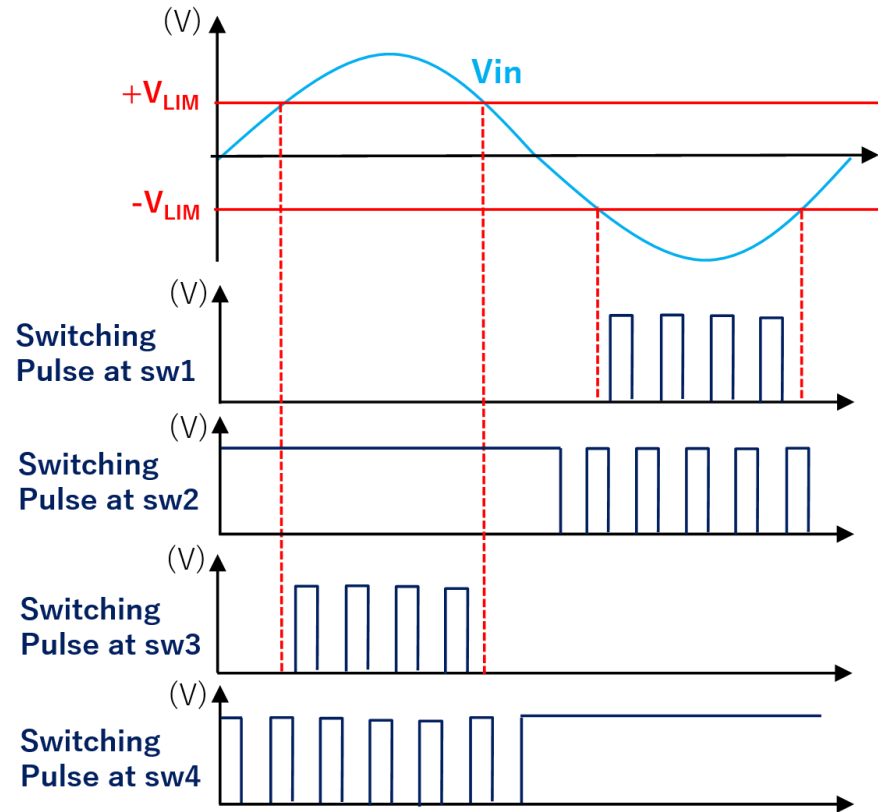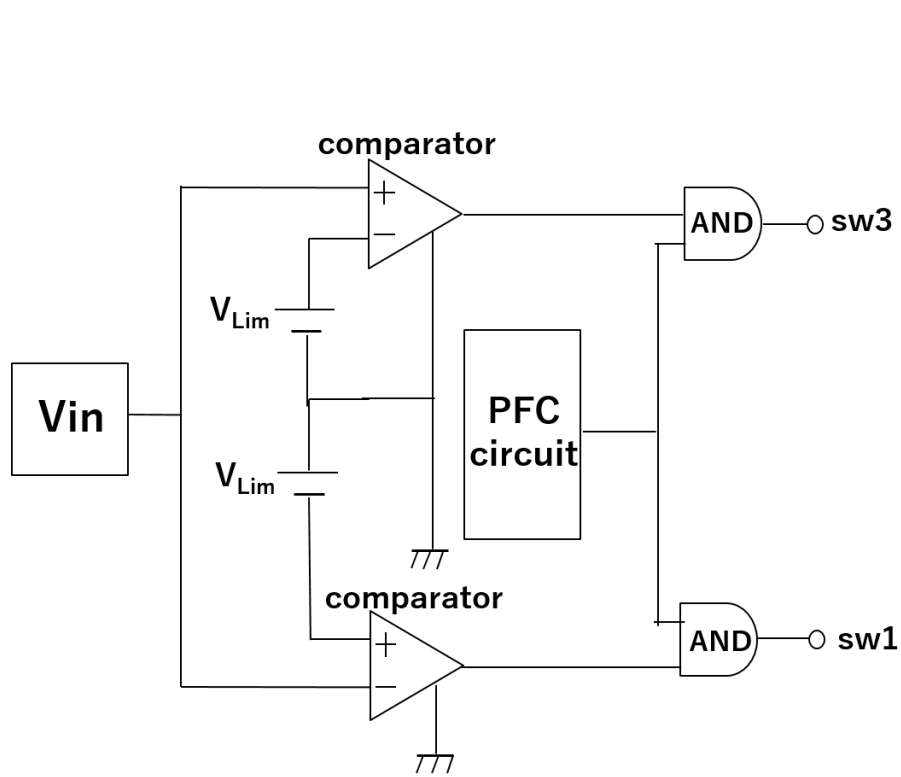

$V_{in} < V_{Lim}$ \longrightarrow sw3 OFF

$V_{in} > -V_{Lim}$ \longrightarrow sw1 OFF

Operation of Full-Bridgeless Circuit (1/4)



$$V_{in} < V_{Lim}$$

sw1 → OFF

sw2 → ON

sw3 → OFF

sw4 → ON

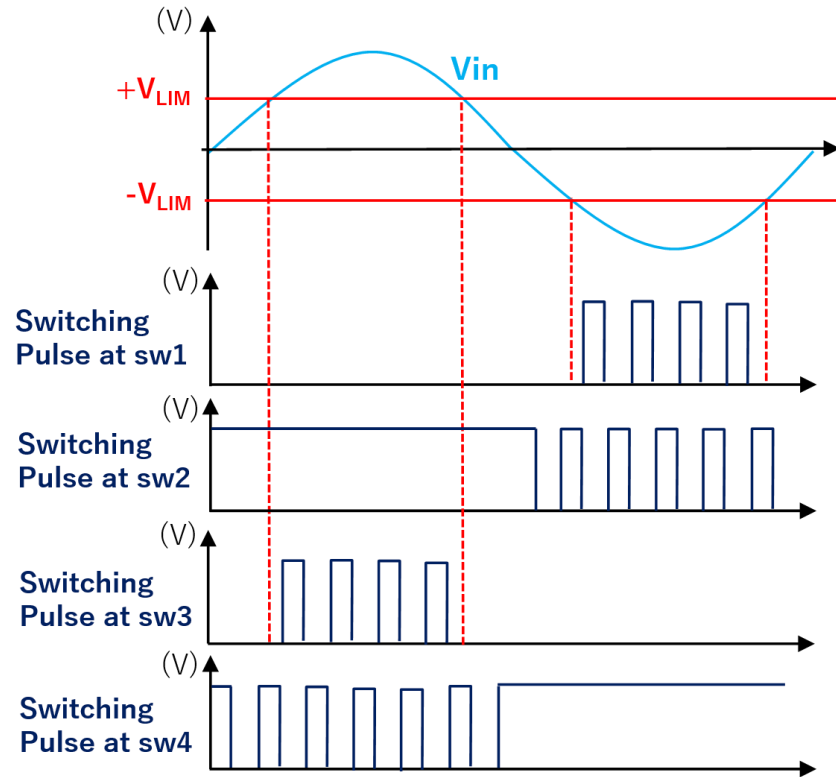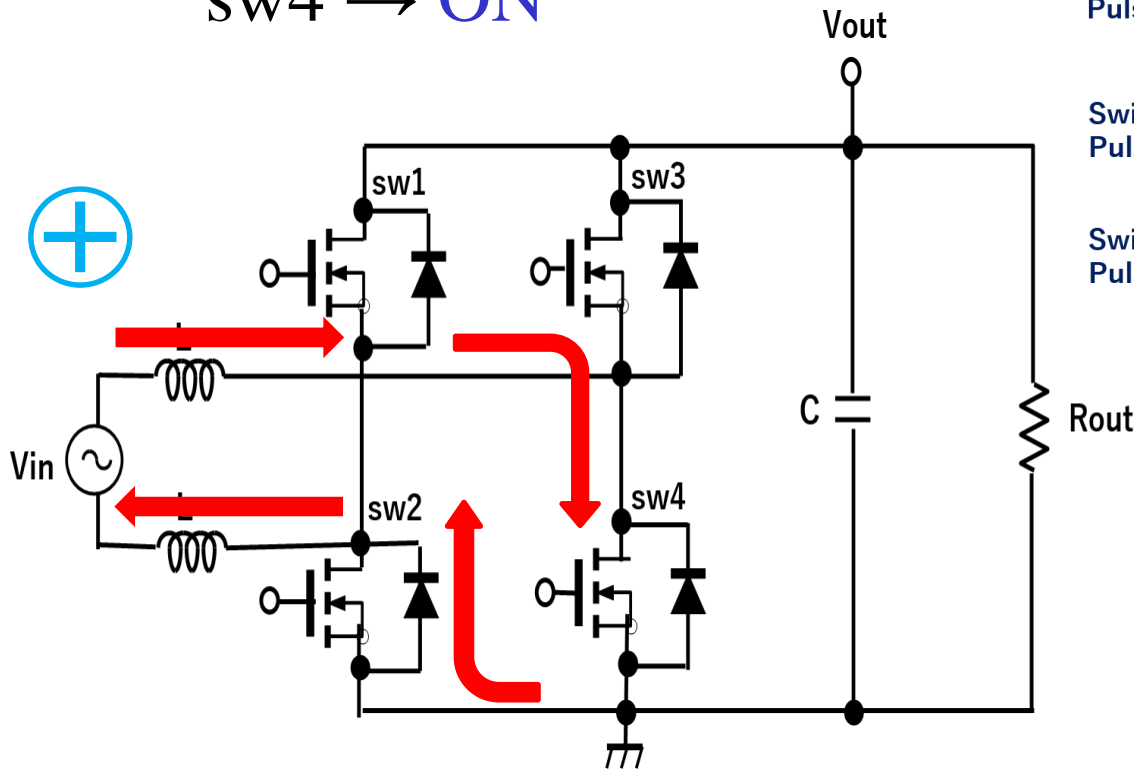

Operation of Full-Bridgeless Circuit (2/4)



$$V_{in} < V_{Lim}$$

sw1 → OFF

sw2 → ON

sw3 → OFF

sw4 → OFF

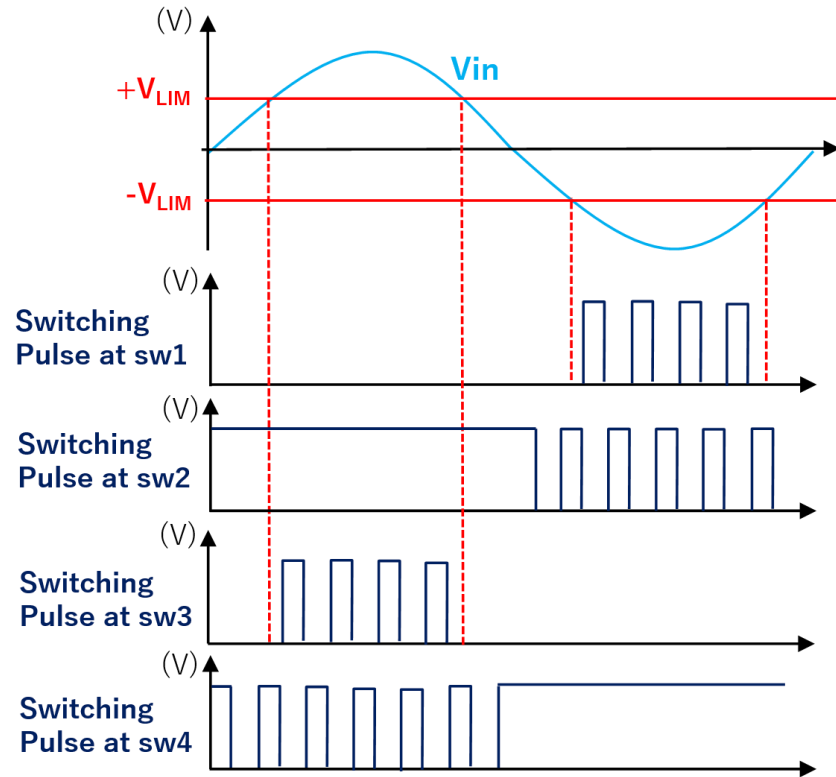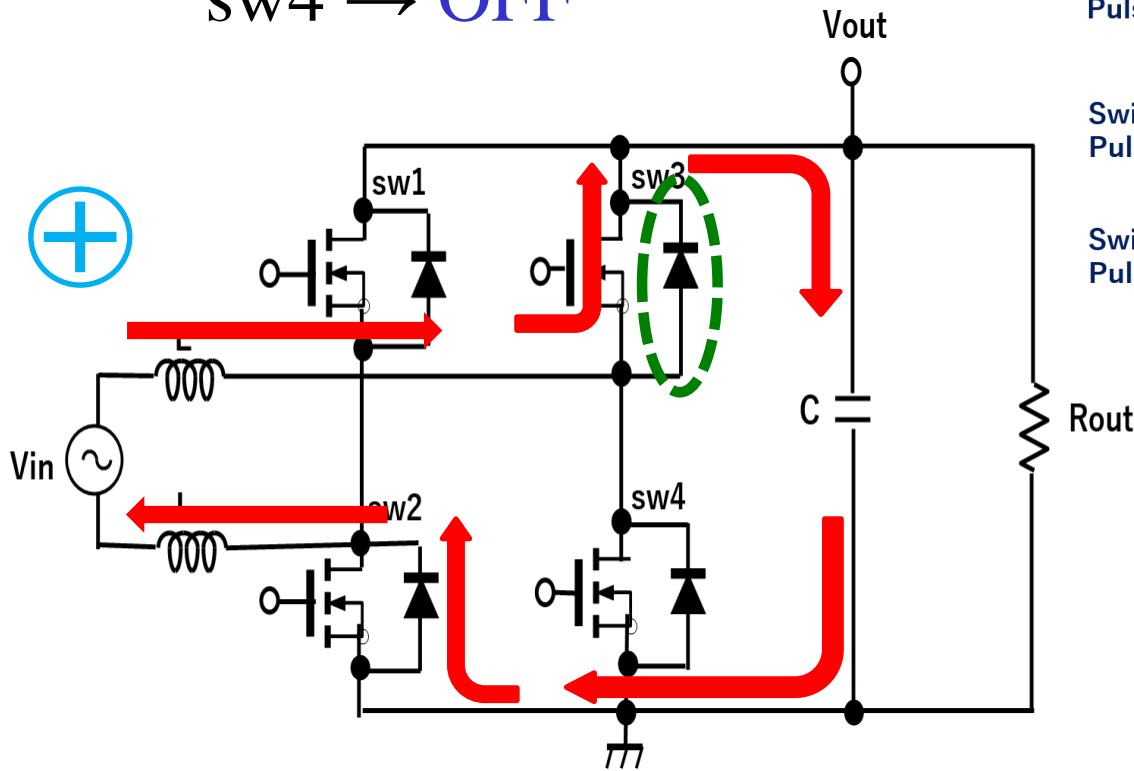

Operation of Full-Bridgeless Circuit (3/4)



$$V_{in} > V_{Lim}$$

sw1 → OFF

sw2 → ON

sw3 → ON

sw4 → OFF

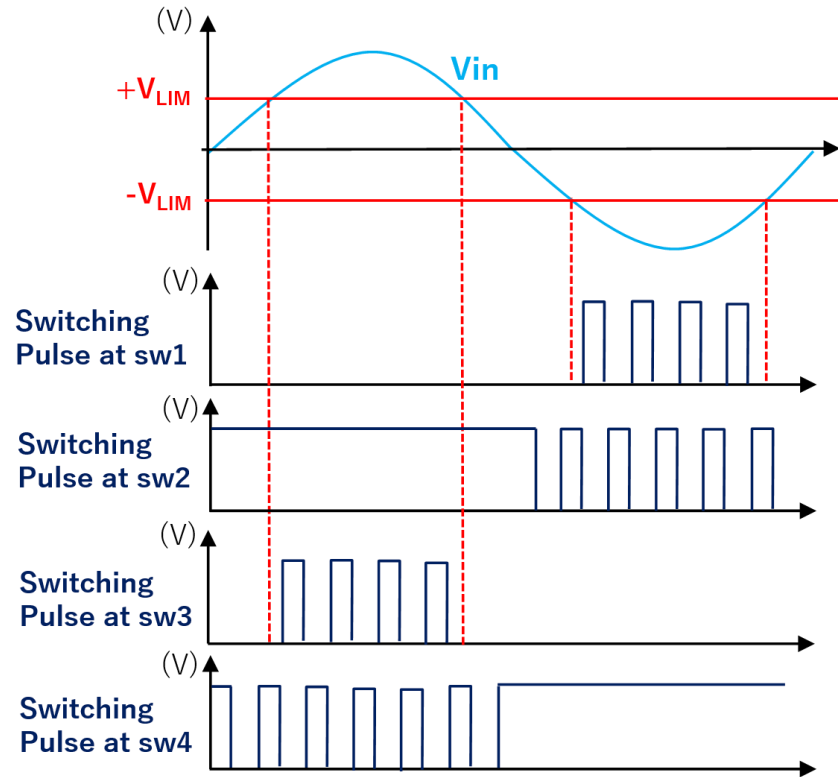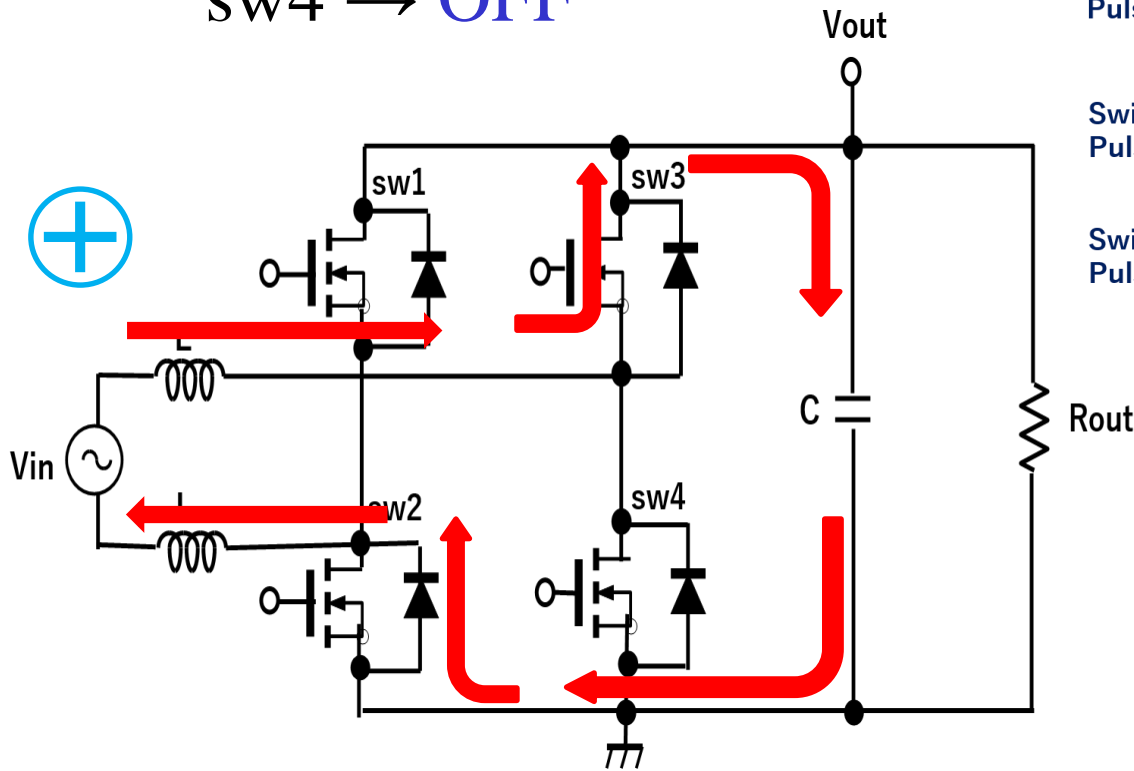

Operation of Full-Bridgeless Circuit (4/4)



$V_{in} > V_{Lim}$

sw1 → OFF

sw2 → ON


sw3 → OFF

sw4 → ON

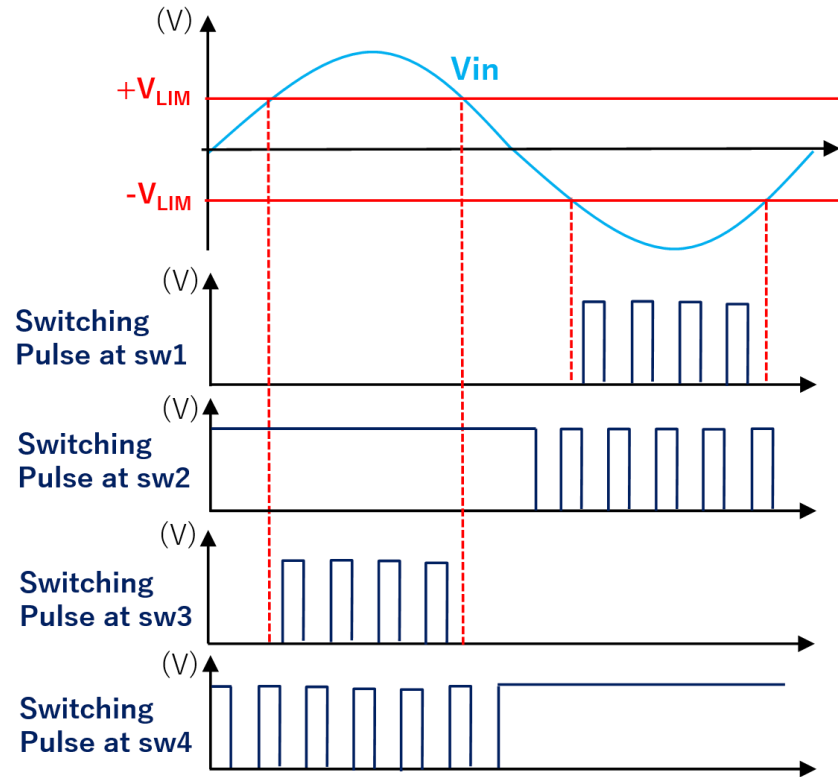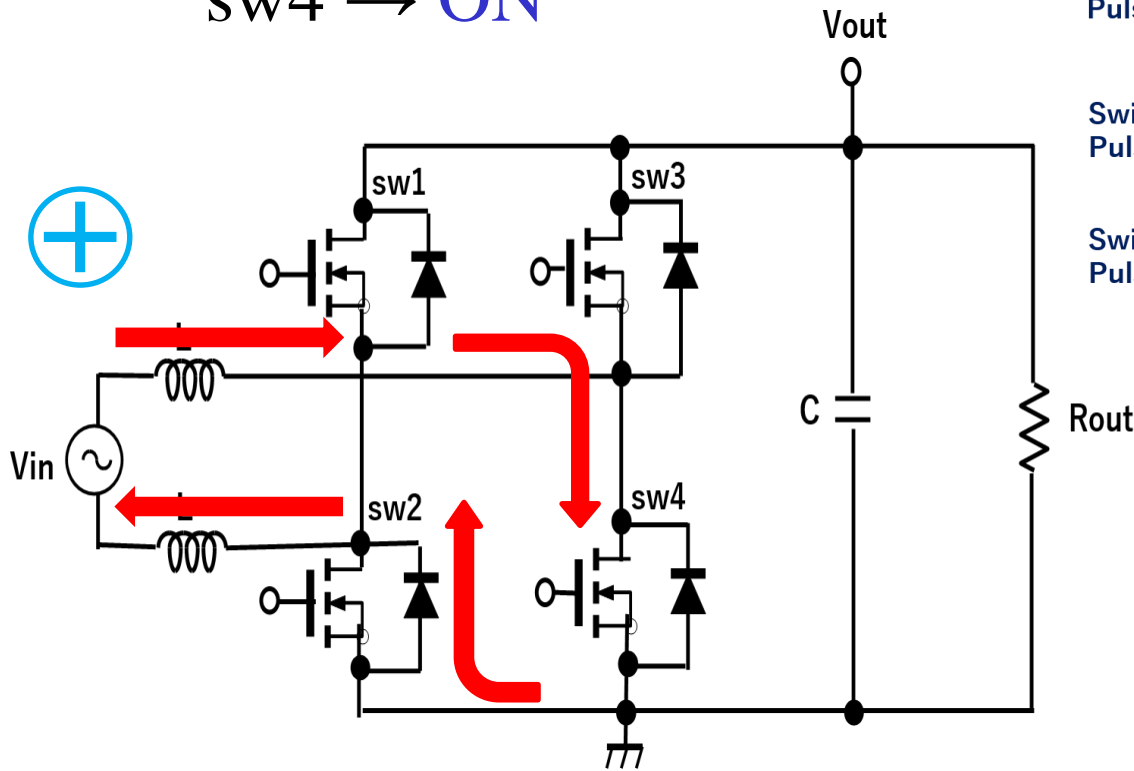

Efficiency of Full-Bridgeless PFC

AC $V_{in}=100[V]$ @50Hz

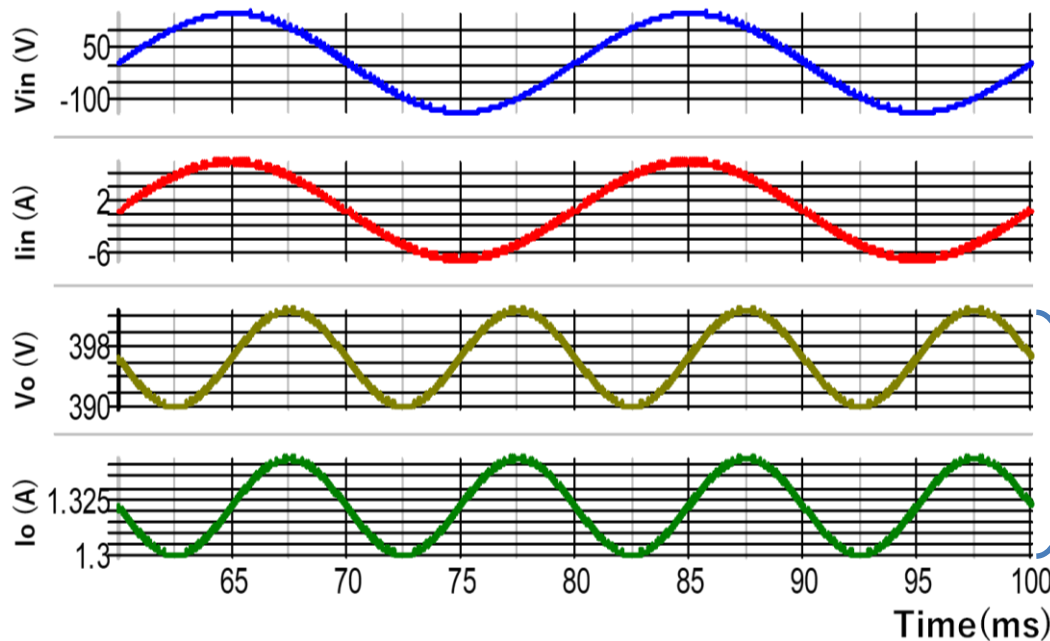

Parameters	Simulation Value
I_{in}	5.25[A]
Input power	525[W]
Output power	523[W]


Expand

$$V_o = 396V \pm 6V$$

$$I_o = 1.32A \pm 0.02A$$

$$\begin{aligned}
 \text{efficiency} &= \frac{\text{Output power}}{\text{Input power}} \times 100 = \frac{523}{526} \times 100 \\
 &= 99.6\% \quad (> 94.3\% \text{ Conventional} > 82.5\% \text{ Basic})
 \end{aligned}$$

Efficiency and Input Voltage

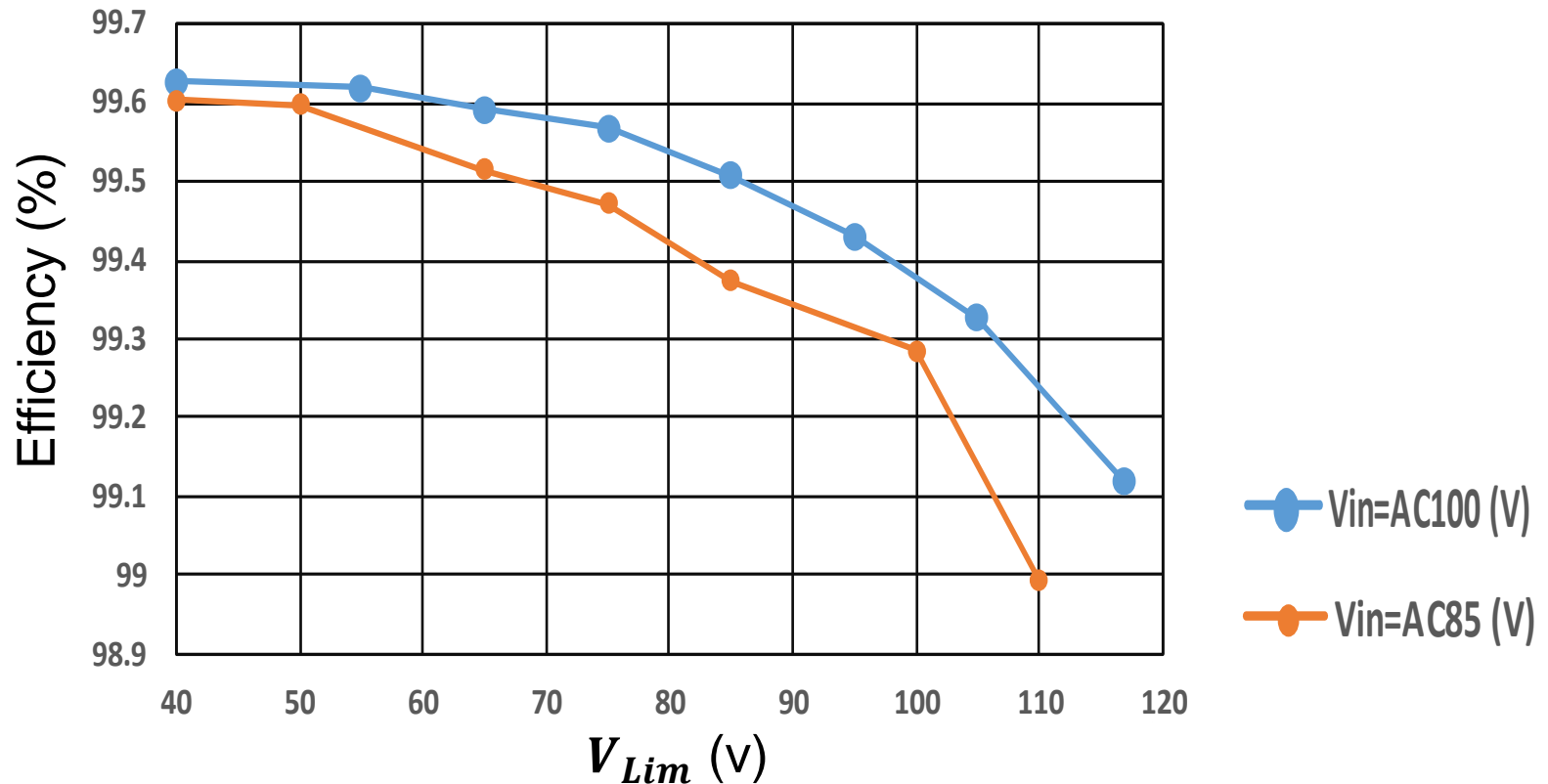

V_{Lim} High



Efficiency Low

Input Voltage High



Efficiency High


Outline

- Background and Purpose
- Basic PFC Circuit
- Conventional PFC (Half-bridgeless) Circuit
- Proposed PFC (Full-bridgeless) Circuit
- **Conclusion**

Conclusion

- Replace diode with MOSFET

Loss reduction → Efficiency improvement

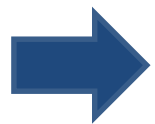

Basic PFC efficiency 82.5%

Conventional PFC (Half-bridgeless) 94.3%

Proposed PFC (Full-bridgeless) 99.6%

- Prevent reverse current in Full-bridgeless PFC by using V_{Lim} controller circuit



Thank you
for your attention!

Question and Advice (1/2)

1. Since the PFC circuit has an inductor, why does the input voltage and input current waveform have the same phase ?

➡ By repeatedly turning on and off the switch (MOSFET), the input current waveform has the same in-phase as the input voltage waveform.

Question and Advice (2/2)

2. In the simulation, replace the ideal switch with an actual MOSFET and try to compare efficiency again.

➡ In the near future I will replace the ideal switch with the actual MOSFET and try to compare efficiency again.

3. In V_{Lim} controller circuit (P18), is the position of the second V_{Lim} correct?

➡ yes, the position is correct.